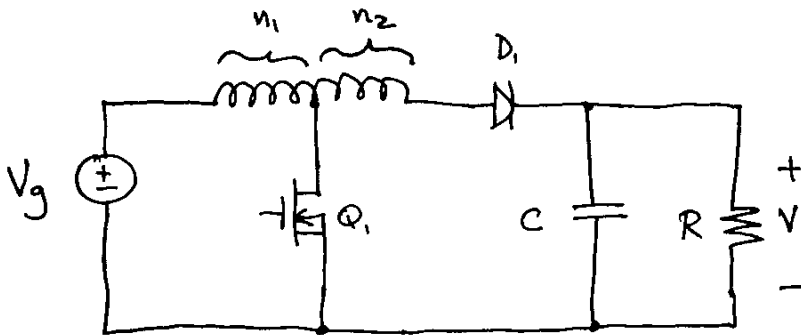


Solution to Problem 6.1

R.W. Erickson  
Fundamentals of  
Power Electronics


Analysis of tapped-inductor boost converter




Inductance of entire  $(n_1+n_2)$  turn inductor is  $L$

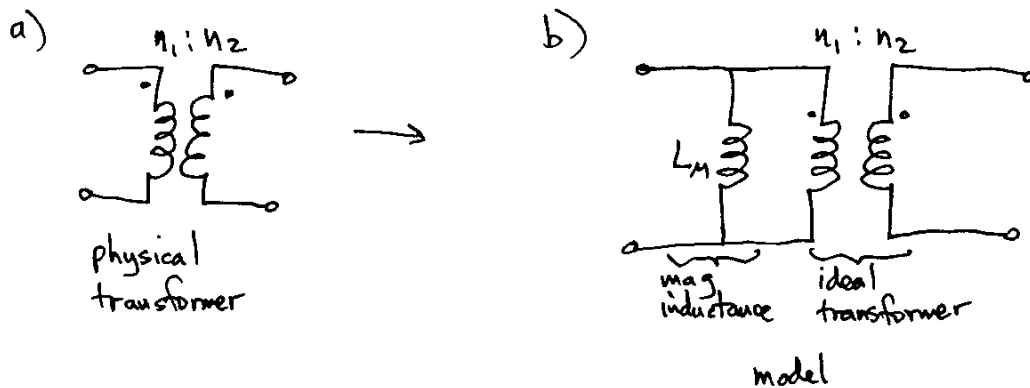- a) Sketch an equivalent circuit model for the tapped inductor, which includes an ideal transformer and a magnetizing inductance.


The equivalent circuit model of Fig. 6.17:



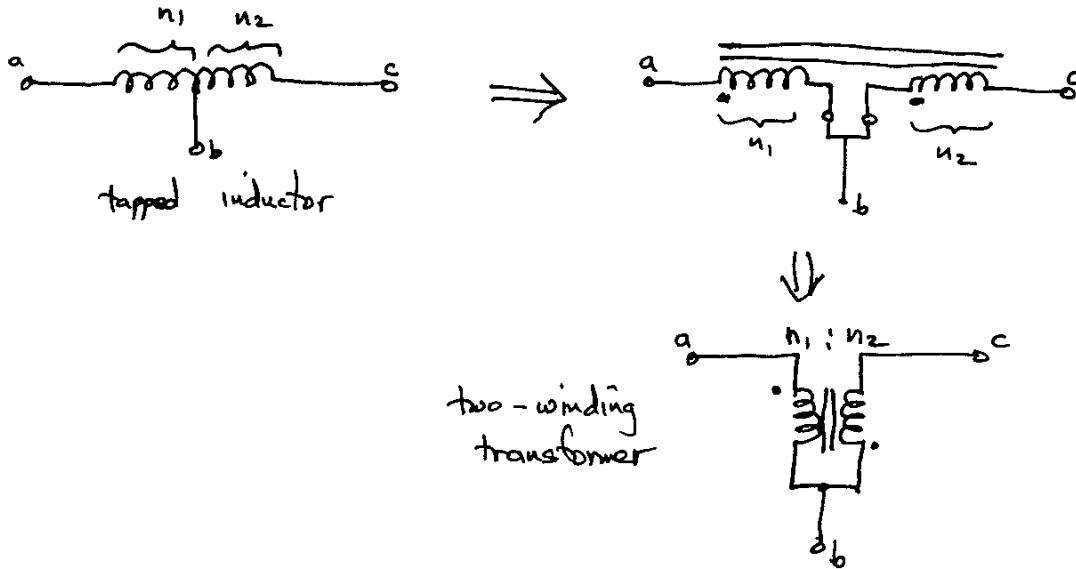The tapped inductor can be viewed as a two-winding transformer:



Use two-winding transformer model:

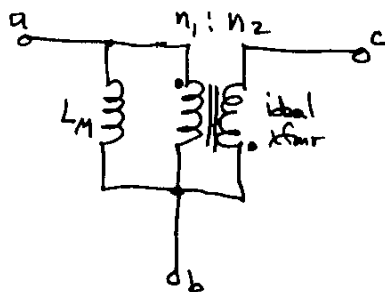


What is the value of  $L_M$ ?

We are given that the inductance of the entire  $(n_1+n_2)$  turn winding is  $L$ . So we should choose the value of  $L_M$  such that the inductance between terminals  $a$  and  $c$ , with terminal  $b$  open, is  $L$ .

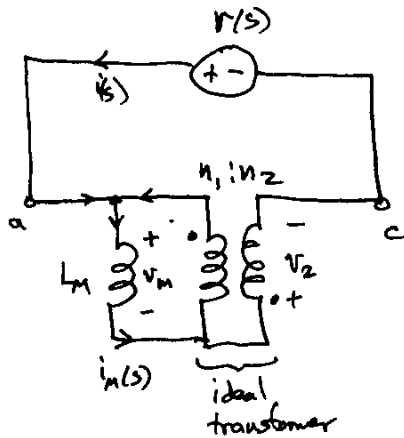(2)

Measurement of inductance between terminals a and c:  
 inject ac voltage  $v$ , measure current  $i$ . Impedance  
 is  $Z(s) = sL = \frac{v(s)}{i(s)}$



• current in  $n_2$  winding is  $i(s)$ , going into dot

$\Rightarrow$  current in  $n_1$  winding is  $\frac{n_2}{n_1} i(s)$ , coming out of dot

$\Rightarrow$  node equation for magnetizing current  $i_M(s)$ :

$$i_M(s) = i(s) + \frac{n_2}{n_1} i(s) = \frac{n_1 + n_2}{n_1} i(s)$$

$\Rightarrow$  voltage across inductor is

$$v_M(s) = sL_M i_M(s) = sL_M \frac{n_1 + n_2}{n_1} i(s)$$

$\Rightarrow$  voltage across  $n_2$  winding is  $v_2 = \frac{n_2}{n_1} v_M(s) = \frac{n_2(n_1 + n_2)}{n_1^2} sL_M i(s)$   
 (positive at dot)

$\Rightarrow$  voltage  $v(s)$  is

$$\begin{aligned} v(s) &= v_M(s) + v_2(s) = sL_M i(s) \left( \frac{n_1 + n_2}{n_1} + \frac{n_2(n_1 + n_2)}{n_1^2} \right) \\ &= s \left( \frac{n_1 + n_2}{n_1} \right)^2 L_M i(s) \end{aligned}$$


(3)

So the inductance between terminals a and c is

$$L = \left( \frac{n_1 + n_2}{n_1} \right)^2 L_M$$


$$\Rightarrow L_M = \left( \frac{n_1}{n_1 + n_2} \right)^2 L$$

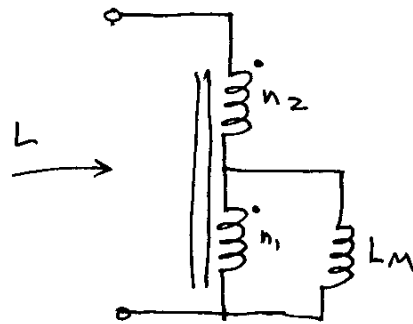an easier way: reflect  $L_M$  through auto transformer



$$L = \left( \frac{n_1 + n_2}{n_1} \right)^2 L_M$$

So the converter circuit becomes

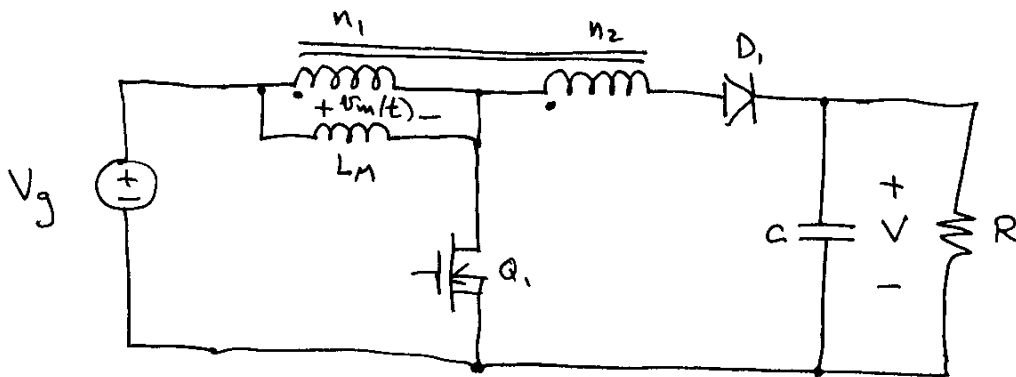


(4)

b) Determine an analytical expression for  $M(D) = \frac{V}{V_g}$  in CCM, no losses.


Apply volt-second balance to LM

$0 < t < DT_s$   $Q_1$  on,  $D_1$  off

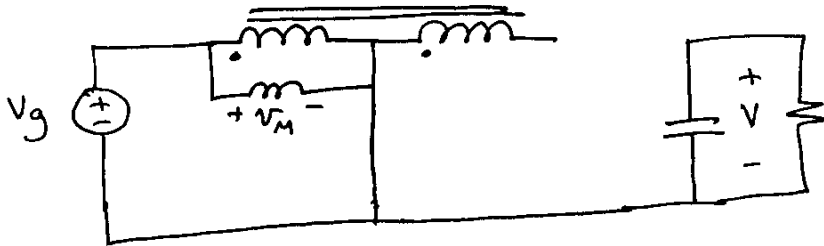


$$v_M = V_g$$

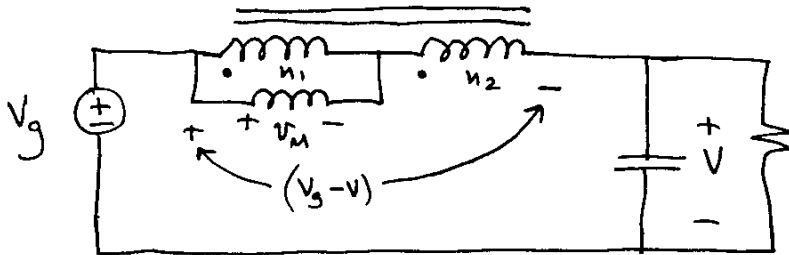$DT_s < t < T_s$   $Q_1$  off,  $D_1$  on


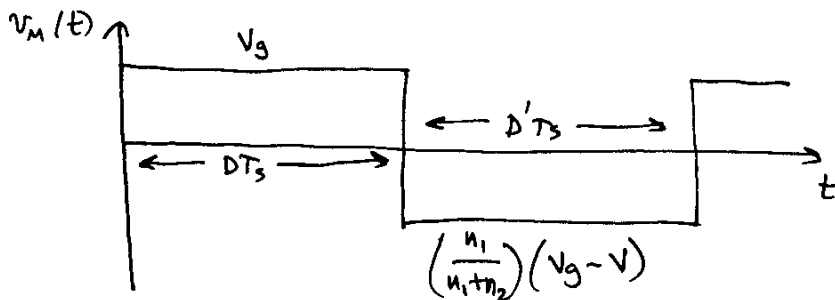
$$v_M = \frac{n_1}{n_1 + n_2} (V_g - V)$$



$$\langle v_M \rangle = 0 = DV_g + D' \left( \frac{n_1}{n_1 + n_2} \right) (V_g - V)$$

5

Solve for  $V$ :


$$V D' \left( \frac{n_1}{n_1+n_2} \right) = DV_g + D' V_g \frac{n_1}{n_1+n_2}$$

$$\Rightarrow \frac{V}{V_g} = \frac{D + D' \left( \frac{n_1}{n_1+n_2} \right)}{D' \left( \frac{n_1}{n_1+n_2} \right)} = \frac{1}{D'} \cdot \left[ D \frac{n_1+n_2}{n_1} + D' \right]$$

$$M(D) = \left( \frac{1}{D'} \right) \left( 1 + \frac{n_2}{n_1} D \right)$$

which differs from the conventional untapped ( $n_2=0$ ) boost  $M(D)$  by a factor of  $\left( 1 + \frac{n_2}{n_1} D \right)$ .

c)

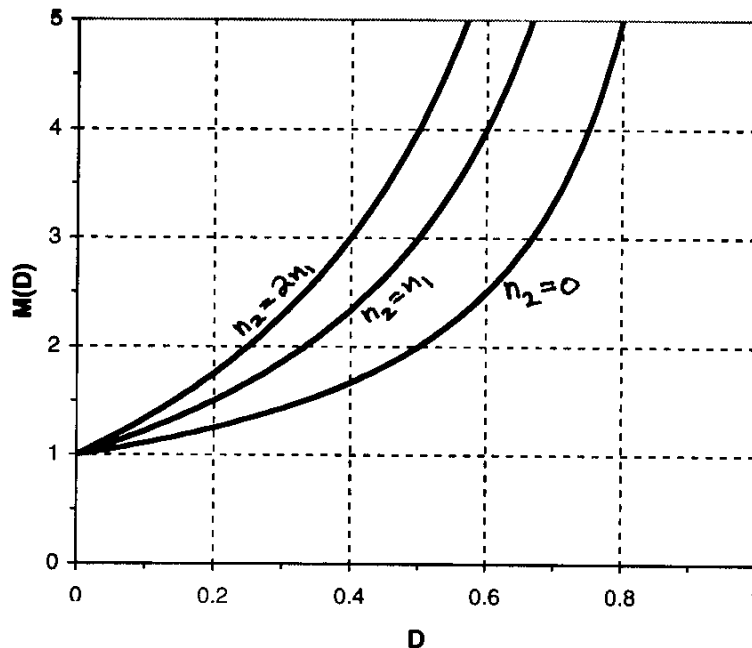

Tapped inductor boost produces increased output voltage.

(6)