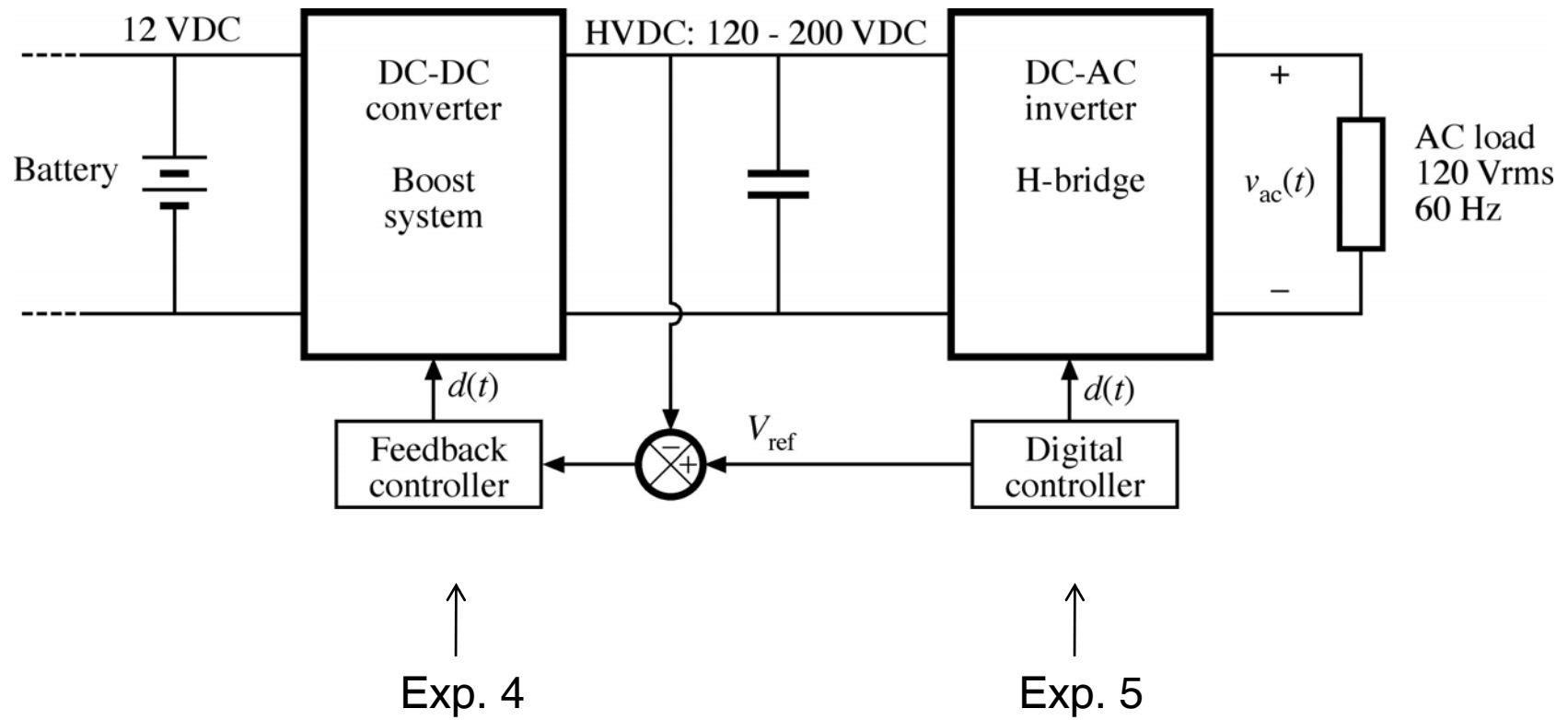


# Lecture 10

ECEN 4517/5517

## Experiment 5

### Inverter system



# Schedule

---

This week: finish Lab 4


Exp. 5 prelab due via D2L by next Tuesday 4/10 12pm

Exp. 4 report due via D2L by Friday, April 20, 5 pm

Final demo: complete PV system working outside, the morning of Thursday May 3 (Expo)

# Exp. 5

## H-bridge inverter, off grid

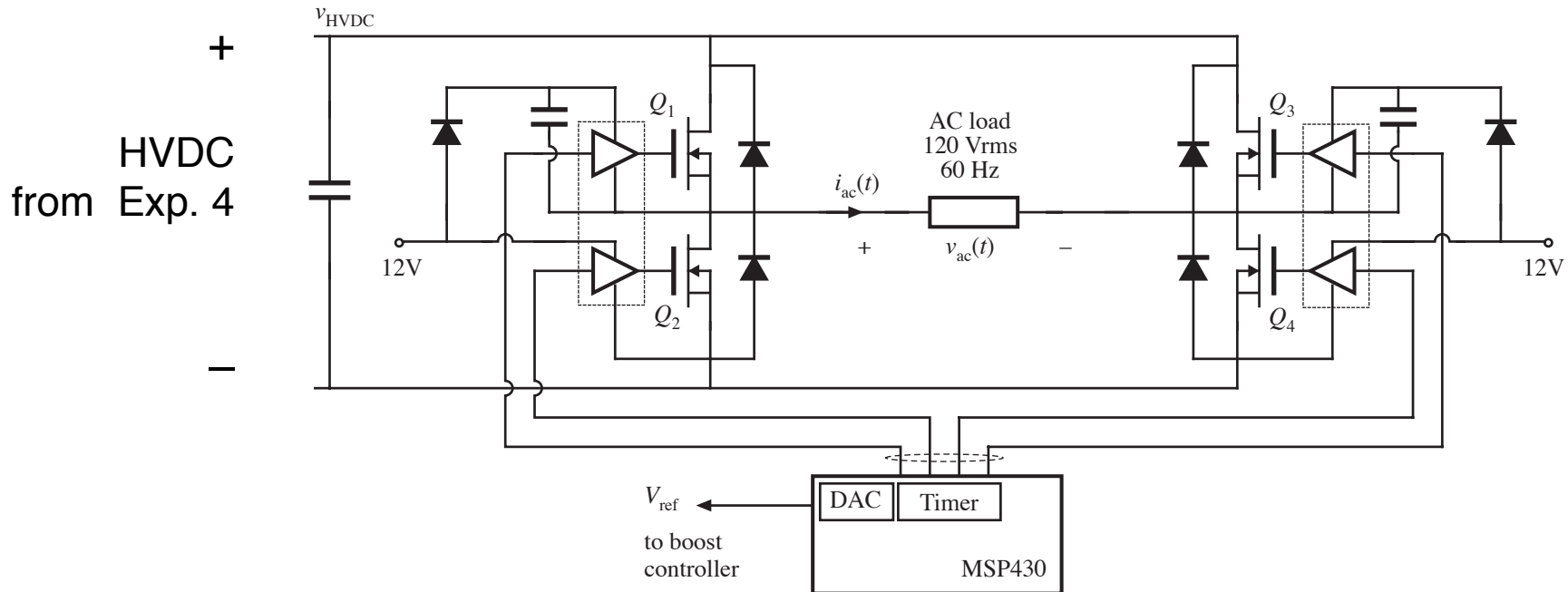

- Filtering of ac output not explicitly shown
- Need MOSFETs and half-bridge gate drivers
- Grid-tied: control  $i_{ac}(t)$
- Off-grid: control  $v_{ac}(t)$


### Exp. 5: off-grid inverter

- Demonstrate modified sine-wave inverter (required)
- Demonstrate PWM inverter (extra credit)
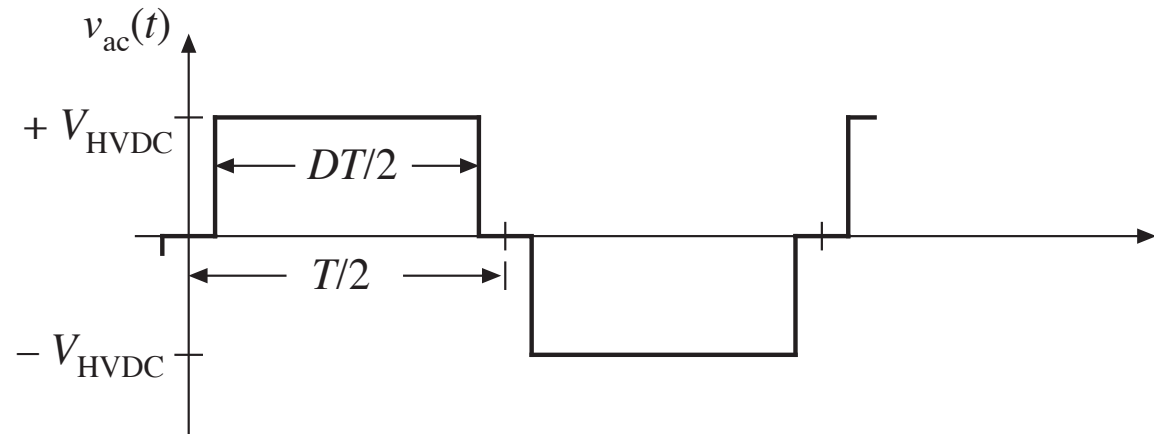
# “Modified Sine-Wave” Inverter

$v_{ac}(t)$  has a rectangular waveform

Inverter transistors switch at 60 Hz,  
 $T = 8.33$  msec



RMS value of  $v_{ac}(t)$  is:


$$V_{ac,RMS} = \sqrt{\frac{1}{T} \int_0^T v_{ac}^2(t) dt} = \sqrt{D} V_{HVDC}$$

- Choose  $V_{HVDC}$  larger than desired  $V_{ac,RMS}$
- Can regulate value of  $V_{ac,RMS}$  by variation of  $D$
- Waveform is highly nonsinusoidal, with significant harmonics
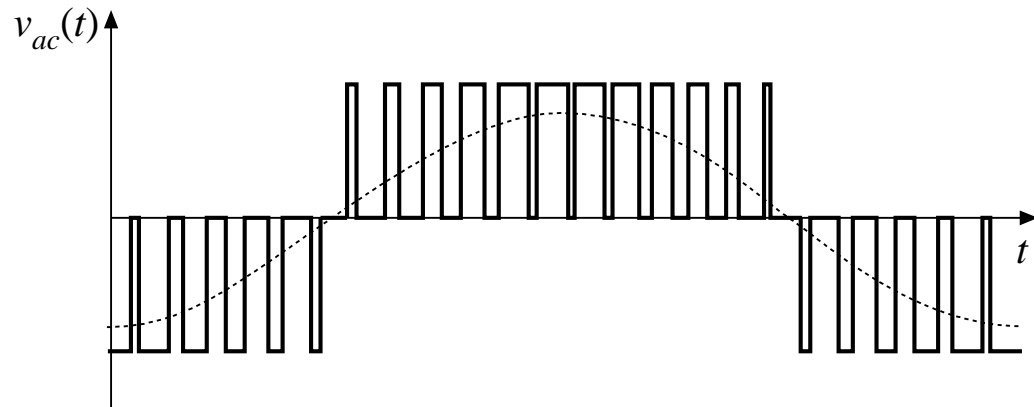
# PWM Inverter


Average  $v_{ac}(t)$  has a sinusoidal waveform

Inverter transistors switch at frequency substantially higher than 60 Hz




- Choose  $V_{HVDC}$  larger than desired  $V_{ac,peak}$
- Can regulate waveshape and value of  $V_{ac,RMS}$  by variation of  $d(t)$  (programming inside microcontroller)
- Can achieve sinusoidal waveform, with negligible harmonics
- Higher switching frequency leads to more switching loss and need to filter high-frequency switching harmonics and common-mode currents
- For the same  $V_{ac,RMS}$ , need larger  $V_{HVDC}$

# Two ways to generate a PWM sinusoid

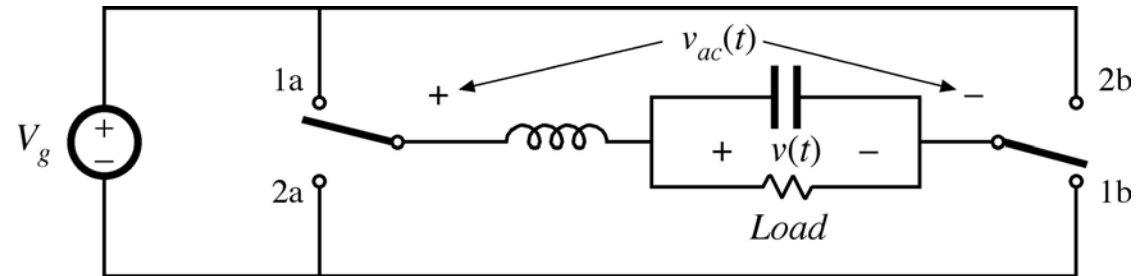


- (a) Operate left and right sides with same (complementary) gate drive signals

$$v(t) = (2d(t) - 1) V_g$$

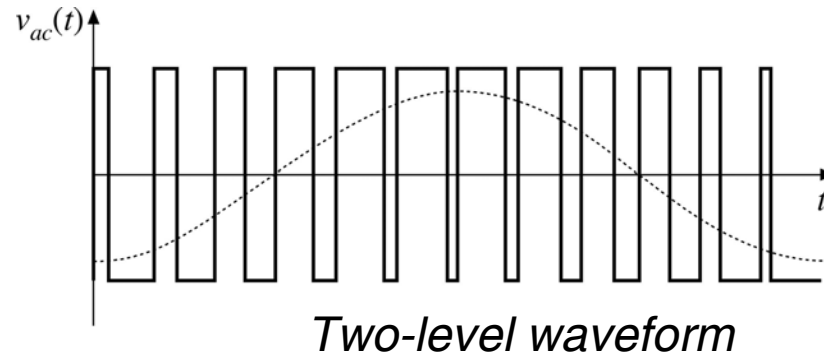

- (b) PWM one side, while other side switches at 60 Hz


$$v(t) = \pm d(t) V_g$$

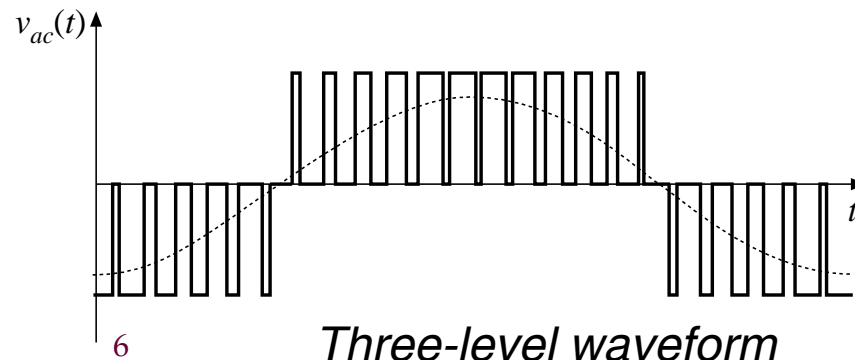
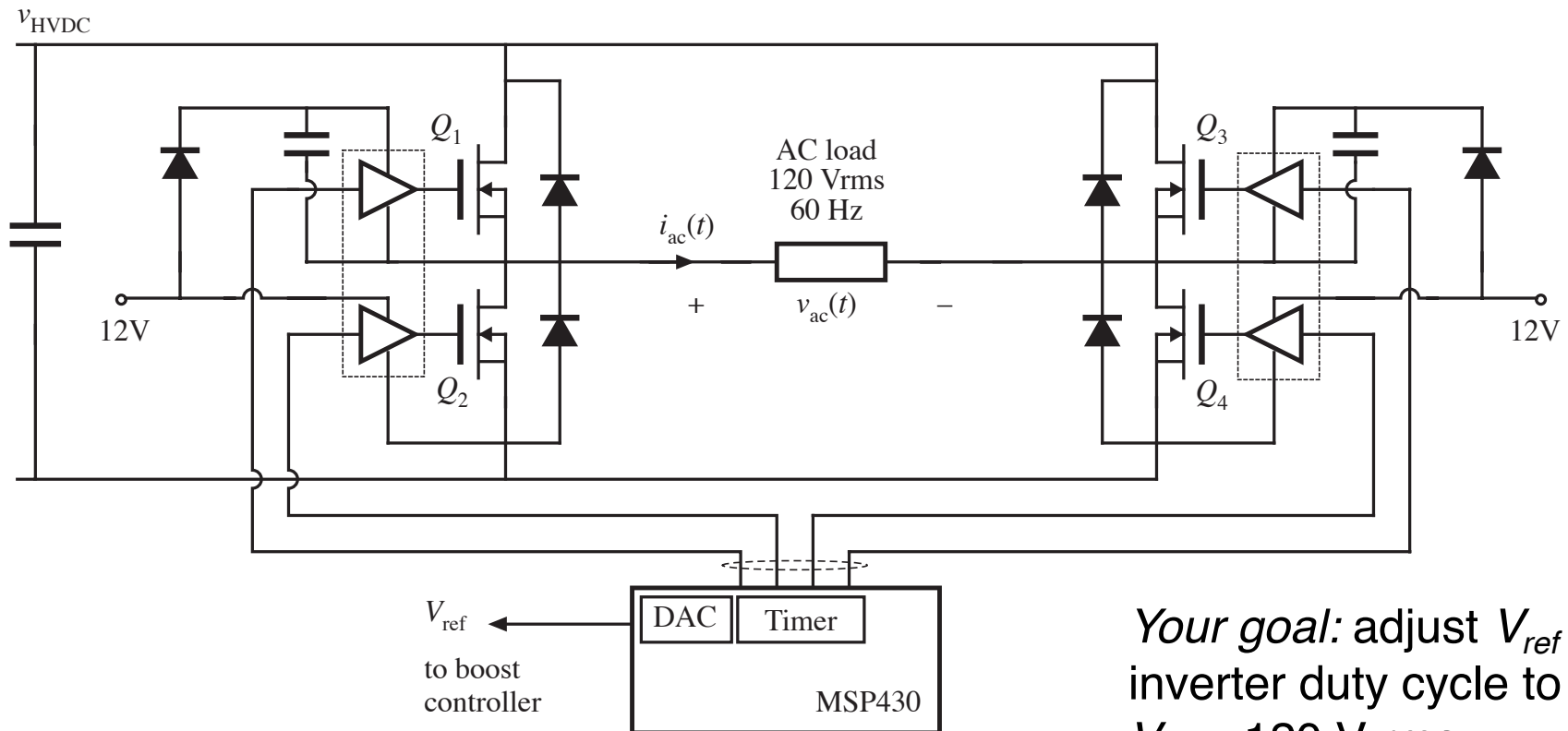
# Controlling the inverter


MSP430 generates logic signals to control the four gate drivers

- Control MSP430 timer (you could use A or B or simply use logic outputs) to generate MOSFET drive signals



*Your goal:* adjust  $V_{ref}$  and inverter duty cycle to obtain  $V_{ac} = 120 \text{ V rms}$

# Gate drive timing

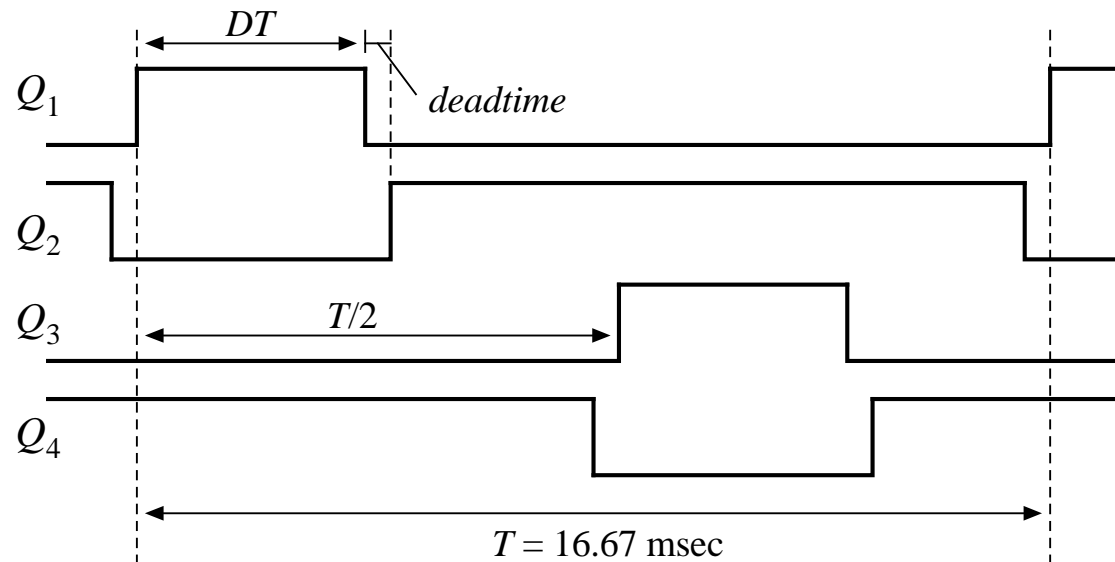

- For modified sine wave inverter: switch once per ac half cycle. Adjust duty cycle to control rms voltage.
- You decide how to do this / which timer to use
- Require deadtime  $>$  (switching/delay times of MOSFETs plus gate drivers); otherwise, simultaneous conduction of  $Q_1$  and  $Q_2$  causes “shoot-through” current that can damage MOSFETs.



# Half-bridge Gate Drivers

example: FAN 73832


Contains two MOSFET drivers:

- Low side driver
- High side driver

High side driver includes

- Level-shifting circuitry
- Provisions for bootstrap power supply

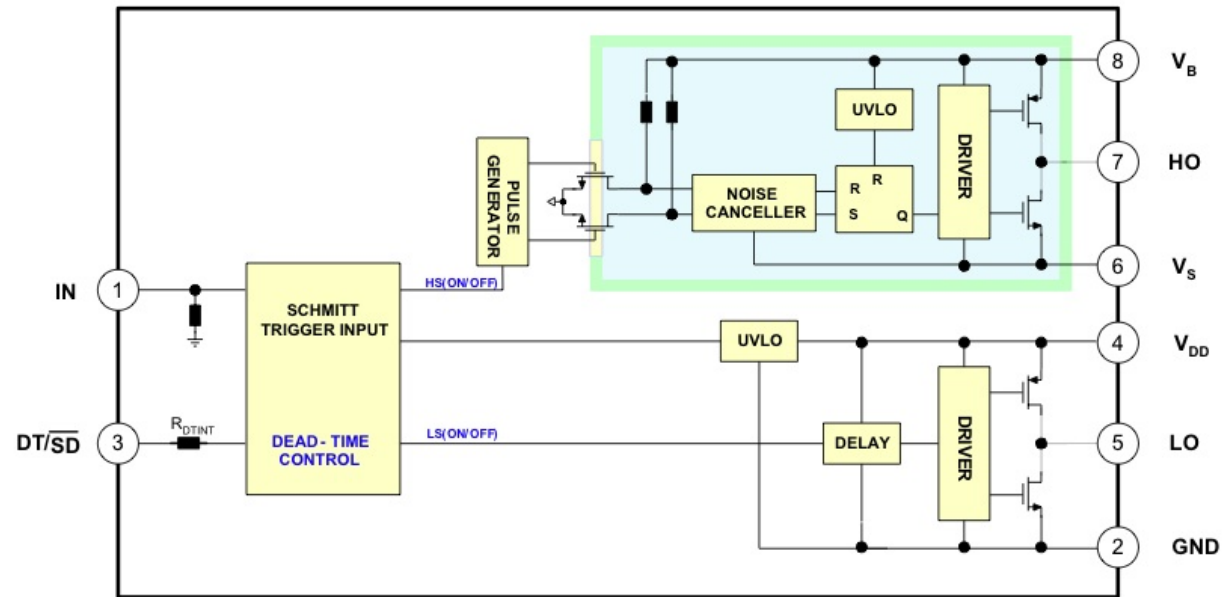Undervoltage lockout circuitry holds MOSFETs off when driver power supply is below threshold



FAN73832 Rev:00

Figure 3. Functional Block Diagram of FAN73832

# Half bridge gate driver circuit example

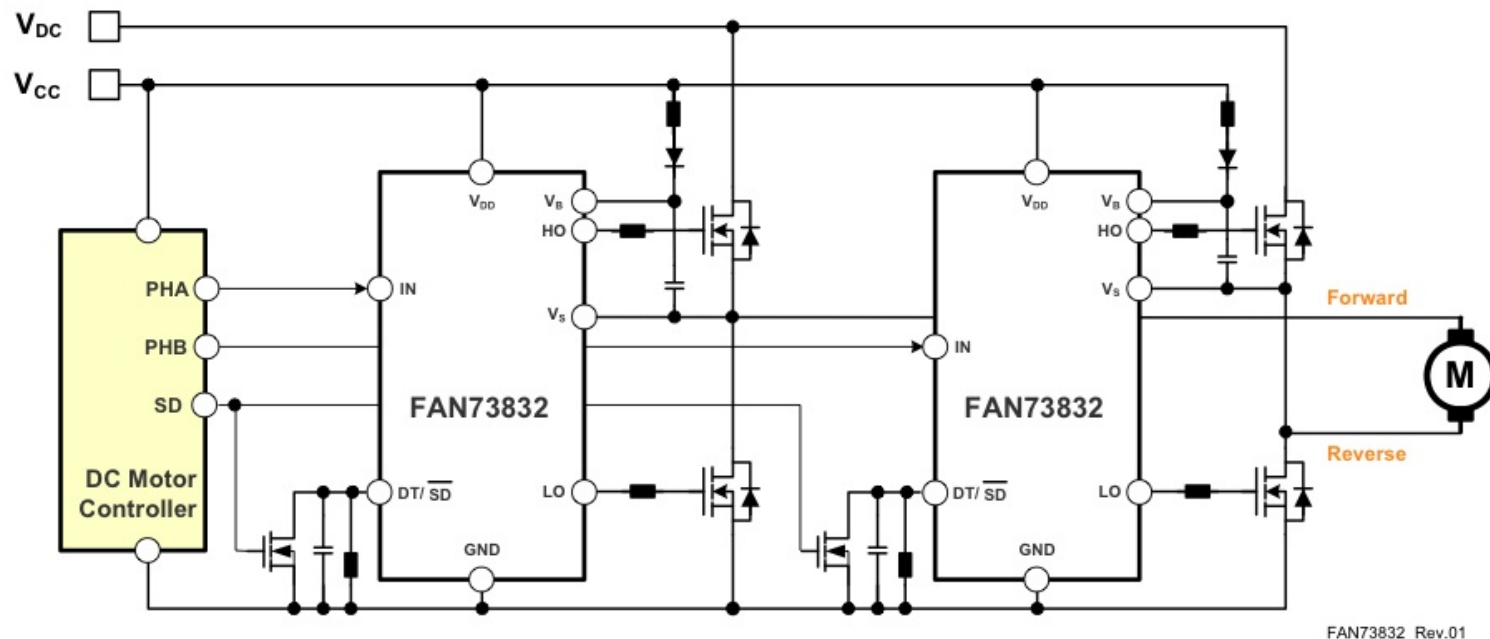



Figure 2. Application Circuit for Full-Bridge DC Motor Driver

High side circuitry includes external diode and capacitor for bootstrap power supply


To charge bootstrap capacitor, low side MOSFET must conduct

In this example,  $V_{CC} = 12\text{ V}$


# Half-Bridge Driver Example 2: IR21094

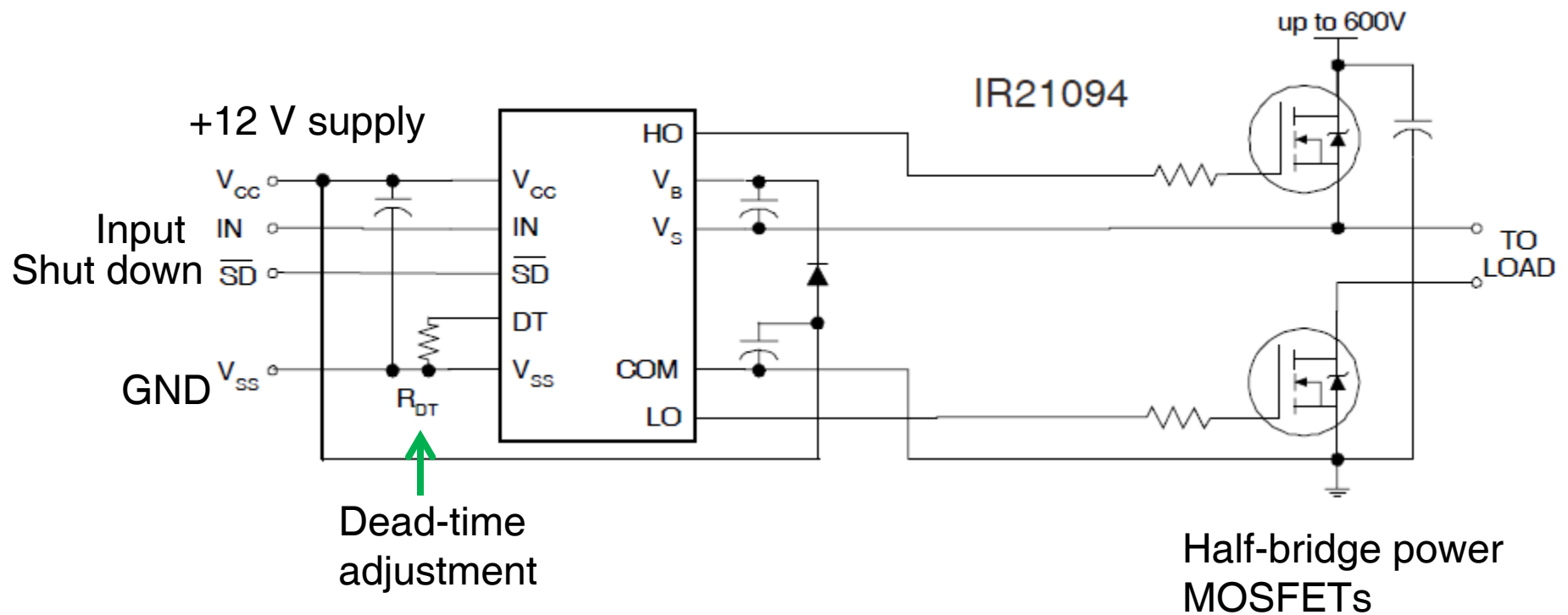

# Half-Bridge Driver Example 2: IR2109

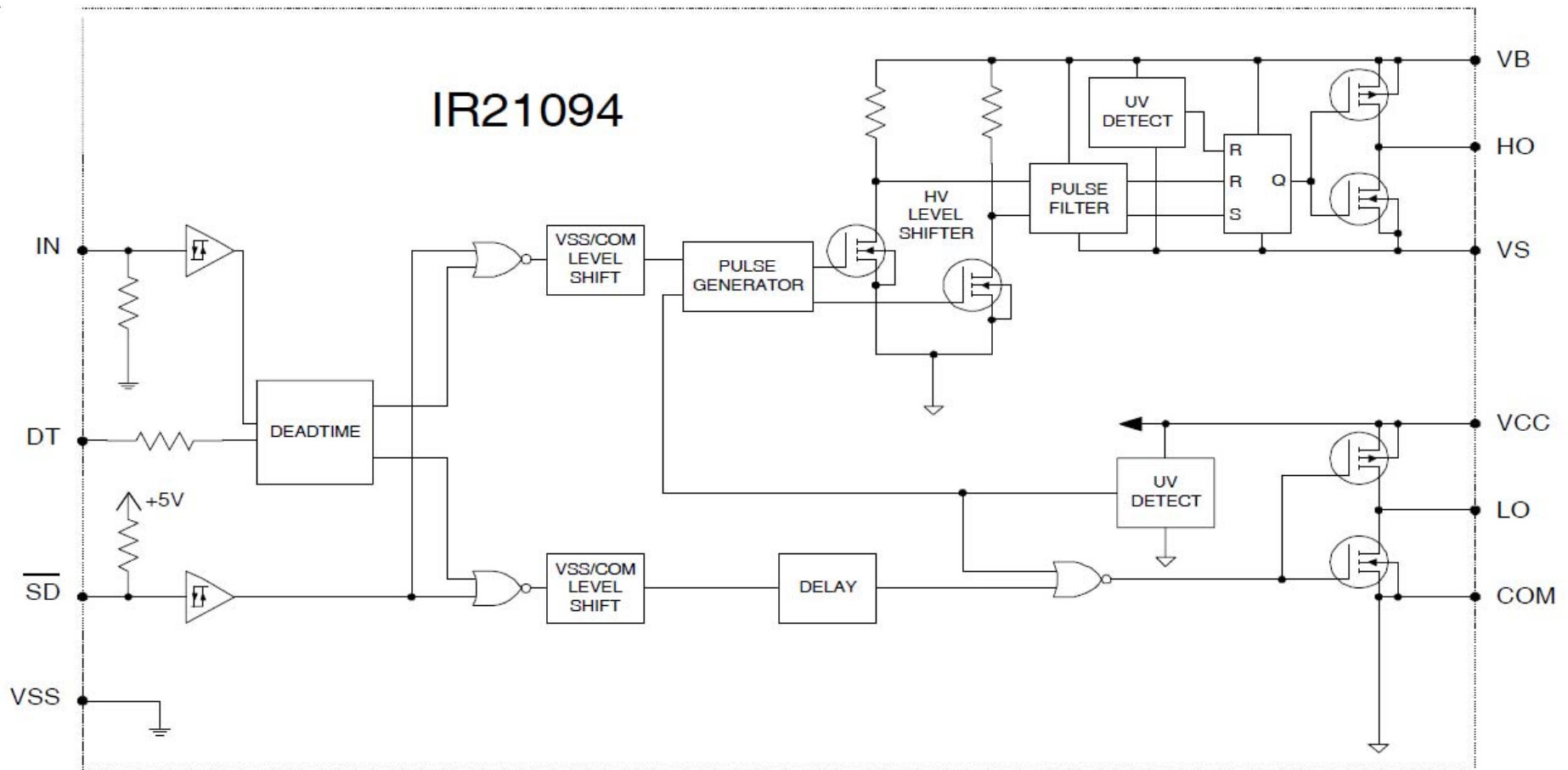

# Filtering the ac output

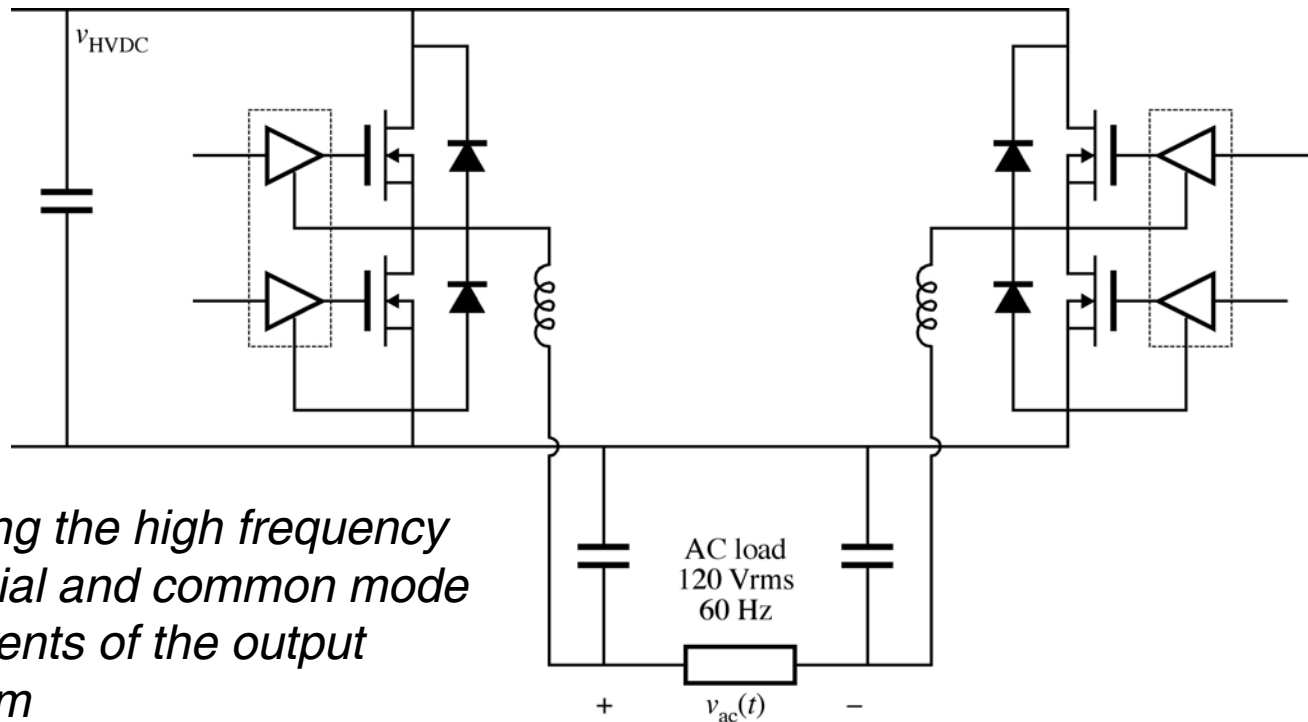

*Removing the high frequency differential and common mode components of the output waveform*

*Note: the “Kill-a-Watt” power meters cannot tolerate high frequency components in the ac voltage waveform. Do not connect these meters to an unfiltered inverter output!*