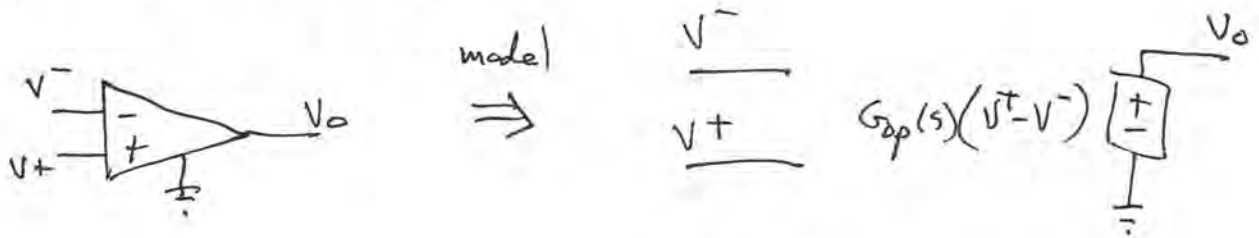


Feedback analysis and compensator design example: RWE ①

Investigation of an op amp lead compensator circuit

9/10/12
Lecture notes
ECEN4517

The op amp in the parts kit (ALD 2702) is a CMOS rail-to-rail input op amp with 1 MHz gain-bandwidth product.




$$G_{op}(s) = G_0 \frac{1}{1 + \frac{s}{\omega_{op}}}$$

$$f_{op} = \frac{\omega_{op}}{2\pi} = 2 \text{ Hz}$$

$$G_0 = 5 \cdot 10^5 \Rightarrow 114 \text{ dB}$$



The gain at 1 MHz is

$$(5 \cdot 10^5) \frac{1}{\left\| 1 + \frac{j 2\pi 10^6}{2\pi \cdot 2} \right\|} = \frac{5 \cdot 10^5}{5 \cdot 10^5} = 1$$

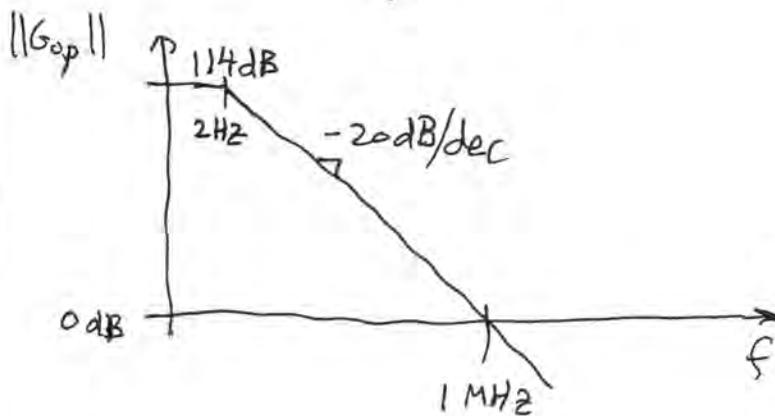


Let's consider a lead compensator (PD) having a transfer function
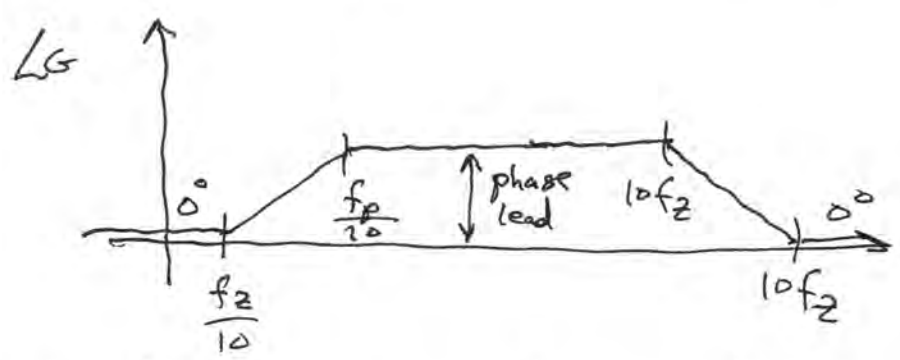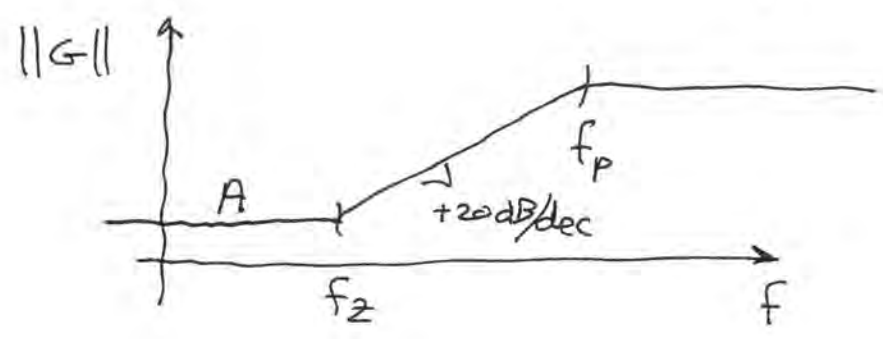
$$G(s) = A \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}$$



Such circuits are sometimes added to feedback loop compensators, to improve phase margin.

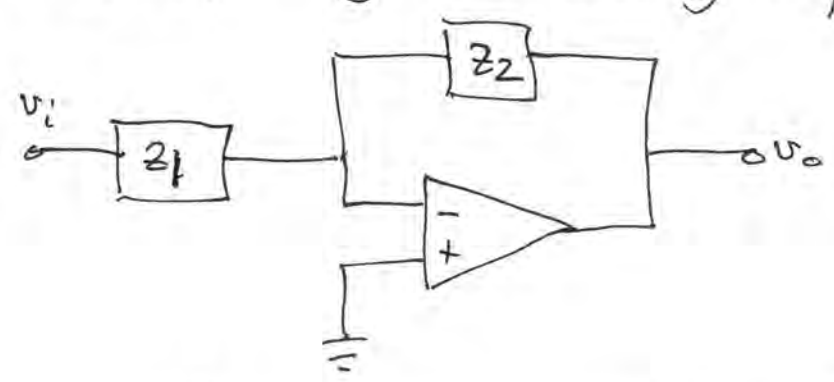A realization using an inverting amplifier:




$$G(s) = - \frac{Z_2}{Z_1} = \frac{v_o}{v_i}$$

$$\|G\|_{dB} = \left\| \frac{Z_2}{Z_1} \right\|_{dB} = \|Z_2\|_{dB} - \|Z_1\|_{dB}$$



(this also adds a minus sign)

Let's make the impedances do this:

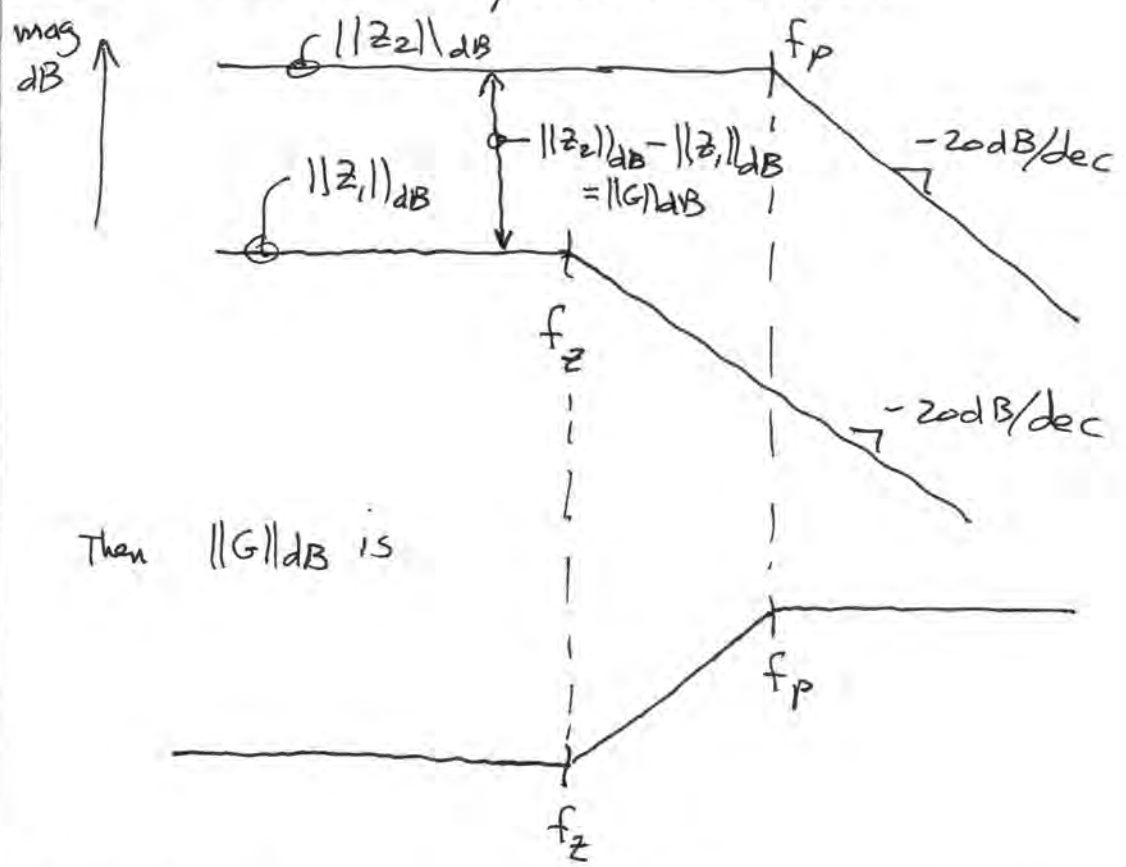

Then $\|G\|_{dB}$ is

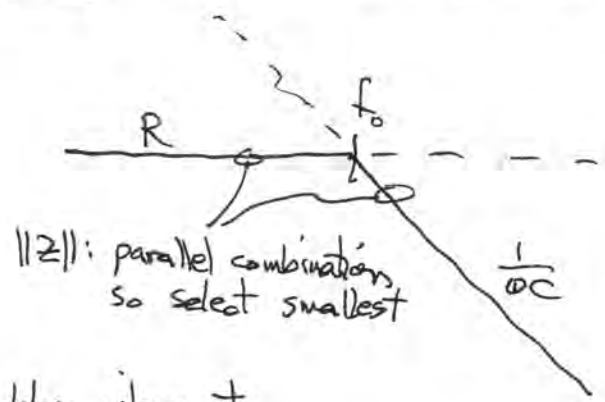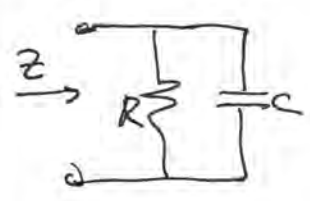Realization of Z_1, Z_2 : a parallel R and C will work



$\|Z\|$: parallel combination so select smallest

At f_0 : asymptotes intersect


$$R = \frac{1}{2\pi f_0 C} \Rightarrow f_0 = \frac{1}{2\pi RC}$$

Suppose we want $A = 10 \Rightarrow 20 \text{ dB}$

$$f_z = 10 \text{ kHz}$$


$$f_p = 100 \text{ kHz}$$

4

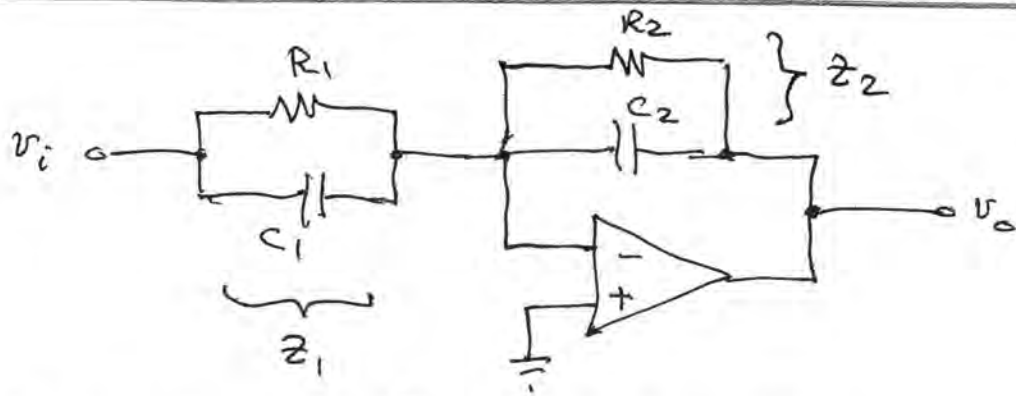

Let's choose (arbitrarily) $R_1 = 1 \text{ k}\Omega$

Then Z_1 and Z_2 should be:

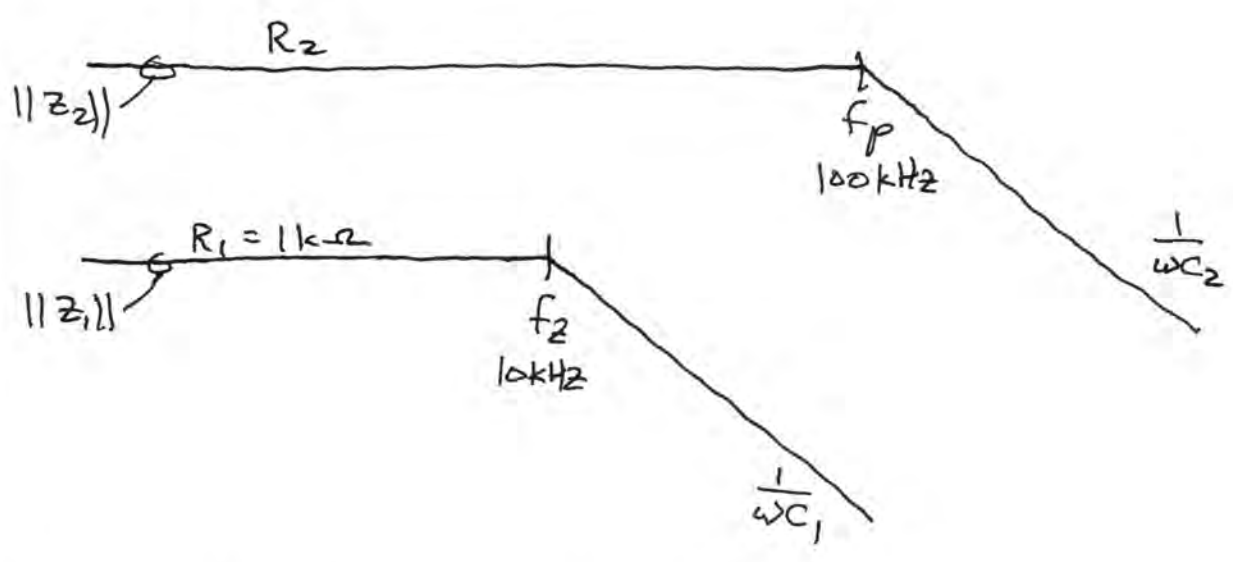

a) we want dc gain $A = 10$

At dc, $Z_1 = R_1$ and $Z_2 = R_2$ so $A = \frac{R_2}{R_1}$

\Rightarrow need $R_2 = 10 \text{ k}\Omega$

b) we want $f_2 = 10 \text{ kHz}$

at f_2 , $R_1 = \frac{1}{2\pi f_2 C_1}$

so $C_1 = \frac{1}{2\pi f_2 R_1}$

$= \frac{1}{2\pi (10 \text{ kHz})(1 \text{ k}\Omega)}$

$= 0.016 \mu\text{F}$

Ⓒ we want $f_p = 100\text{kHz}$


$$\text{at } f_p, R_2 = \frac{1}{2\pi f_p C_2}$$

$$\text{so } C_2 = \frac{1}{2\pi f_p R_2}$$

$$= \frac{1}{2\pi (100\text{kHz})(10\text{k}\Omega)}$$

$$= 160\text{pF}$$


so the circuit is

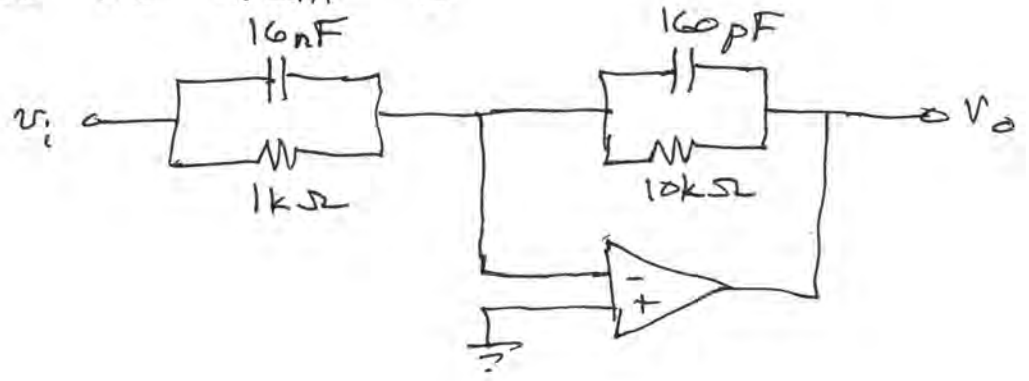


A problem with this design!

we are trying to obtain more gain than the op amp is capable of producing.

The formula $G(s) = -\frac{z_2}{z_1}$ is true for ideal op amps with $G_{op} \rightarrow \infty$ (ie., for $|k_{op}|$ sufficiently large). But at high frequency, G_{op} rolls off.

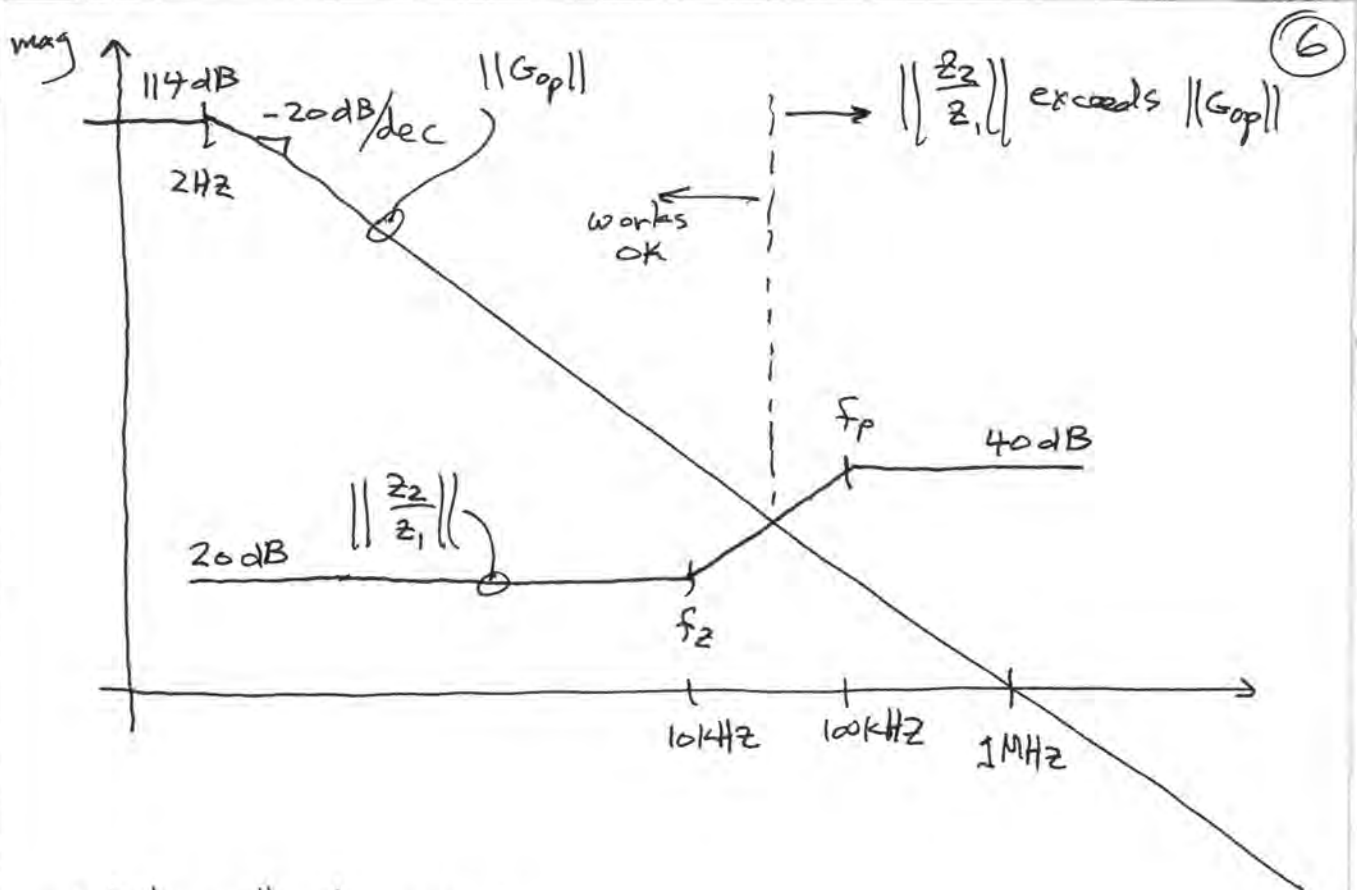

What really happens:

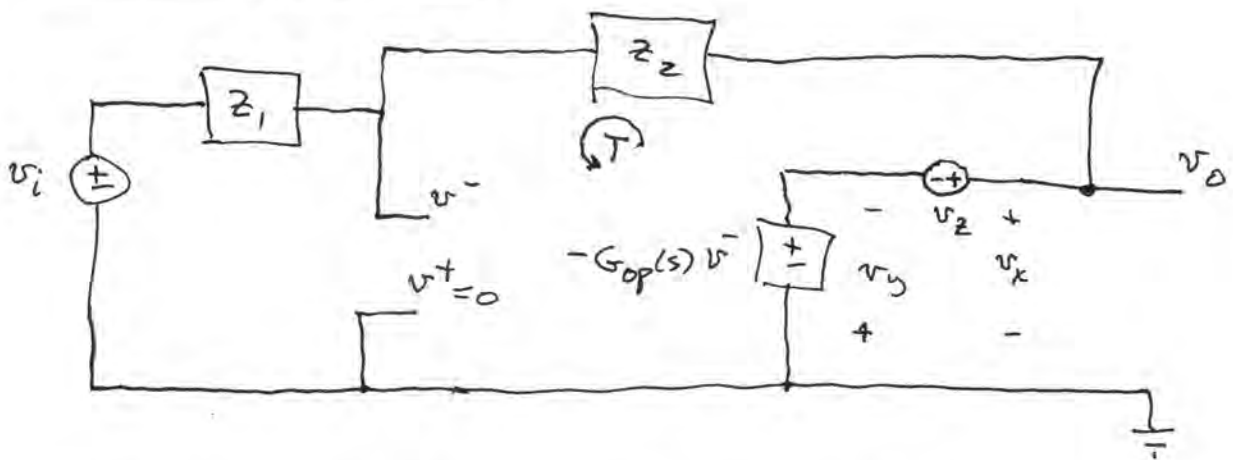

To find loop gain (or measure loop gain):

inject a voltage v_2 at output of op amp
 given v_x , find v_y . Loop gain is $T(s) = \frac{v_y}{v_x}$

with $v_i = 0$

Analysis: with $v_i = 0$, $v^- = \frac{z_1}{z_1 + z_2} v_x$ and $-v_y = -G_{op} v^-$
 so $v_y = \frac{z_1}{z_1 + z_2} G_{op} v_x$ and $T(s) = \frac{z_1}{z_1 + z_2} G_{op}(s)$

The actual gain is


(7)

$$G(s) = \frac{v_o}{v_i} = \underbrace{\left(-\frac{z_2}{z_1}\right)}_{\text{ideal gain}} \underbrace{\left(\frac{T}{1+T}\right)}_{\text{effect of finite } G_{op}}$$


Construct loop gain: $\frac{z_1}{z_1+z_2} = \frac{1}{1+\frac{z_2}{z_1}}$

Since $\|z_2\| \gg \|z_1\|$ everywhere, this is approximately
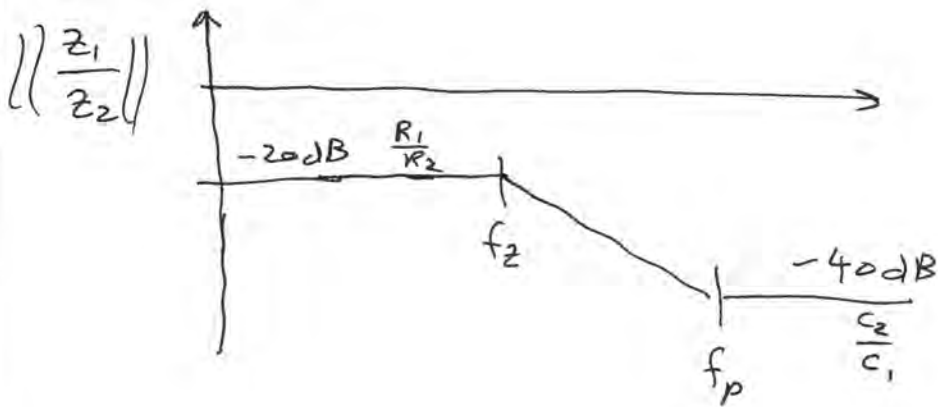
$$\frac{1}{1+\frac{z_2}{z_1}} \approx \frac{z_1}{z_2} \quad \text{which is (ideal gain)}$$



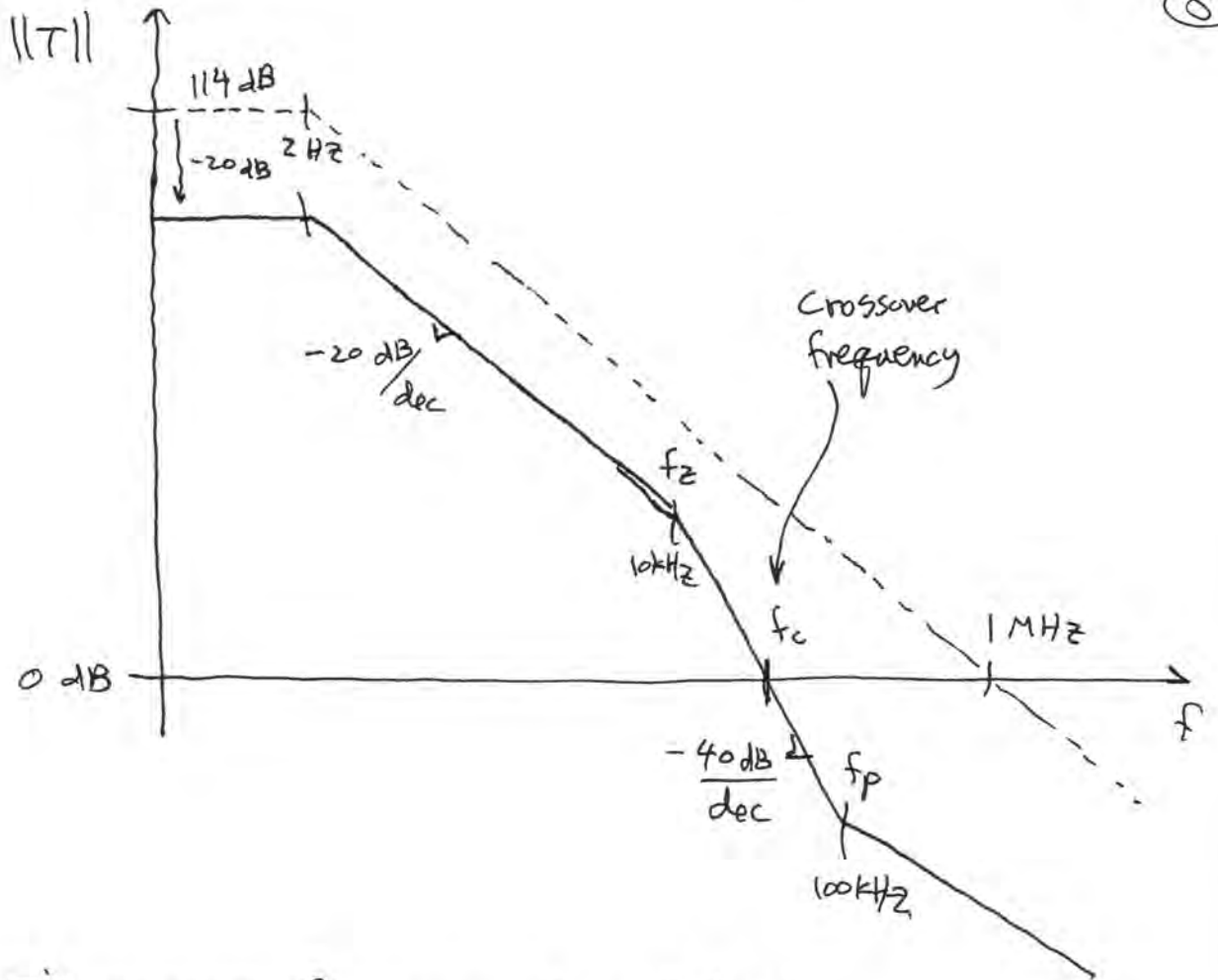So $T \approx \frac{z_1}{z_2} G_{op}$ is decreased relative to G_{op}



Find crossover frequency where $\|T\| = 1$

$$T = \frac{z_1}{z_1 + z_2} G_0 \approx \frac{z_1}{z_2} G_0 = \frac{R_1}{R_2} \frac{(1 + \frac{s}{\omega_p})}{(1 + \frac{s}{\omega_z})} \frac{G_0}{(1 + \frac{s}{\omega_{op}})}$$

for $f_2 < f < f_p$, $T \approx \frac{R_1}{R_2} \frac{(1 + \frac{s}{\omega_p})}{(1 + \frac{s}{\omega_z})} \frac{G_0}{(1 + \frac{s}{\omega_{op}})}$

so $\|T\| \approx \frac{R_1}{R_2} G_0 \frac{\omega_z \omega_{op}}{\omega^2}$

at $f = f_c$, $\|T\| = 1 = \frac{R_1}{R_2} G_0 \frac{f_z f_{op}}{f_c^2}$

$\Rightarrow f_c^2 = \frac{R_1}{R_2} G_0 f_z f_{op}$

$f_c = \sqrt{\frac{R_1}{R_2} G_0 f_z f_{op}} \approx 30 \text{ kHz}$

What is the phase margin?

$\angle T$ at $f = f_c$ is

-90° from the pole at $f_{op} = 2\text{kHz}$

from the pole at f_z and zero at f_p :

see textbook Fig. 9.16 or Eq. (9.34).

The result is $-\tan^{-1}\left(\frac{\sqrt{10} - \sqrt{0.1}}{2}\right) = -55^\circ$

So $\angle T = -90^\circ - 55^\circ = -145^\circ$ at f_c


phase margin = $180^\circ + \angle T = 35^\circ$

From textbook Fig. 9.13, this leads to closed-loop

$Q \approx 1.57 \Rightarrow 4\text{dB}$


construction of $\frac{T}{1+T}$

$$\frac{T}{1+T} \approx \begin{cases} 1, & \|T\| \gg 1 \\ T, & \|T\| \ll 1 \end{cases}$$

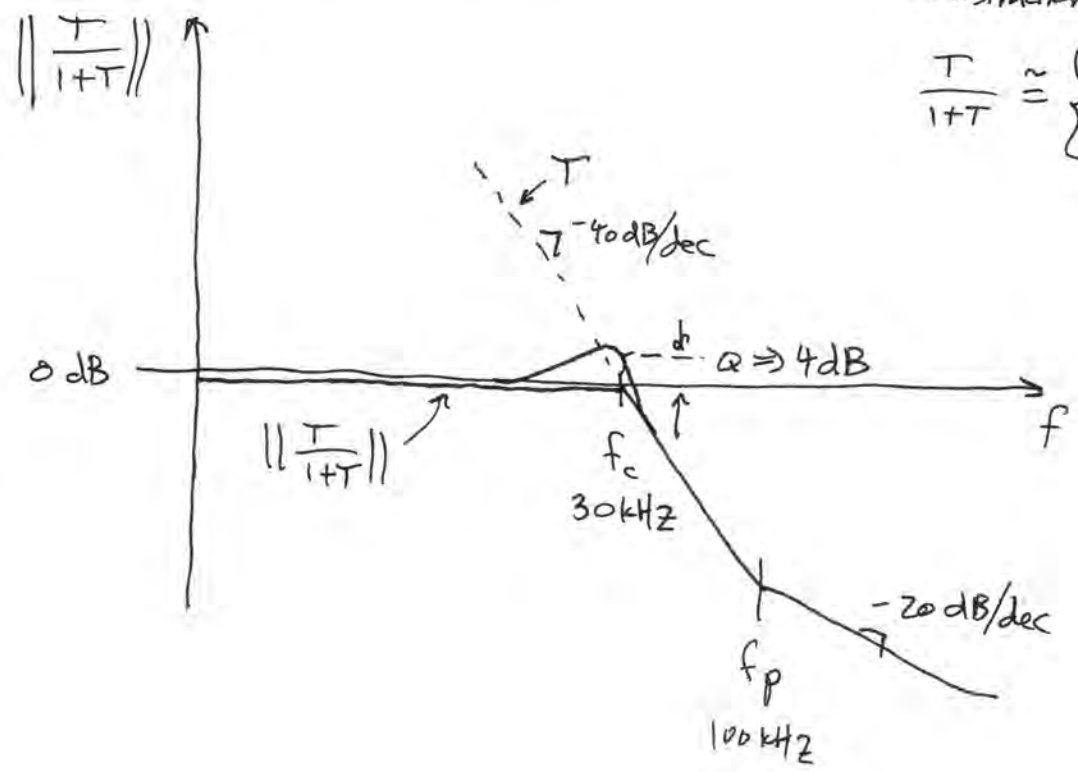

Actual transfer function

$$-\frac{z_2}{z_1} \frac{T}{1+T}$$

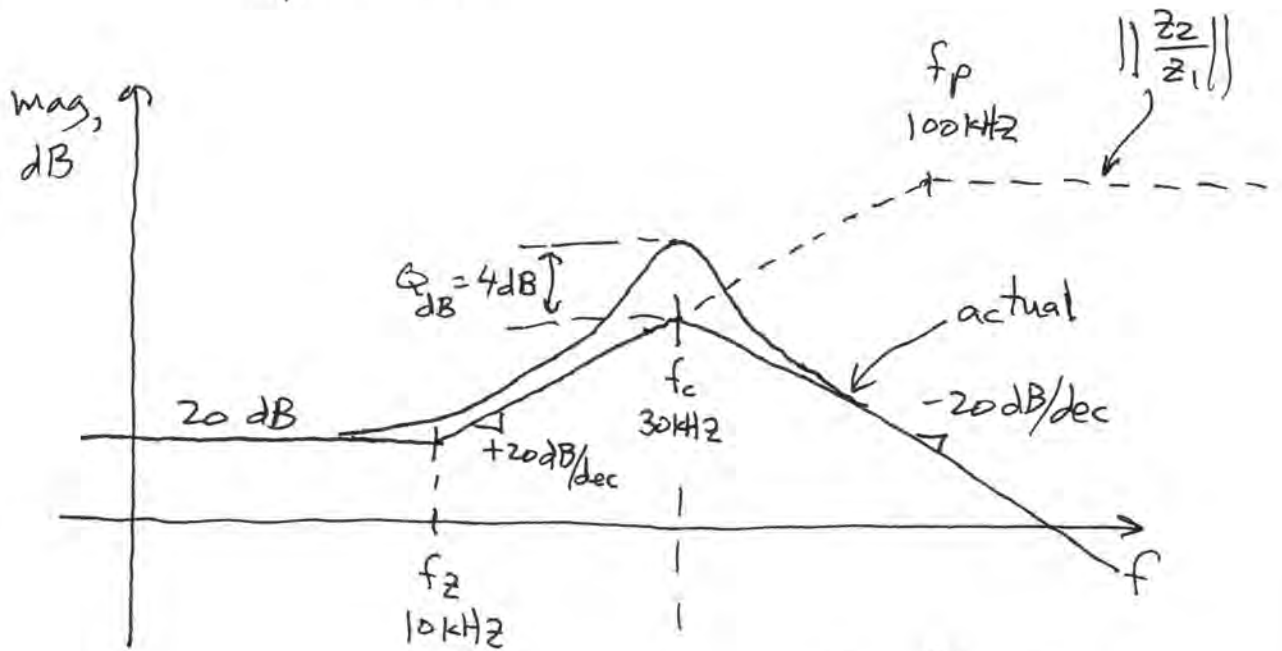

for $f < f_c$,

$$G \approx -\frac{z_2}{z_1}$$

for $f > f_c$,

$$\begin{aligned}
 G &\approx \left(-\frac{z_2}{z_1}\right) \left(\frac{T}{1+T}\right) \\
 &= \left(-\frac{z_2}{z_1}\right) (T) \\
 &= \left(-\frac{z_2}{z_1}\right) \left(\frac{z_1}{z_2} T\right) \\
 &= -G_{op}
 \end{aligned}$$

So the actual transfer function follows the ideal value $\left(-\frac{z_2}{z_1}\right)$ as long as $\|G_{op}\| \gg \left\|\frac{z_2}{z_1}\right\|$. But when $\|G_{op}\| < \left\|\frac{z_2}{z_1}\right\|$ then the actual transfer function follows $(-G_{op})$ instead.