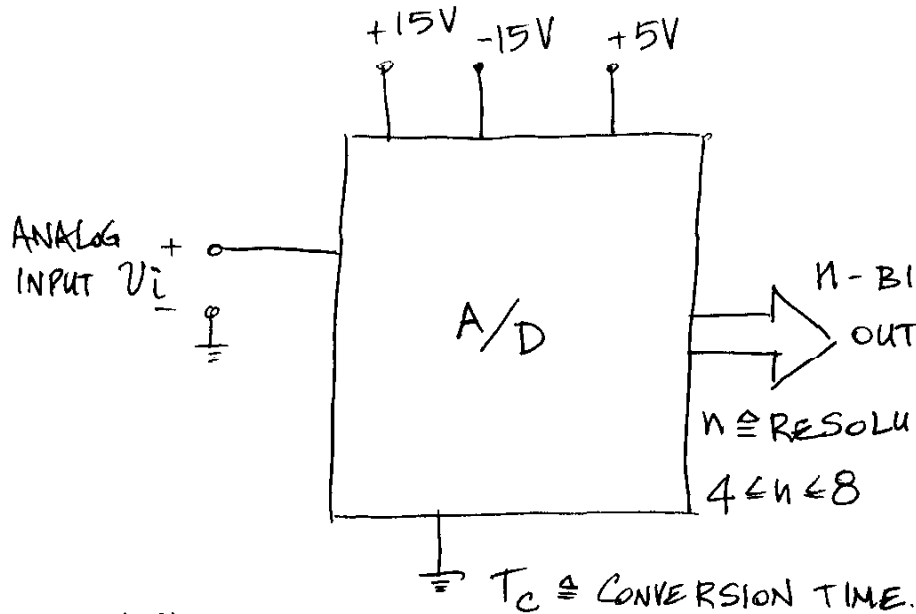


LAB 6: A/D CONVERTER DESIGN (OR CHOOSE ANOTHER TOPIC)




YOU MAY USE ANY COMPONENTS FROM PREVIOUS LABS (INCLUDING DAC0808), AS WELL AS ANY DIGITAL GATES, COUNTERS, LATCHES, ETC. WHAT IS NOT ALLOWED IS AN A/D CHIP!

$$0 \leq V_i \leq 10V$$

$V_{ref} \equiv$ FULL SCALE VOLTAGE


EXAMPLE OF OPERATION FOR $n = 2$

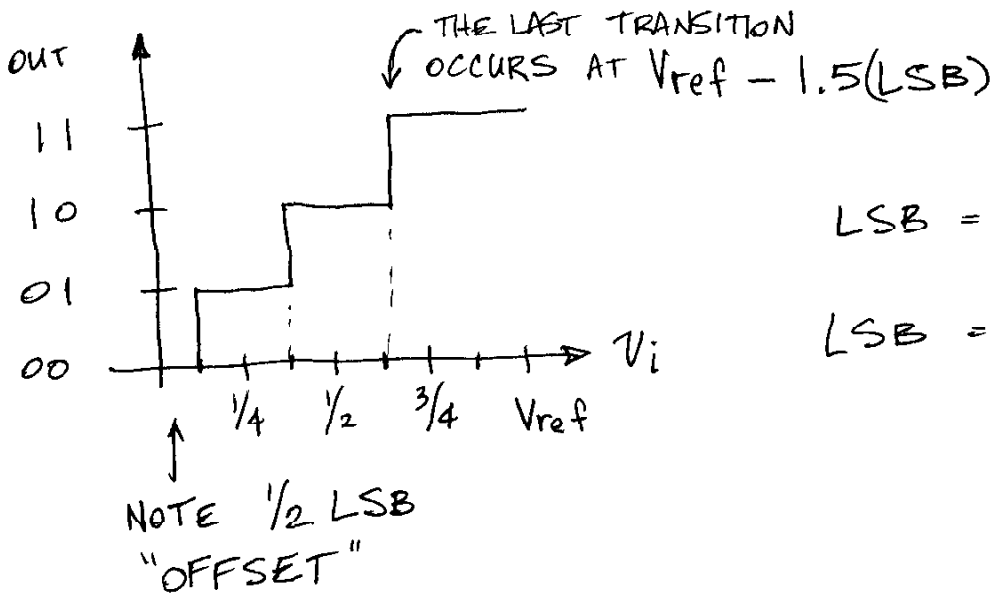

LSB = ANALOG VOLTAGE EQUIVALENT OF 1 BIT

$$LSB = \frac{V_{ref}}{2^n}$$

TESTING OF YOUR A/D CONVERTER

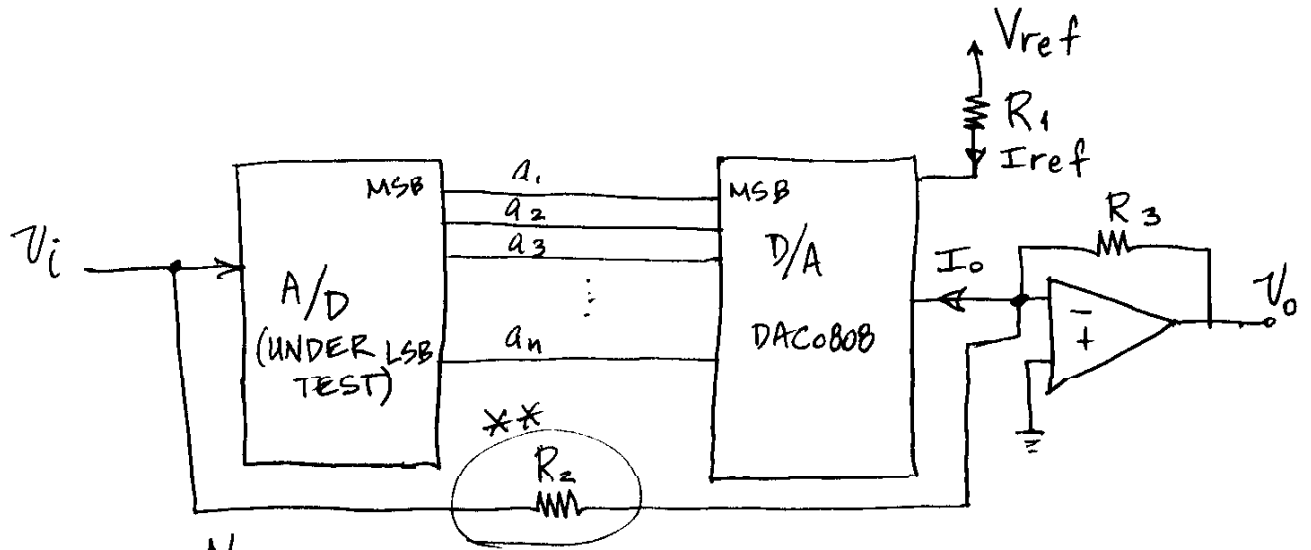

$I_o = \frac{N}{2^n} \cdot I_{ref}$ WHERE N IS THE DECIMAL EQUIVALENT OF THE DIGITAL WORD OUTPUT


$$N = \sum_{k=1}^n a_k 2^{n-k}$$

$$V_o = R_3 I_o = R_3 \frac{N}{2^n} I_{ref} = \frac{R_3}{R_1} (V_{ref}) \frac{N}{2^n}$$

IF YOU CHOOSE $R_3 = R_1$, $V_o = V_{ref} \frac{N}{2^n}$

DEFINE:
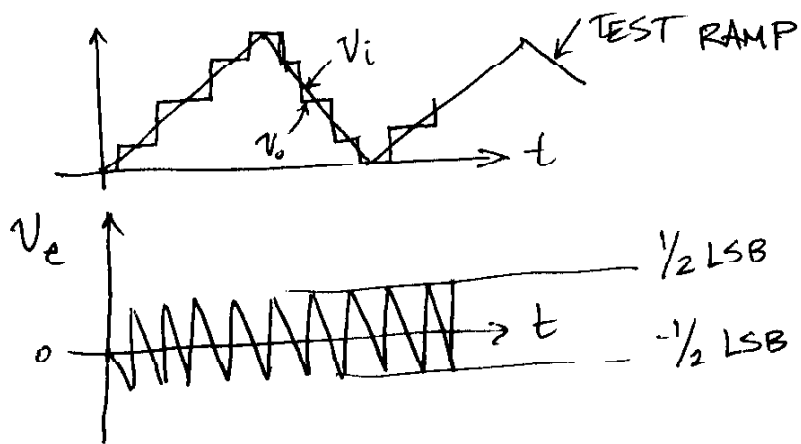
$$V_e = V_i - V_o \triangleq \text{ERROR OF A/D}$$



** BY ADDING R_2 , V_o BECOMES V_e (ERROR)

MAKE SURE THAT $R_1 = R_2$

$$V_o = V_e = R_3 I_o - \frac{R_3}{R_2} V_i$$

$$V_o - V_e = R_3 \left(\frac{N}{2^n} \frac{V_{ref}}{R_1} - \frac{1}{R_2} V_i \right)$$

$$V_e = \frac{R_3}{R_1} \left(\frac{N}{2^n} V_{ref} - V_i \right)$$