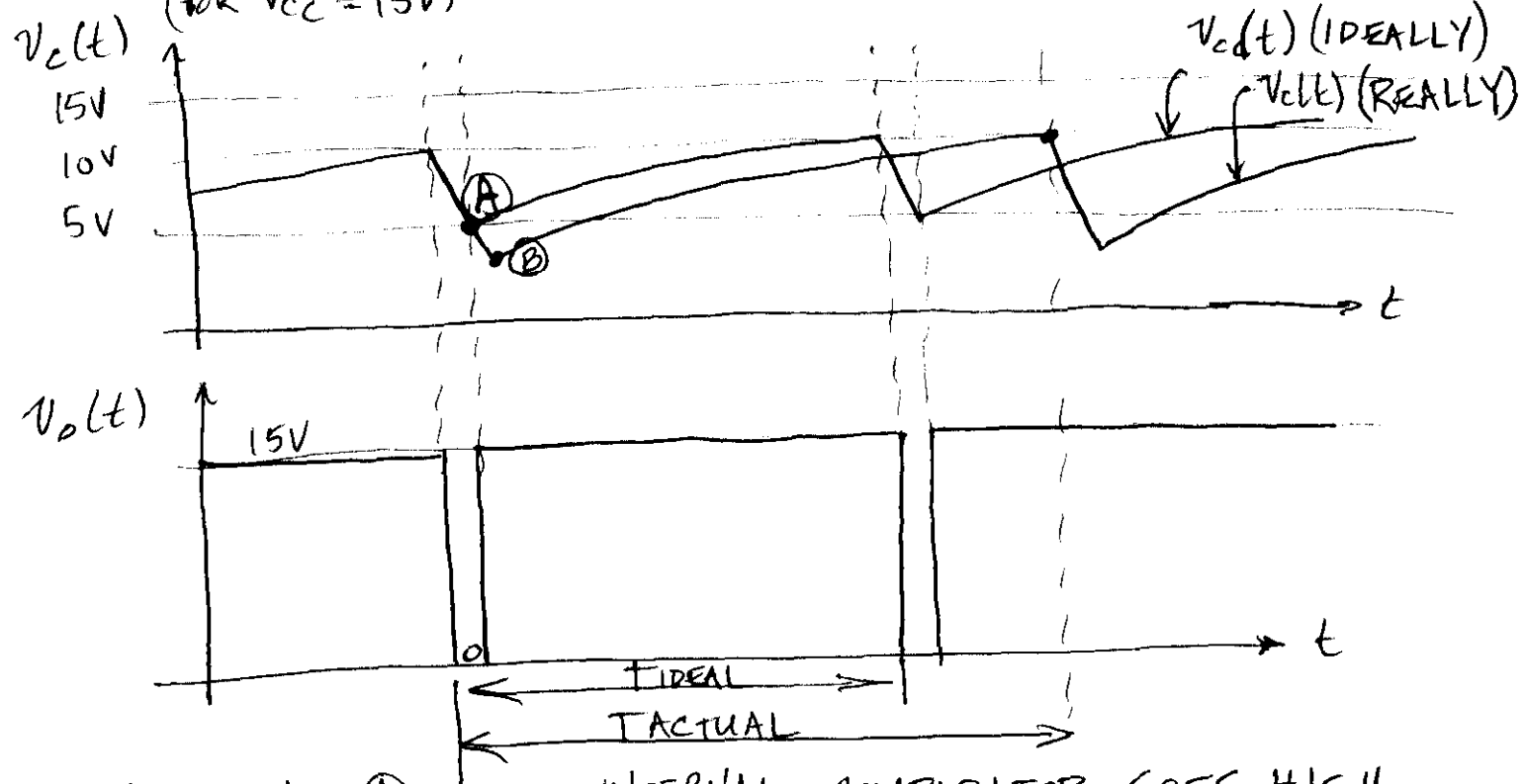


9/11/98

LAB 1, PART 3.2, QUESTION ABOUT WHY  $f_p$  IS TOO LOW...

(FOR  $V_{CC} = 15V$ )




AT POINT (A), THE INTERNAL COMPARATOR GOES HIGH, THE INTERNAL FLIP-FLOP IS SET,  $\bar{Q}$  GOES LOW,  $Q_{14}$  (BJT INSIDE 555) IS TURNED OFF, AND THEN THE CAPACITOR IS CHARGING UP THRU  $R_A$  AND  $R_B$ . THE PROPAGATION DELAY ASSOCIATED WITH THESE STEPS CAUSES THE CAPACITOR VOLTAGE TO CONTINUE TO FALL UNTIL POINT (B), WHEN THE BJT  $Q_{14}$  ACTUALLY TURNS OFF. THE SUBSEQUENT CAPACITOR CHARGE WAVEFORM STARTS FROM AN INITIAL CONDITION LESS THAN THE IDEAL INITIAL CONDITION OF (A), RESULTING IN A LONGER RISE TIME AND LOWER FREQUENCY  $f_p$ .

PAGE 1

9/11/98

# RAMP WAVEFORM GENERATOR

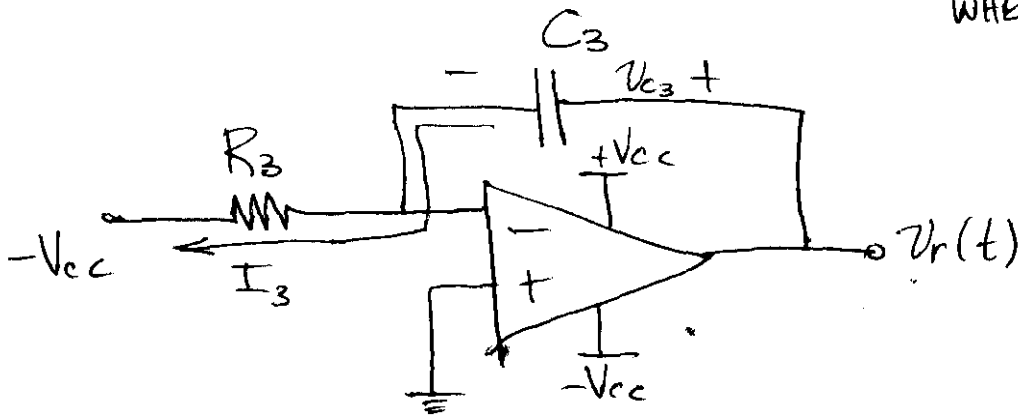WHEN MOSFET IS OFF

$$V_{c3}(0) \approx 0 \quad (\text{INITIAL CONDITION})$$

$$V_r(t) = V_- + V_{c3}(t)$$

$$V_r(t) = V_{c3}(t)$$

$$I_3 = \frac{V_{cc}}{R_3} = \text{CONSTANT}$$

$$C_3 \frac{dV_{c3}(t)}{dt} = I_3$$

$$\frac{dV_{c3}(t)}{dt} = \frac{V_{cc}}{R_3 C_3}$$


$$V_{c3}(t) = \frac{V_{cc}}{R_3 C_3} t = V_r(t)$$

(EQUATION FOR RAMP FUNCTION)

(PAGE 2)

9/11/98

(SAWTOOTH) RAMP WAVEFORM GENERATOR

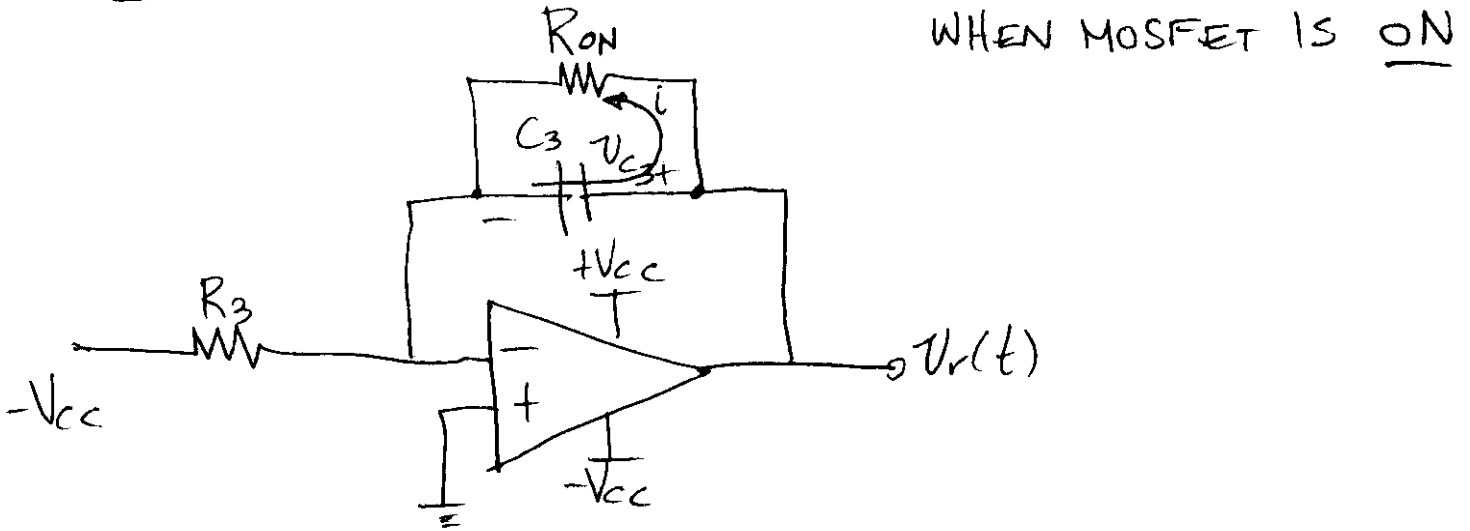

THERE IS A SMALL "ON-RESISTANCE" ASSOCIATED WITH ANY REAL MOSFET. THE CAPACITOR  $C_3$  DISCHARGES THROUGH  $R_{ON}$ .

$R_{ON} \approx$  SEVERAL OHMS

$$\tau = R_{ON} C_3$$

$$V_{C3}(t) = V_r(t)_{[MAX]} e^{-t/\tau}, \quad V_{C3}(0) = V_r(t)_{[MAX]} (\approx 4V)$$

MAKE  $V_{C3}(t_1) = 0$

FOR  $t_1$  AS SMALL AS POSSIBLE

