
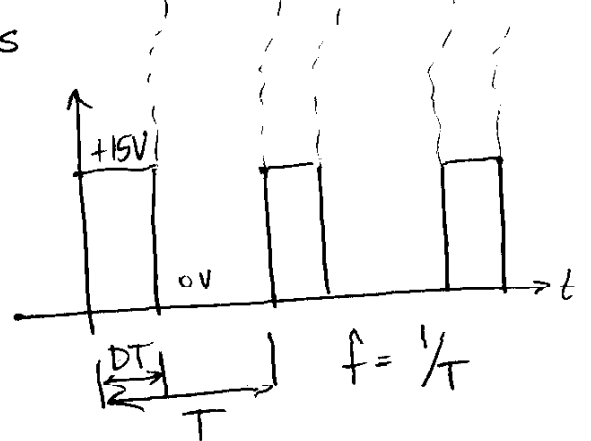
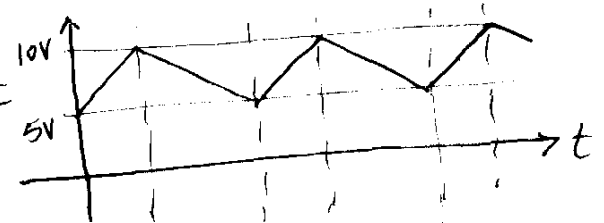


VOLTAGE CONTROLLED WAVEFORM GENERATOR

SPECS:

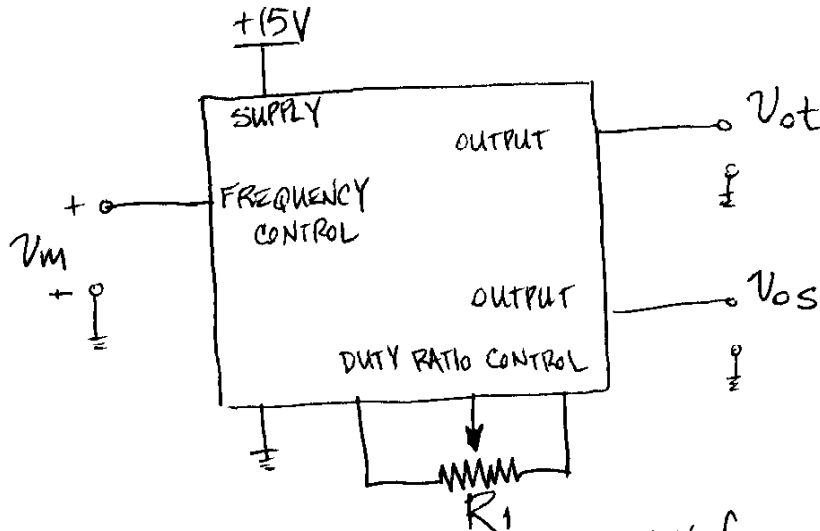

INPUT VOLTAGE  $V_m$  CONTROLS FREQUENCY  $f$

$$f = K_o V_m$$


$K_o \triangleq$  GAIN OF THE VOLTAGE-CONTROLLED OSCILLATOR

$$K_o = 5 \text{ KHz/V}$$


$R_1 \Rightarrow$  ADJUSTS DUTY RATIO  $D$  OF THE OUTPUT  $V_{os}$

CONSTRAINTS: ONLY ONE SUPPLY OF +15V  
 CONTROL OF DUTY RATIO SHOULD BE  
INDEPENDENT OF  $V_m$ , AND CONTROL OF  
 FREQUENCY SHOULD BE INDEPENDENT  
 OF  $R_1$ .

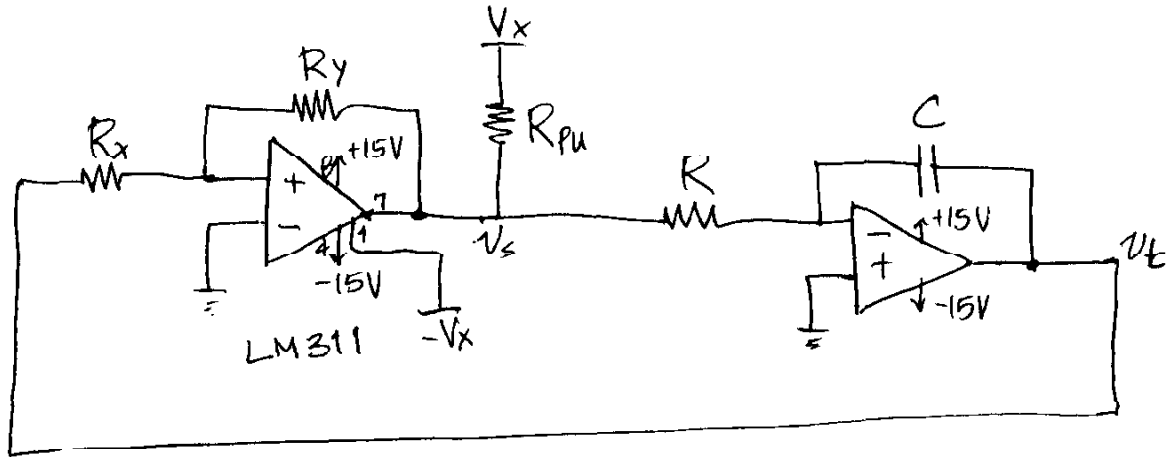HERE'S A DESIGN WITH ALL SUPPLIES AVAILABLE.



INSIDE A LM311:


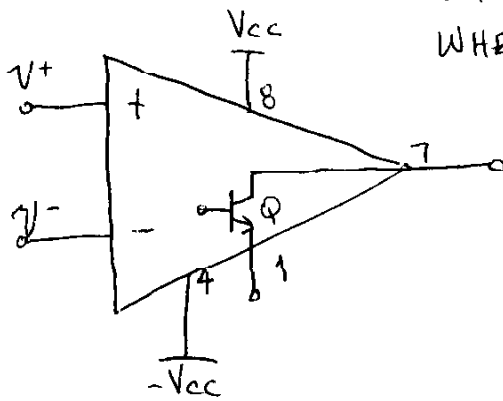


WHEN  $V^+ > V^-$ , Q IS CUTOFF  
 WHEN  $V^+ < V^-$ , Q IS ON,  $V_{t1} \approx 0V$ .

WITHOUT A PULL-UP RESISTOR ( $R_{pu}$ ), THE OUTPUT (PIN 7) VOLTAGE IS FLOATING. MAKE SURE TO USE A PULL-UP RESISTOR


HOW TO ANALYZE BEHAVIOR? REFERRING TO TOP DIAGRAM,

SUPPOSE  $V_s = +V_x$ ,  $t = 0$

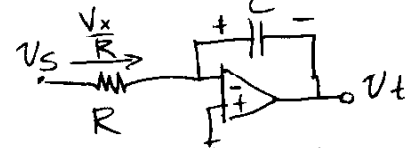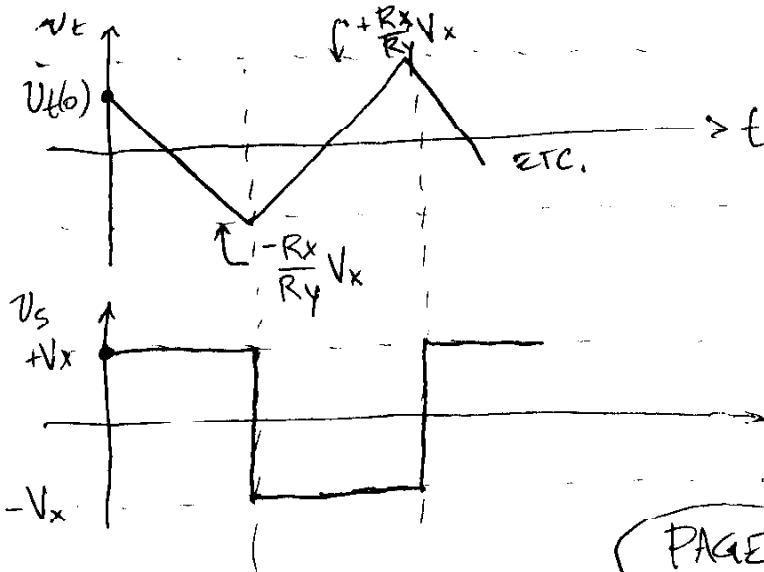

$$U_t(t) = -\frac{V_x}{RC} t + U_t(0)$$

OVER  $\Rightarrow$

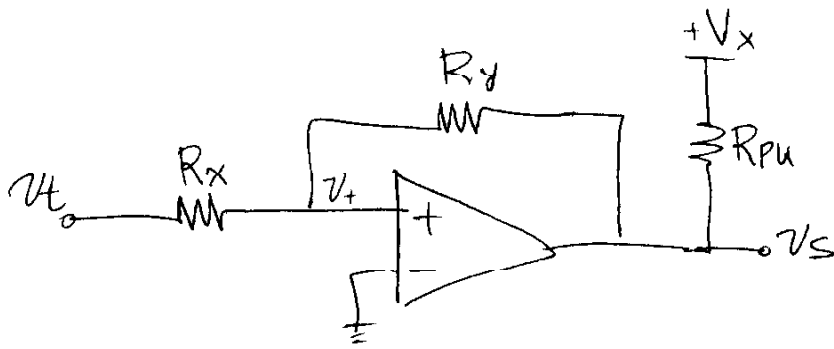

$$v_+ = \frac{R_y}{R_y + R_x} v_t + \frac{R_x}{R_x + R_y} v_s \quad (\text{BY SUPERPOSITION})$$

WE WANT TO KNOW WHEN  $v_+ > 0$  TO VERIFY ASSUMPTION THAT  $v_s = +V_x$

$$\frac{R_y}{R_x + R_y} v_t + \frac{R_x}{R_x + R_y} (+V_x) > 0 \Rightarrow v_t > \frac{-R_x}{R_y} V_x$$

WHEN THIS CONDITION IS VIOLATED, THE COMPARATOR OUTPUT  $v_s$  GOES TO  $-V_x$ .

THE EQUATIONS ARE SIMILAR FOR WHEN  $v_s = -V_x$ .