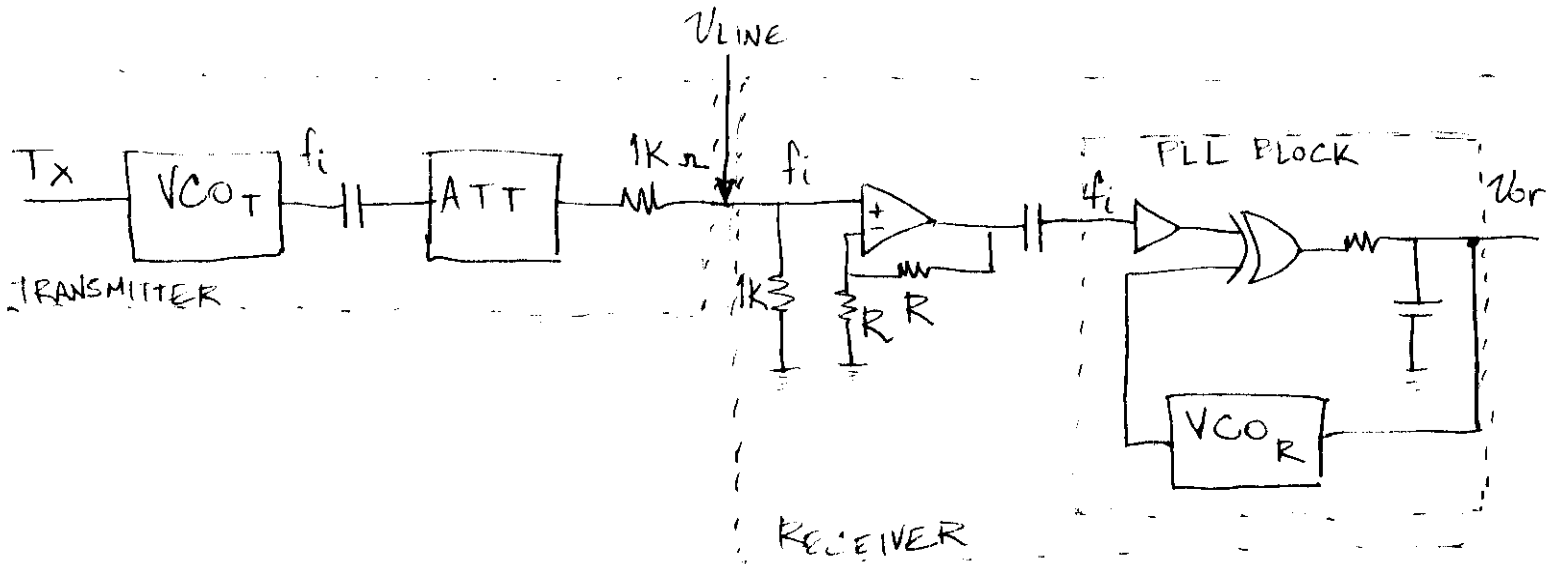



FSK MODEM MODEL

CIRCUIT BLOCK DIAGRAM

3/12/99



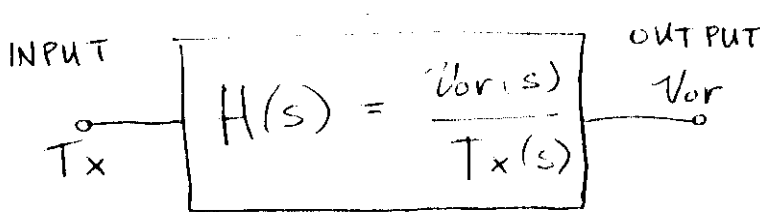
WE WANT THE TRANSFER FUNCTION OF THE MODEM:



→ THE SYSTEM $H(s)$ IS LINEAR IF THE PLL IS ALWAYS LOCKED

MODEL

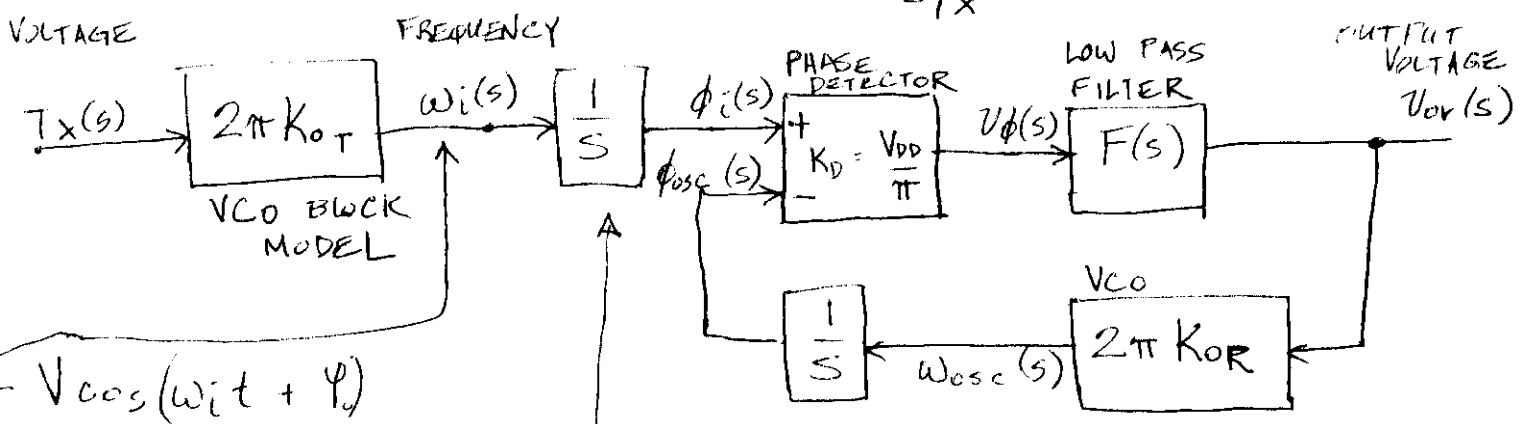$\omega_i = 2\pi f_i$, $K_{oT} \cong \frac{\Delta f_i}{\Delta T_x}$



$V \cos(\omega_i t + \phi_i)$

$\phi_i = \omega_i t + \phi_0 \Rightarrow \omega_i = \frac{d\phi_i}{dt}$
 $\phi_i(s) = \left(\frac{1}{s}\right) \omega_i(s)$

$V_\phi(s) = K_D (\phi_i - \phi_{osc})$

NOW, SOLVE THE MODEL

$$\phi_i(s) = \left(\frac{2\pi K_{OT}}{s} \right) T_x(s)$$

$$V_{or}(s) = F(s) V_{\phi}(s)$$

$$V_{\phi}(s) = K_D (\phi_i(s) - \phi_{osc}(s))$$

$$V_{\phi}(s) = K_D \left(\phi_i(s) - \left(\frac{2\pi K_{OR}}{s} \right) V_{or}(s) \right)$$



$$\Rightarrow V_{or}(s) = F(s) K_D \left[\left(\frac{2\pi K_{OT}}{s} \right) T_x(s) - \left(\frac{2\pi K_{OR}}{s} \right) V_{or}(s) \right]$$

$$H(s) = \frac{V_{or}(s)}{T_x(s)} = \frac{K_{OT}}{K_{OR}} \left(\frac{1}{1 + \frac{s}{2\pi K_{OR} K_D} + \frac{s^2}{\omega_p 2\pi K_{OR} K_D}} \right)$$

FOR $F(s) = \frac{1}{1 + \frac{s}{\omega_p}}$


\therefore THE FSK MODEM IS A 2nd ORDER DYNAMIC SYSTEM

LET'S LOOK AT THE STEP RESPONSE:

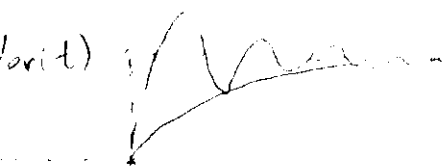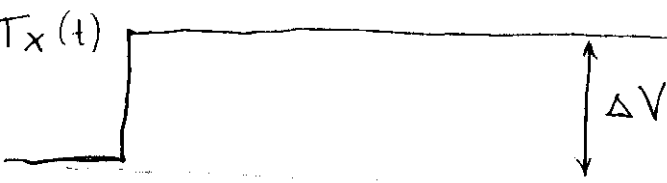

THE SYSTEM RESPONSE DEPENDS ON THE Q FACTOR OF THE SYSTEM

$\Delta V \left(\frac{K_{OT}}{K_{OR}} \right)$ SINCE $H(s) \Big|_{s \rightarrow 0} = \frac{K_{OT}}{K_{OR}}$

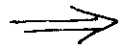


THE TRANSFER FUNCTION CAN BE WRITTEN AS

$$\Rightarrow H(s) = \frac{K_{OT}}{K_{OR}} \left(\frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2} \right)$$

WHERE $\omega_0 = \sqrt{\omega_p 2\pi K_D K_{OR}}$


$$Q = \sqrt{\frac{K_{OR} K_D}{f_p}}$$

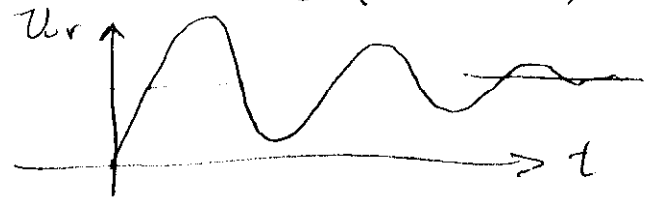A LARGE Q RESULTS
IN AN UNDERDAMPED
RESPONSE (NOT GOOD)



$Q < \frac{1}{2}$ RESULTS IN
NO OVERSHOOT OR RINGING

$Q \approx 1$ IS ACCEPTABLE

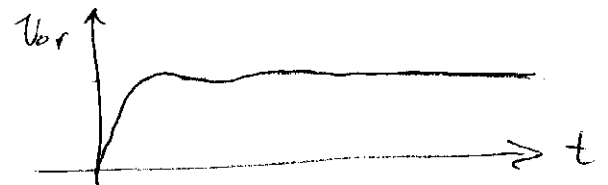

Now,

IF f_p GOES DOWN,

AC RIPPLE GOES DOWN (GOOD)

CAPTURE RANGE GOES DOWN (BAD)

Q GOES UP (BAD)

TRY TO USE THIS RESULT IN YOUR DESIGN!