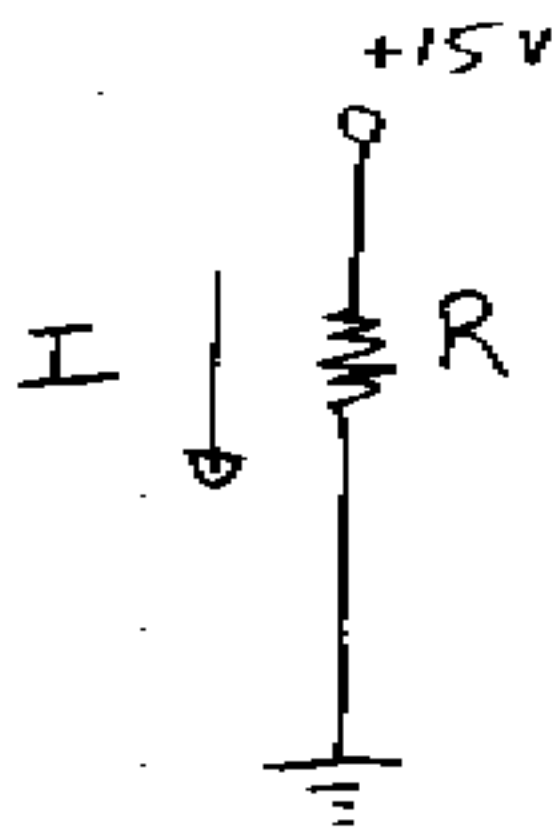


Hand out #1 LAB 3.

①



R has max Power of .25W

$$15 = IR$$


$$P = \frac{V^2}{R} = I^2 R$$

$$.25 = \frac{(15)^2}{R}$$

$$R = 900\Omega$$


⇒ Choose $R > 900\Omega$ when connected +15V to ground.

②

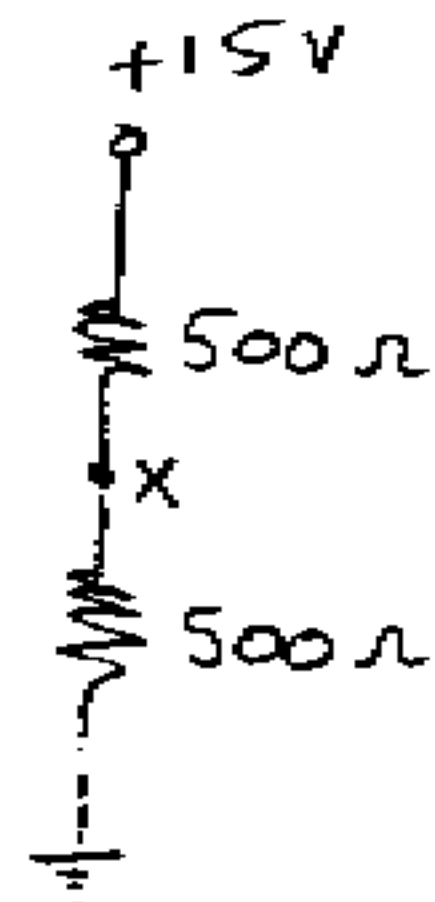

$$V_x = 7.5V$$


③

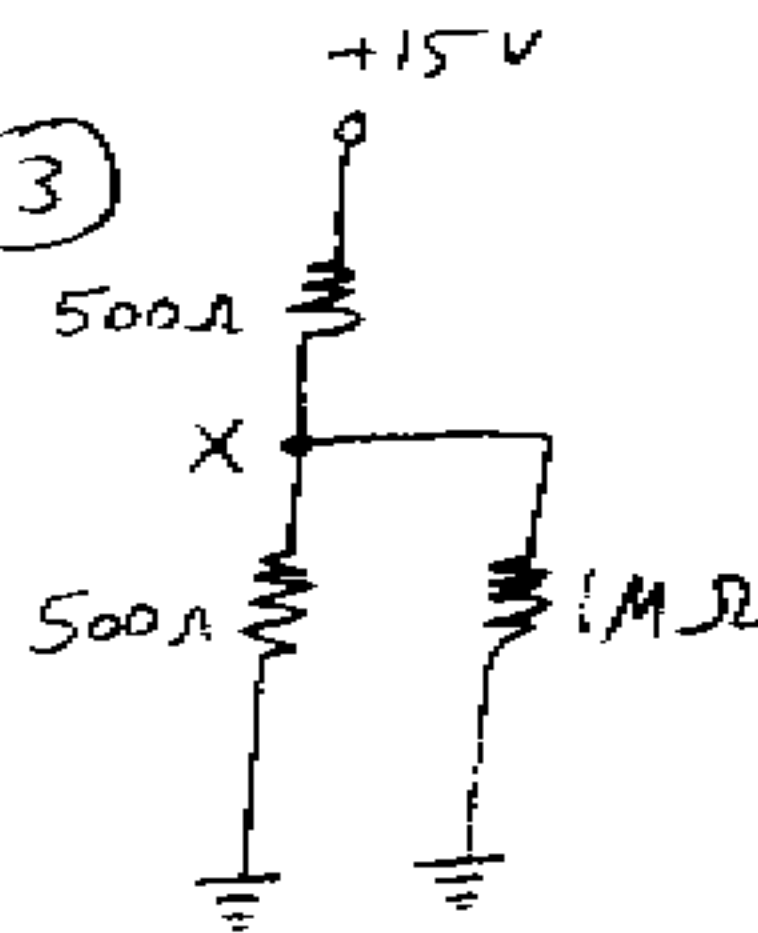

$$V_x = 7.498V$$

OK


④

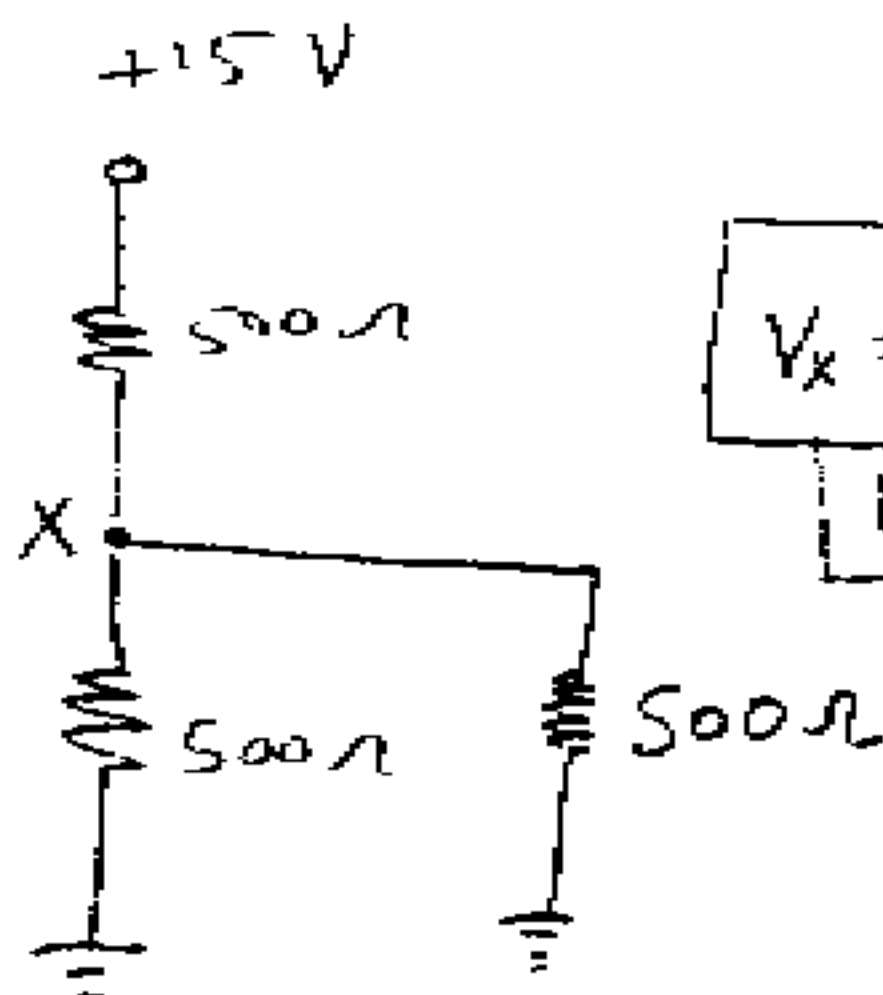

$$V_x = 5V$$


bad

⑤

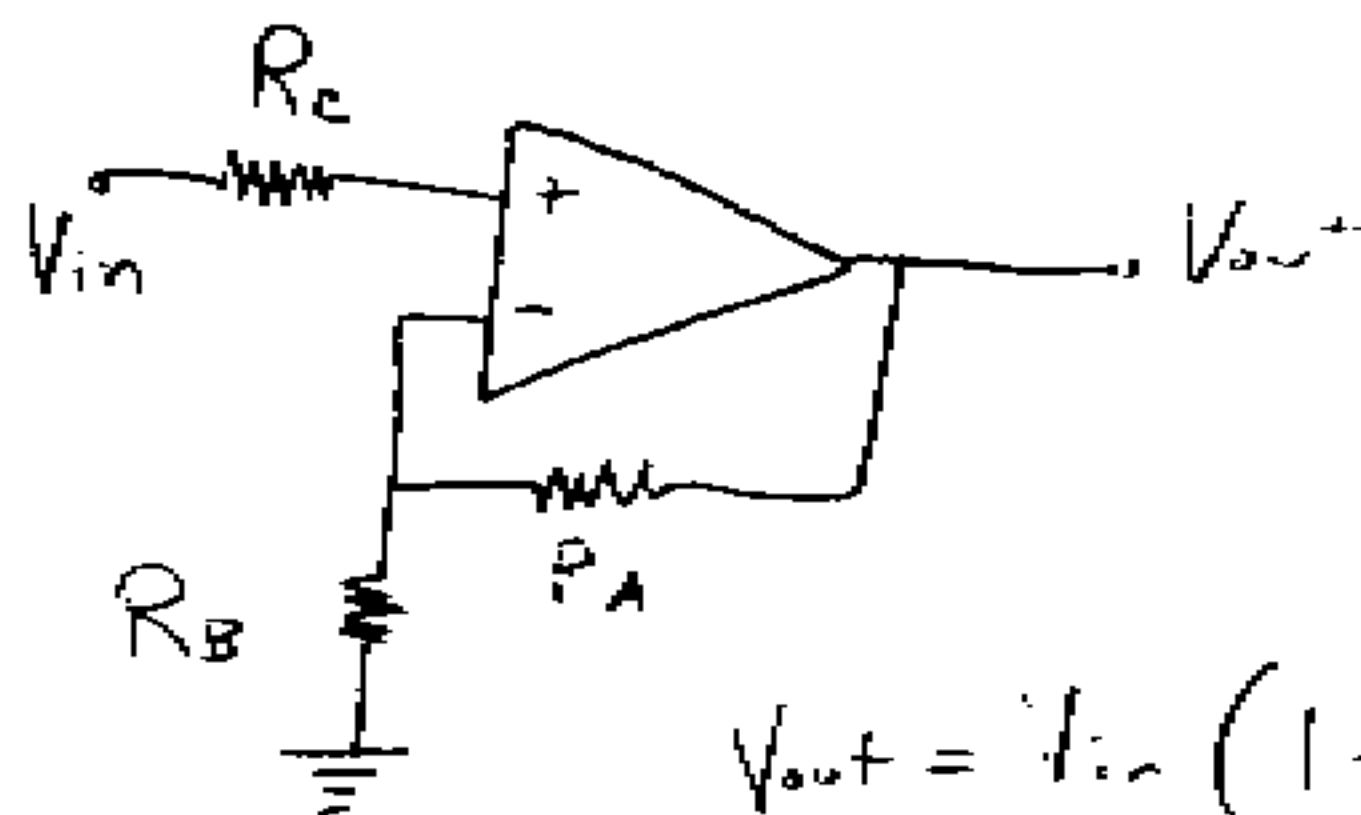

$$V_{out} = V_{in} \left(1 + \frac{R_A}{R_B} \right)$$

⑤

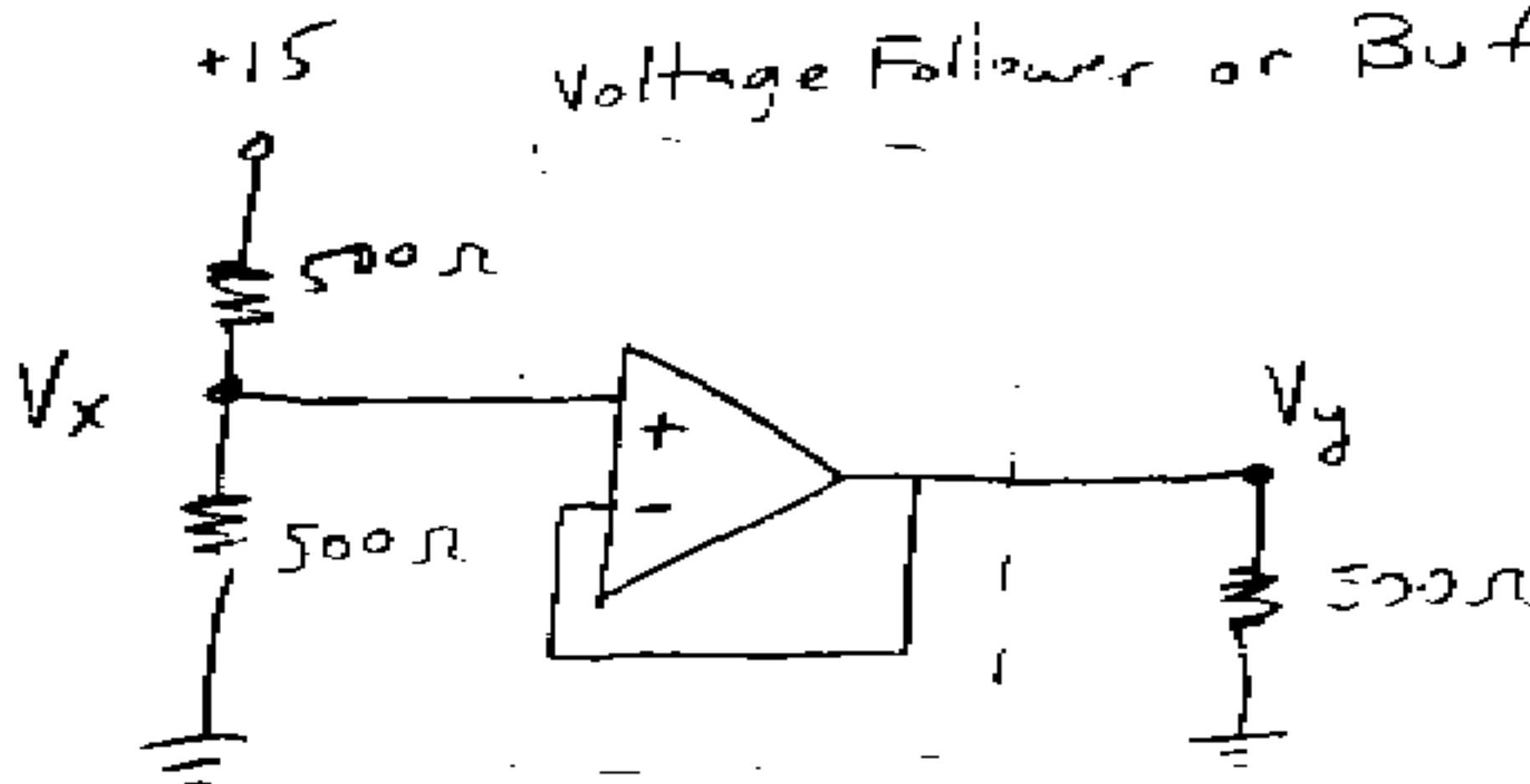

Voltage Follower or Buffer. ($R_A = 0, R_B \rightarrow \infty$)

$$V_x = V_y = 7.5V$$

OK.

VII. Finding V_L , V_H .

$$V_L: V_g(t) = V_t(t) \left[\frac{R_f}{R_f - R_{f2}} \right] + V_s(t) \left[\frac{R_{f2}}{R_f + R_{f2}} \right]$$

V_L is the value of $V_t(t)$ when $V_g(t) = 0$. $V_s(t) = 15$

$$\Rightarrow V_t(t) \overset{V_L}{R_f} = -V_s(t) R_{f2}$$

$$\Rightarrow \boxed{V_L = \frac{-15 R_{f2}}{R_f}}$$

see pt ② from lecture

$$V_H: V_g(t) = V_t(t) \left(\frac{R_f}{R_f + R_{f2}} \right) + V_s(t) \left[\frac{R_{f2}}{R_f - R_{f2}} \right]$$

V_H is the value of $V_t(t)$ when $V_g(t) = 0$ $V_s(t) = -15$

$$V_t(t) \overset{V_H}{R_f} = -V_s(t) R_{f2}$$

$$\boxed{V_H = \frac{15 R_{f2}}{R_f}}$$

see pt ④ from lecture

This page corresponds with LAB3 Figure 2.