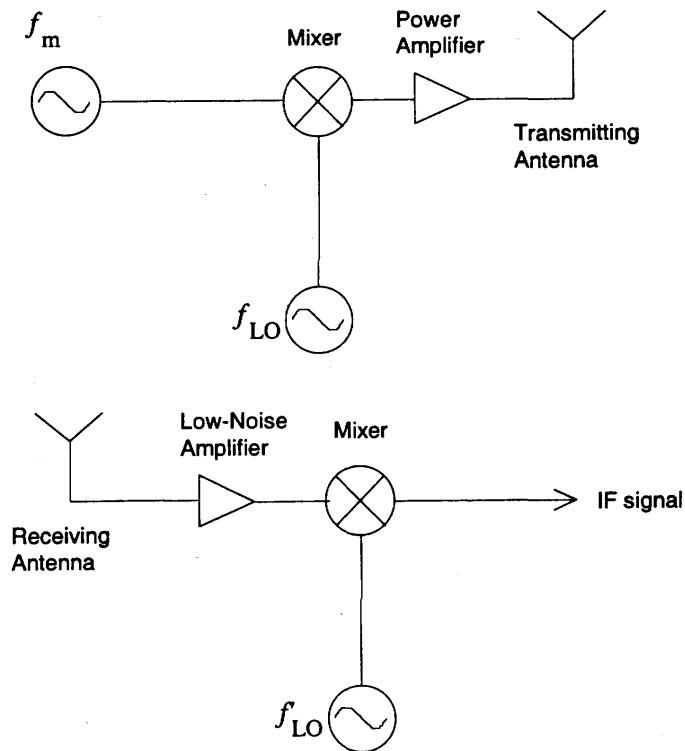


## Final Exam (Written Section)

Open Notes.  
Show (i. e., *explain*) all work.

- (20) 1. Consider the microwave link shown in the figure. The transmitting and receiving antennas are separated by a distance of 100 m.



The modulating frequency sent to the transmitter's mixer is  $f_m = 10$  kHz, the local oscillator frequency of the transmitter is  $f_{LO} = 10$  GHz, and the local oscillator frequency of the receiver is  $f'_{LO} = 10.020$  GHz. The output from the transmitter's mixer is 6 dBm, and the gain of the power amplifier is 15 dB. The transmitting antenna's gain is 12 dB, the receiving antenna's effective area is  $0.005$  m<sup>2</sup>, the low-noise amplifier's gain is 9 dB, and the receiver mixer's conversion loss is 5 dB. All components are impedance-matched to their respective transmission lines and sources.

- What frequency components appear in the IF signal at the right end of the receiver?
- How many watts of power appear at the output of the receiver in the IF signal? What is this value in dBm?

(20) 2. A Schottky diode is connected in shunt across a lossless transmission line of characteristic impedance  $Z_0 = 50 \Omega$  at  $z = 0$ . An RF voltage wave of RMS amplitude  $V_+ = 1$  volt is incident from  $z < 0$  towards the diode. The DC bias current on the diode is zero. The diode's parameters (in accordance with eqns. (3.6) ff. of the course notes) are:  $I_S = 25 \mu\text{A}$ ,  $\alpha = 50 \text{ V}^{-1}$ .

(a) Assume that modeling the diode as a linear RF conductance  $G_d$  is sufficiently accurate for determining the small-signal RF voltage and current. Find the reflection coefficient  $\rho$  and transmission coefficient  $\tau$  on the transmission line due to this diode.

(b) Determine the DC component of the diode current  $I_{DC}$  which results from the incident voltage wave.

(20) 3. A Gunn diode is modeled by the nonlinear conductance

$$G_D = G_d + \frac{G_d''}{8} V_1^2$$

where  $V_1$  is the RF voltage,  $G_d = -2 \text{ mS}$  and  $G_d'' = 3 \text{ mS/V}^2$ . The Gunn diode is connected to a resonant load whose admittance is

$$Y_L = \frac{1}{R_L} + j\omega C + \frac{1}{j\omega L}$$

where  $C = 10 \text{ pF}$ ,  $R_L = 2 \text{ k}\Omega$ , and  $L = 30 \mu\text{H}$ . Find the frequency  $f$  at which this circuit oscillates, and the RF voltage  $V_1$  of the oscillation.

1) (a) Inputs to transmit mixer are:

$f_m, f_{LO} \Rightarrow$  its output is  $f_m, f_{LO}, f_{LO} \pm f_m, 2f_m, 2f_{LO}$ , and others at higher order.

Only  $f_{LO}, f_{LO} \pm f_m, 2f_{LO}$  survive to receive antenna, these input to 2nd mixer to give, with  $f'_{LO}$ ,

$f'_{LO} \pm f_{LO}, f'_{LO} \pm f_{LO} \pm f_m, 2f_{LO} \pm f'_{LO}, 2f'_{LO}, 2f_{LO}, 2(f_{LO} \pm f_m), 4f_{LO}$

$$\lambda = \frac{c}{f} = \frac{3 \times 10^8}{10^{10}} = .03 \text{ m}$$

(b)  $P_{tr} = 6 \text{ dBm} \Rightarrow 4 \text{ mW}$

$$P_r = P_{tr} G_{tr} G_r \left(\frac{\lambda}{4\pi r}\right)^2 \quad (\text{absolute})$$

$$\text{or} \quad = P_{tr, \text{dBm}} + G_{tr, \text{dB}} + G_{r, \text{dB}} + 20 \log_{10} \left(\frac{\lambda}{4\pi r}\right) \quad (\text{dB})$$

Also

$$P_r = P_{tr} G_{tr} A_r \frac{1}{4\pi r^2}$$

$$\text{or} \quad = P_{tr, \text{dBm}} + G_{tr, \text{dB}} + 10 \log_{10} \left(\frac{A_r}{4\pi r^2}\right)$$

$$\text{so} \quad P_r = 6 \text{ dBm} + 12 \text{ dB} + \underbrace{10 \log_{10} \left(\frac{.005}{4\pi (100)^2}\right)}_{\approx -74 \text{ dB}} + 15 \text{ dB}$$

$$= -41 \text{ dBm}$$

Amp output is  $-32 \text{ dBm}$ . Conversion loss at mixer gives IF of  $-37 \text{ dBm}$  or  $0.2 \mu\text{W}$ .

2) (a)



$$\rho = \frac{47.059 - 50}{50 + 47.059} = -0.03$$

$$\gamma = 1 + \rho = 0.97$$

$$V_d = V_1 \gamma = 0.97 \text{ V (RMS)}$$

$$\Rightarrow v = \frac{0.97}{\sqrt{2}} \cos \omega t \Rightarrow v_{\text{av}}^2 = (0.97)^2$$

$$I_{\text{DC}} = \frac{v_{\text{av}}^2}{2} G_d' = \frac{(0.97)^2}{2} \alpha G_d = 29.38 \text{ mA}$$

$$G_d = \alpha I_s = 0.00125 \text{ S}$$

$$\text{or} \quad R_j = 800 \Omega$$

$$R_j \parallel Z_0 = \frac{50(800)}{850} = 47.059 \Omega$$

$$3) f: \frac{1}{j\omega L} + j\omega C = 0 \Rightarrow \omega = \frac{1}{\sqrt{LC}} \Rightarrow f = \frac{1}{2\pi\sqrt{LC}} \\ = \underline{\underline{9.189 \text{ MHz}}}$$

$$G_D + \frac{1}{R_L} = 0 \Rightarrow G_d + \frac{G_d''}{8} V_1^2 + \frac{1}{R_L} = 0$$


$$V_1^2 = -\left(G_d + \frac{1}{R_L}\right) \frac{8}{G_d''} = 4 \Rightarrow \underline{\underline{V_1 = 2V}}$$

## Final Exam

Open Notes.

Show (i. e., *explain*) all work.

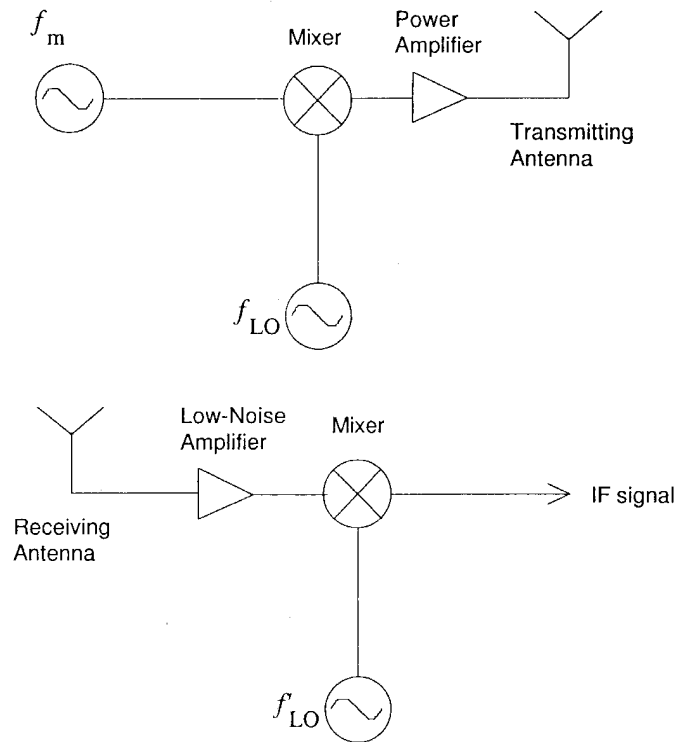1. Consider the microwave link shown in the figure. The transmitting and receiving antennas are separated by a distance  $r$ .



The modulation sent to the transmitter's mixer is a 100 kHz sine wave. The local oscillator frequency of the transmitter is  $f_{LO} = 2$  GHz, and the local oscillator frequency of the receiver is  $f'_{LO} = 2.050$  GHz. Each mixer has a conversion loss of 3.5 dB, the gain of the power amplifier is 12 dB and the low-noise amplifier's gain is 9 dB. The transmitting antenna's gain is 18 dB and the receiving antenna's gain is 6 dB. All components are impedance-matched to their respective transmission lines and sources, except for the antennas, each of which has a reflection coefficient of  $|\rho| = 0.5$  when connected to the transmission lines.

- What frequency components appear in the IF signal at the right end of the receiver? Assume the mixers are square-law ( $I$  is a quadratic function of  $V$ ) diodes.
- The modulation signal has a power of 1 mW. If the IF output signal from the receive end has a power of -40 dBm, what is the distance  $r$  between the transmitting and receiving antennas?

2. A Schottky diode's parameters (in accordance with eqns. (4.6)-(4.9) of the course notes) are:  $I_S = 60 \mu\text{A}$ ,  $\alpha = 100 \text{ V}^{-1}$ . The diode is connected in series with a  $100 \Omega$  resistor at the end ( $z = 0$ ) of a lossless transmission line whose characteristic impedance is  $Z_0 = 50 \Omega$ . An RF voltage wave of RMS amplitude  $V_+$  is incident from  $z < 0$  towards the diode. The DC bias current on the diode is zero.
- Assume that modelling the diode as a linear RF conductance  $G_d$  is sufficiently accurate for determining the small-signal RF voltage and current. Find the reflection coefficient  $\rho$  on the transmission line due to this diode.
  - A DC component of the diode current  $I_{\text{DC}} = 25 \mu\text{A}$  is measured through the diode. Find the rms amplitude of the incident voltage wave.
3. A Gunn diode is modelled by the nonlinear conductance

$$G_D = G_d + \frac{G_d''}{8} V_1^2$$

where  $V_1$  is the RF voltage. If the DC bias voltage is 7 volts,  $G_d = -3 \text{ mS}$  and  $G_d'' = 12 \text{ mS/V}^2$ . If the bias voltage is 5 volts,  $G_d = -1 \text{ mS}$ , while  $G_d''$  remains the same. The Gunn diode is connected to a resonant load whose admittance is

$$Y_L = \frac{1}{R_L} + j\omega C + \frac{1}{j\omega L}$$

Find a value for  $R_L$  for which the circuit will oscillate when the bias voltage is 7 volts, but not when it is 5 volts.

4. A 5 cm length of  $50 \Omega$  coaxial cable is short circuited at both ends. If this is to be used as a resonator for a Gunn diode oscillator, at what frequencies might the oscillator produce power? Should the diode be connected to the midpoint of this cable or not, and why?