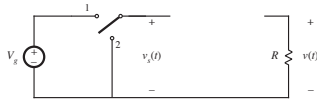


Chapter 2 Principles of Steady-State Converter Analysis


- 2.1. Introduction
- 2.2. Inductor volt-second balance, capacitor charge balance, and the small ripple approximation
- 2.3. Boost converter example
- 2.4. Cuk converter example
- 2.5. Estimating the ripple in converters containing two-pole low-pass filters
- 2.6. Summary of key points

2.1 Introduction Buck converter

SPDT switch changes dc component



Switch output voltage waveform

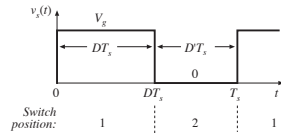


Duty cycle D :

$$0 \leq D \leq 1$$

complement D' :

$$D' = 1 - D$$

Dc component of switch output voltage


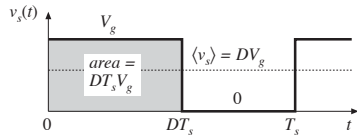


Fourier analysis: Dc component = average value


$$\langle v_s \rangle = \frac{1}{T_s} \int_0^{T_s} v_s(t) dt$$

$$\langle v_s \rangle = \frac{1}{T_s} (DT_s V_g) = DV_g$$

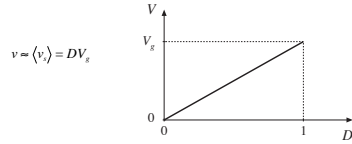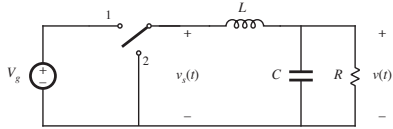Insertion of low-pass filter to remove switching harmonics and pass only dc component




Three basic dc-dc converters

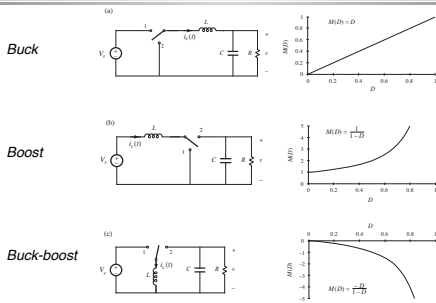

Objectives of this chapter

- Develop techniques for easily determining output voltage of an arbitrary converter circuit
- Derive the principles of *inductor volt-second balance* and *capacitor charge (amp-second) balance*
- Introduce the key *small ripple approximation*
- Develop simple methods for selecting filter element values
- Illustrate via examples

Boost converter analysis

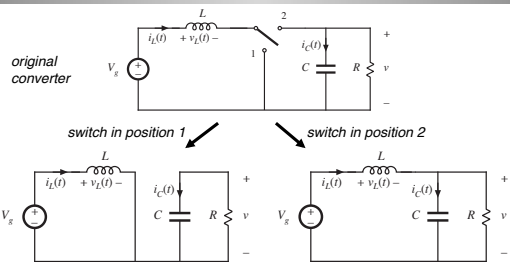

Subinterval 1: switch in position 1

Inductor voltage and capacitor current


$$v_L = V_g$$

$$i_C = -v/R$$

Small ripple approximation:

$$v_L = V_g$$

$$i_C = -V/R$$

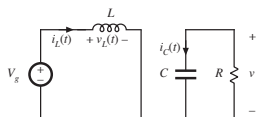

Subinterval 2: switch in position 2

Inductor voltage and capacitor current


$$v_L = V_g - v$$

$$i_C = i_L - v/R$$


Small ripple approximation:

$$v_L = V_g - V$$

$$i_C = I - V/R$$

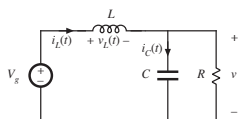

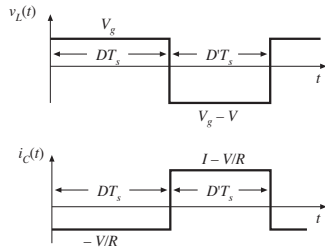Inductor voltage and capacitor current waveforms



Inductor volt-second balance

Net volt-seconds applied to inductor over one switching period:

$$\int_0^{T_s} v_L(t) dt = (V_g) DT_s + (V_g - V) DT_s$$

Equate to zero and collect terms:


$$V_g(D + D) - V D = 0$$

Solve for V:


$$V = \frac{V_g}{D}$$

The voltage conversion ratio is therefore
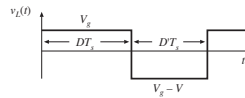
$$M(D) = \frac{V}{V_g} = \frac{1}{D} = \frac{1}{1-D}$$




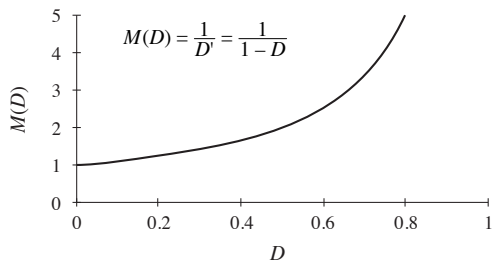Conversion ratio $M(D)$ of the boost converter




2.4 Cuk converter example

Cuk converter, with ideal switch

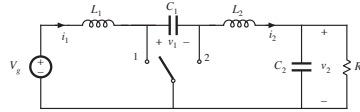

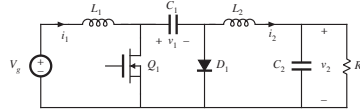Cuk converter: practical realization using MOSFET and diode



Analysis strategy

This converter has two inductor currents and two capacitor voltages, that can be expressed as


$$i_1(t) = I_1 + i_{1,ripple}(t)$$

$$i_2(t) = I_2 + i_{2,ripple}(t)$$

$$v_1(t) = V_1 + v_{1,ripple}(t)$$

$$v_2(t) = V_2 + v_{2,ripple}(t)$$

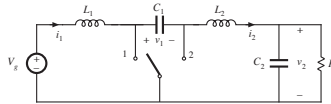To solve the converter in steady state, we want to find the dc components I_1 , I_2 , V_1 , and V_2 , when the ripples are small.




Strategy:


- Apply volt-second balance to each inductor voltage
- Apply charge balance to each capacitor current
- Simplify using the small ripple approximation
- Solve the resulting four equations for the four unknowns I_1 , I_2 , V_1 , and V_2 .

Cuk converter circuit with switch in positions 1 and 2

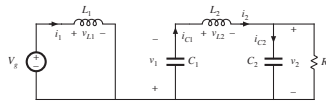
Switch in position 1:
MOSFET conducts
Capacitor C_1 releases energy to output



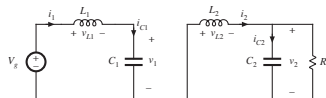Switch in position 2:
diode conducts
Capacitor C_1 is charged from input



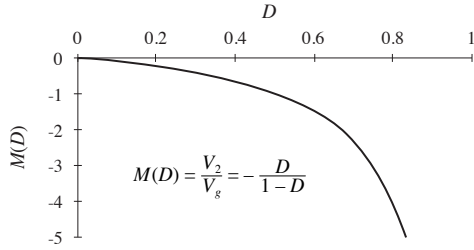Cuk converter conversion ratio $M = V/V_g$




Inductor current waveforms

Interval 1 slopes, using small ripple approximation:

$$\frac{di_1(t)}{dt} = \frac{v_{L1}(t)}{L_1} = \frac{V_g}{L_1}$$

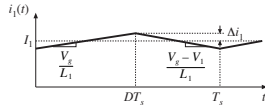
$$\frac{di_2(t)}{dt} = \frac{v_{L2}(t)}{L_2} = \frac{-V_1 - V_2}{L_2}$$



Interval 2 slopes:

$$\frac{di_1(t)}{dt} = \frac{v_{L1}(t)}{L_1} = \frac{V_g - V_1}{L_1}$$
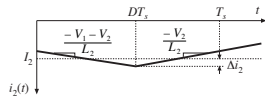
$$\frac{di_2(t)}{dt} = \frac{v_{L2}(t)}{L_2} = \frac{-V_2}{L_2}$$




Capacitor C_1 waveform

Subinterval 1:

$$\frac{dv_1(t)}{dt} = \frac{i_{C1}(t)}{C_1} = \frac{I_2}{C_1}$$

Subinterval 2:
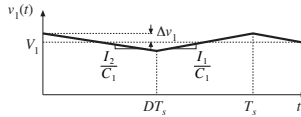
$$\frac{dv_1(t)}{dt} = \frac{i_{C1}(t)}{C_1} = \frac{I_1}{C_1}$$



2.6 Summary of Key Points

1. The dc component of a converter waveform is given by its average value, or the integral over one switching period, divided by the switching period. Solution of a dc-dc converter to find its dc, or steady-state, voltages and currents therefore involves averaging the waveforms.
2. The linear ripple approximation greatly simplifies the analysis. In a well-designed converter, the switching ripples in the inductor currents and capacitor voltages are small compared to the respective dc components, and can be neglected.
3. The principle of inductor volt-second balance allows determination of the dc voltage components in any switching converter. In steady-state, the average voltage applied to an inductor must be zero.

Summary of Chapter 2

4. The principle of capacitor charge balance allows determination of the dc components of the inductor currents in a switching converter. In steady-state, the average current applied to a capacitor must be zero.
5. By knowledge of the slopes of the inductor current and capacitor voltage waveforms, the ac switching ripple magnitudes may be computed. Inductance and capacitance values can then be chosen to obtain desired ripple magnitudes.
6. In converters containing multiple-pole filters, continuous (nonpulsating) voltages and currents are applied to one or more of the inductors or capacitors. Computation of the ac switching ripple in these elements can be done using capacitor charge and/or inductor flux-linkage arguments, without use of the small-ripple approximation.
7. Converters capable of increasing (boost), decreasing (buck), and inverting the voltage polarity (buck-boost and Cuk) have been described. Converter circuits are explored more fully in a later chapter.
