

Chapter 3. Steady-State Equivalent Circuit Modeling, Losses, and Efficiency

- 3.1. The dc transformer model
- 3.2. Inclusion of inductor copper loss
- 3.3. Construction of equivalent circuit model
- 3.4. How to obtain the input port of the model
- 3.5. Example: inclusion of semiconductor conduction losses in the boost converter model
- 3.6. Summary of key points

3.1. The dc transformer model

Basic equations of an ideal dc-dc converter:


$$P_{in} = P_{out} \quad (\eta = 100\%)$$

$$V_g I_g = V I$$

$$V = M(D) V_g \quad (\text{ideal conversion ratio})$$


$$I_g = M(D) I$$

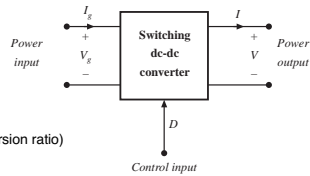These equations are valid in steady-state. During transients, energy storage within filter elements may cause $P_{in} \neq P_{out}$




Equivalent circuits corresponding to ideal dc-dc converter equations
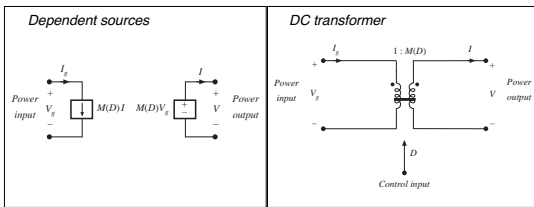
$$P_{in} = P_{out} \quad V_g I_g = V I \quad V = M(D) V_g \quad I_g = M(D) I$$



The DC transformer model



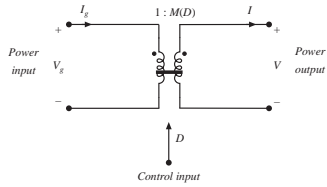


Models basic properties of ideal dc-dc converter:

- conversion of dc voltages and currents, ideally with 100% efficiency
- conversion ratio M controllable via duty cycle

- Solid line denotes ideal transformer model, capable of passing dc voltages and currents
- Time-invariant model (no switching) which can be solved to find dc components of converter waveforms

Example: use of the DC transformer model

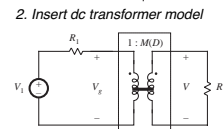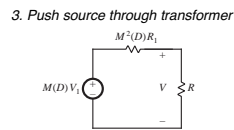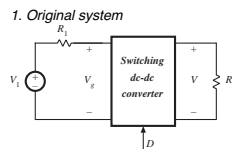


4. Solve circuit


$$V = M(D) V_g \frac{R}{R + M^2(D) R_1}$$

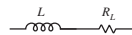3.2. Inclusion of inductor copper loss

Dc transformer model can be extended, to include converter nonidealities.
 Example: inductor copper loss (resistance of winding):



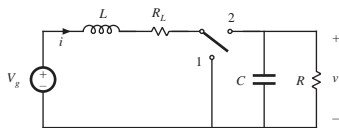Insert this inductor model into boost converter circuit:




Inductor voltage and capacitor current waveforms

Average inductor voltage:

$$\langle v_L(t) \rangle = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt$$
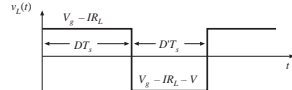
$$= D(V_g - I R_L) + D'(V_g - I R_L - V)$$




Inductor volt-second balance:

$$0 = V_g - I R_L - D'V$$

Average capacitor current:
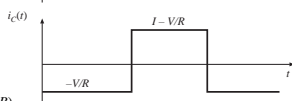
$$\langle i_C(t) \rangle = D(-V/R) + D'(I - V/R)$$



Capacitor charge balance:

$$0 = D'I - V/R$$

Solution for output voltage


We now have two equations and two unknowns:

$$0 = V_g - I R_L - D'V$$

$$0 = D'I - V/R$$

Eliminate I and solve for V :
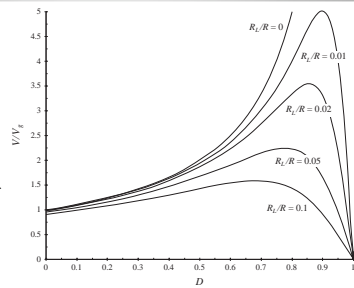
$$\frac{V}{V_g} = \frac{1}{D'} \frac{1}{(1 + R_L/D'^2 R)}$$



3.3. Construction of equivalent circuit model

Results of previous section (derived via inductor volt-sec balance and capacitor charge balance):

$$\langle v_L \rangle = 0 = V_g - I R_L - D'V$$


$$\langle i_C \rangle = 0 = D'I - V/R$$

View these as loop and node equations of the equivalent circuit.
Reconstruct an equivalent circuit satisfying these equations

Inductor voltage equation

$$\langle v_L \rangle = 0 = V_s - I R_L - DV$$

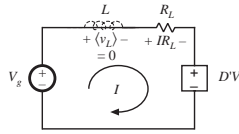- Derived via Kirchoff's voltage law, to find the inductor voltage during each subinterval
- Average inductor voltage then set to zero
- This is a loop equation: the dc components of voltage around a loop containing the inductor sum to zero




- $I R_L$ term: voltage across resistor of value R_L having current I
- DV term: for now, leave as dependent source

Capacitor current equation

$$\langle i_C \rangle = 0 = DI - V/R$$

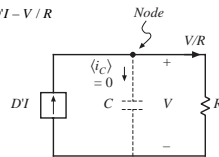
- Derived via Kirchoff's current law, to find the capacitor current during each subinterval
- Average capacitor current then set to zero
- This is a node equation: the dc components of current flowing into a node connected to the capacitor sum to zero




- V/R term: current through load resistor of value R having voltage V
- DI term: for now, leave as dependent source

Complete equivalent circuit


The two circuits, drawn together:

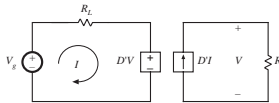

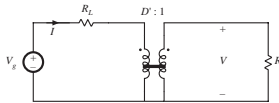
The dependent sources are equivalent to a D' : 1 transformer:



Dependent sources and transformers

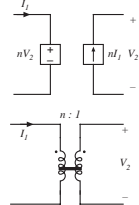

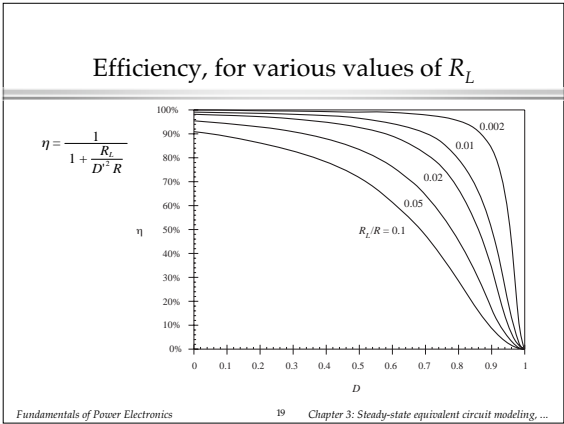- sources have same coefficient
- reciprocal voltage/current dependence



3.4. How to obtain the input port of the model

Buck converter example — use procedure of previous section to derive equivalent circuit

Average inductor voltage and capacitor current:

$$\langle v_L \rangle = 0 = DV_g - I_L R_L - V_C \quad \langle i_C \rangle = 0 = I_L - V_C / R$$

Fundamentals of Power Electronics 20 Chapter 3: Steady-state equivalent circuit modeling, ...

Construct equivalent circuit as usual


$\langle v_L \rangle = 0 = DV_g - I_L R_L - V_C$
 $\langle i_C \rangle = 0 = I_L - V_C / R$

What happened to the transformer?
• Need another equation

Fundamentals of Power Electronics 21 Chapter 3: Steady-state equivalent circuit modeling, ...

Modeling the converter input port

Input current waveform $i_g(t)$:

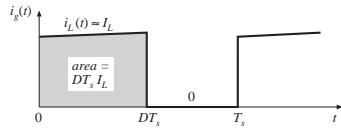


Dc component (average value) of $i_g(t)$ is

$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = DI_L$$


Input port equivalent circuit
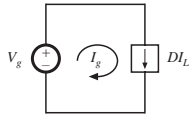
$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = DI_L$$




Complete equivalent circuit, buck converter

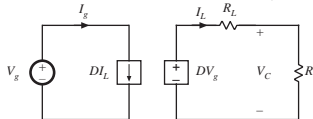Input and output port equivalent circuits, drawn together:




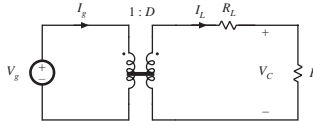Replace dependent sources with equivalent dc transformer:



3.5. Example: inclusion of semiconductor conduction losses in the boost converter model

Boost converter example

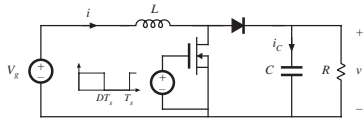


Models of on-state semiconductor devices:

MOSFET: on-resistance R_{on}


Diode: constant forward voltage V_D plus on-resistance R_D

Insert these models into subinterval circuits

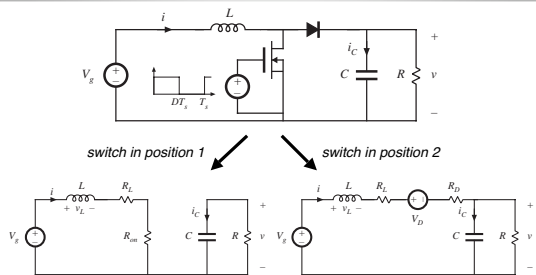Boost converter example: circuits during subintervals 1 and 2



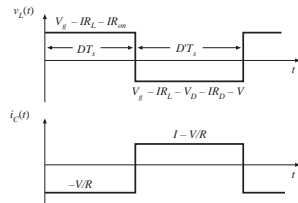Average inductor voltage and capacitor current



$$\langle v_L \rangle = D(V_g - IR_L - IR_{on}) + D'(V_g - IR_L - V_D - IR_D - V) = 0$$

$$\langle i_C \rangle = D(-V/R) + D'(I - V/R) = 0$$
