

## Chapter 5. The Discontinuous Conduction Mode

- 5.1. Origin of the discontinuous conduction mode, and mode boundary
- 5.2. Analysis of the conversion ratio  $M(D,K)$
- 5.3. Boost converter example
- 5.4. Summary of results and key points

---

---

---

---

---

---

---

---

---

---

### Introduction to Discontinuous Conduction Mode (DCM)

- Occurs because switching ripple in inductor current or capacitor voltage causes polarity of applied switch current or voltage to reverse, such that the current- or voltage-unidirectional assumptions made in realizing the switch are violated.
- Commonly occurs in dc-dc converters and rectifiers, having single-quadrant switches. May also occur in converters having two-quadrant switches.
- Typical example: dc-dc converter operating at light load (small load current). Sometimes, dc-dc converters and rectifiers are purposely designed to operate in DCM at all loads.
- Properties of converters change radically when DCM is entered:
  - $M$  becomes load-dependent
  - Output impedance is increased
  - Dynamics are altered
  - Control of output voltage may be lost when load is removed

---

---

---

---

---

---

---


---

---

---

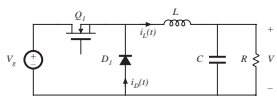
### 5.1. Origin of the discontinuous conduction mode, and mode boundary

Buck converter example, with single-quadrant switches



Minimum diode current is  $(I - \Delta i_L)$   
 Dc component  $I = V/R$   
 Current ripple is  
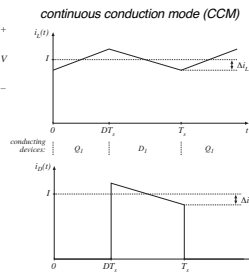
$$\Delta i_L = \frac{(V_s - V)}{2L} DT_s = \frac{V_s D DT_s}{2L}$$
  
 Note that  $I$  depends on load, but  $\Delta i_L$  does not.




---

---

---

---

---

---

---


---

---

---



## K and $K_{crit}$ vs. D

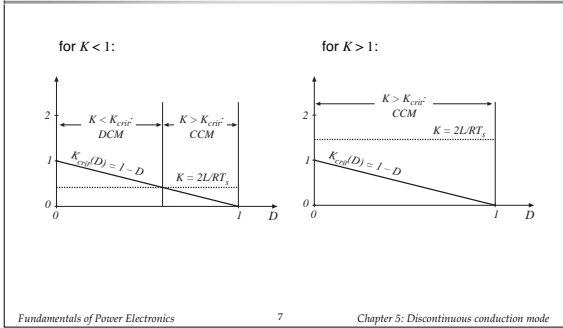


---

---

---

---

---

---

---

---

---

---

## Critical load resistance $R_{crit}$

Solve  $K_{crit}$  equation for load resistance  $R$ :

$R < R_{crit}(D)$  for CCM  
 $R > R_{crit}(D)$  for DCM

where  $R_{crit}(D) = \frac{2L}{DT_s}$

Fundamentals of Power Electronics      8      Chapter 5: Discontinuous conduction mode

---

---

---

---

---

---

---

---

---

---

## Summary: mode boundary

$K > K_{crit}(D)$  or  $R < R_{crit}(D)$  for CCM  
 $K < K_{crit}(D)$  or  $R > R_{crit}(D)$  for DCM

*Table 5.1. CCM-DCM mode boundaries for the buck, boost, and buck-boost converters*

Converter	$K_{crit}(D)$	$\max_{0 < D < 1} (K_{crit})$	$R_{crit}(D)$	$\min_{0 < D < 1} (R_{crit})$
Buck	$(1-D)$	1	$\frac{2L}{(1-D)T_s}$	$2 \frac{L}{T_s}$
Boost	$D(1-D)^2$	$\frac{4}{27}$	$\frac{2L}{D(1-D)^2 T_s}$	$\frac{27}{2} \frac{L}{T_s}$
Buck-boost	$(1-D)^2$	1	$\frac{2L}{(1-D)^2 T_s}$	$2 \frac{L}{T_s}$

Fundamentals of Power Electronics      9      Chapter 5: Discontinuous conduction mode

---

---

---

---

---

---

---

---

---

---

## 5.2. Analysis of the conversion ratio $M(D,K)$

Analysis techniques for the discontinuous conduction mode:

Inductor volt-second balance

$$\langle v_L \rangle = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = 0$$

Capacitor charge balance

$$\langle i_C \rangle = \frac{1}{T_s} \int_0^{T_s} i_C(t) dt = 0$$

Small ripple approximation sometimes applies:

$$v(t) \approx V \quad \text{because } \Delta v \ll V$$

$$i(t) \approx I \quad \text{is a poor approximation when } \Delta i > I$$

Converter steady-state equations obtained via charge balance on each capacitor and volt-second balance on each inductor. Use care in applying small ripple approximation.

---

---

---

---

---

---

---

---


---

---

---

---
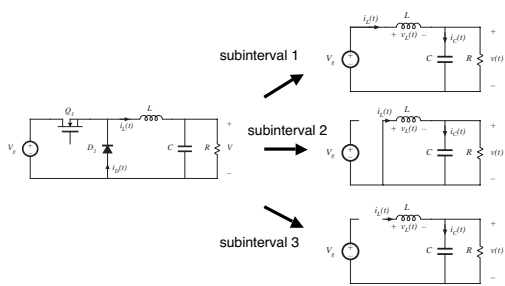
### Example: Analysis of DCM buck converter $M(D,K)$




---

---

---

---

---

---

---

---

---

---

---

---

### Subinterval 1


$$v_L(t) = V_g - v(t)$$

$$i_C(t) = i_L(t) - v(t) / R$$

Small ripple approximation for  $v(t)$  (but not for  $i(t)$ ):

$$v_L(t) \approx V_g - V$$

$$i_C(t) \approx i_L(t) - V / R$$

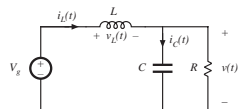


---

---

---

---

---

---

---

---

---

---

---

---

### Subinterval 2


$$v_L(t) = -v(t)$$

$$i_C(t) = i_L(t) - v(t) / R$$

Small ripple approximation  
for  $v(t)$  but not for  $i(t)$ :

$$v_L(t) = -V$$

$$i_C(t) = i_L(t) - V / R$$

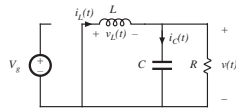


---

---

---

---

---

---

---

---

---

---

### Subinterval 3


$$v_L = 0, \quad i_C = 0$$

$$i_L(t) = i_C(t) - v(t) / R$$

Small ripple approximation:

$$v_L(t) = 0$$

$$i_C(t) = -V / R$$

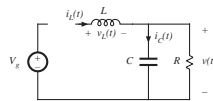


---

---

---

---

---

---


---

---

---

---

### Inductor volt-second balance

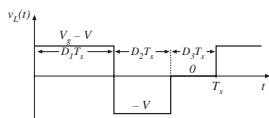

Volt-second balance:

$$\langle v_L(t) \rangle = D_1(V_g - V) + D_2(-V) + D_3(0) = 0$$

Solve for  $V$ :

$$V = V_g \frac{D_1}{D_1 + D_2} \quad \text{note that } D_2 \text{ is unknown}$$

---

---

---

---

---

---

---


---

---

---



### Buck converter $M(D,K)$

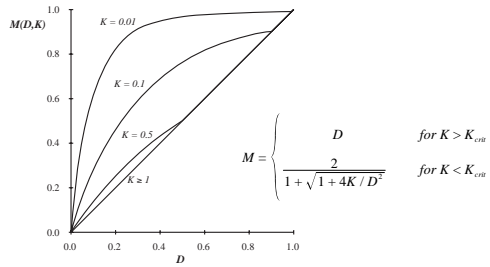


---

---

---

---


---

---

---

---

### 5.3. Boost converter example

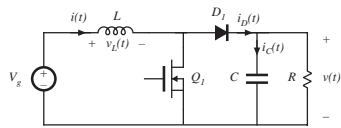

Mode boundary:

$$I > \Delta i_L \text{ for CCM}$$

$$I < \Delta i_L \text{ for DCM}$$

Previous CCM soln:

$$I = \frac{V_g}{D^2 R} \quad \Delta i_L = \frac{V_g}{2L} DT_s$$

---

---

---

---

---

---

---

---

### Mode boundary


$$\frac{V_g}{D^2 R} > \frac{DT_s V_g}{2L} \text{ for CCM}$$

$$\frac{2L}{RT_s} > DD^2 \text{ for CCM}$$

$$K > K_{crit}(D) \text{ for CCM}$$

$$K < K_{crit}(D) \text{ for DCM}$$

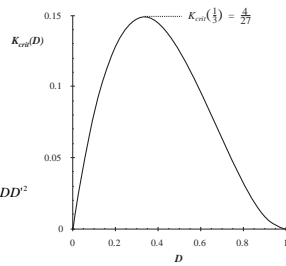where  $K = \frac{2L}{RT_s}$  and  $K_{crit}(D) = DD^2$




---

---

---

---

---

---

---

---



### Subinterval 2


$$v_L(t) = V_g - v(t)$$

$$i_C(t) = i(t) - v(t) / R$$

Small ripple approximation  
for  $v(t)$  but not for  $i(t)$ :

$$v_L(t) = V_g - V$$

$$i_C(t) = i(t) - V / R$$

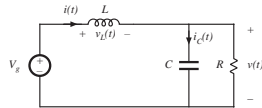

$$D_1 T_s < t < (D_1 + D_2) T_s$$

---

---

---

---

---

---

---

---

---

---

### Subinterval 3


$$v_L = 0, \quad i = 0$$

$$i_C(t) = -v(t) / R$$

Small ripple approximation:

$$v_L(t) = 0$$

$$i_C(t) = -V / R$$

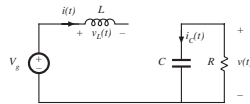

$$(D_1 + D_2) T_s < t < T_s$$

---

---

---

---

---

---


---

---

---

---

### Inductor volt-second balance

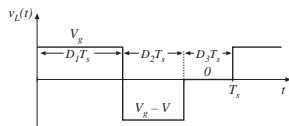

Volt-second balance:

$$D_1 V_g + D_2 (V_g - V) + D_3 (0) = 0$$

Solve for  $V$ :

$$V = \frac{D_1 + D_2}{D_2} V_g \quad \text{note that } D_2 \text{ is unknown}$$

---

---

---

---

---

---

---

---

---

---



### Solution for $V$

Two equations and two unknowns ( $V$  and  $D_2$ ):

$$V = \frac{D_1 + D_2}{D_2} V_g \quad (\text{from inductor volt-second balance})$$

$$\frac{V D_1 D_2 T_s}{2L} = \frac{V}{R} \quad (\text{from capacitor charge balance})$$

Eliminate  $D_2$ , solve for  $V$ . From volt-sec balance eqn:

$$D_2 = D_1 \frac{V_g}{V - V_g}$$

Substitute into charge balance eqn, rearrange terms:

$$V^2 - V V_g - \frac{V_g^2 D_1^2}{K} = 0$$

---

---

---

---

---

---

---

---

---

---

---

---

### Solution for $V$

$$V^2 - V V_g - \frac{V_g^2 D_1^2}{K} = 0$$

Use quadratic formula:

$$\frac{V}{V_g} = \frac{1 \pm \sqrt{1 + 4D_1^2 / K}}{2}$$

Note that one root leads to positive  $V$ , while other leads to negative  $V$ . Select positive root:

$$\frac{V}{V_g} = M(D_1, K) = \frac{1 + \sqrt{1 + 4D_1^2 / K}}{2}$$

where  $K = 2L / RT_s$   
valid for  $K < K_{crit}(D)$

Transistor duty cycle  $D = \text{interval } 1 \text{ duty cycle } D_1$

---

---

---

---

---

---

---

---


---

---

---

---

### Boost converter characteristics

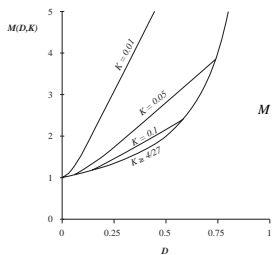

$$M = \begin{cases} \frac{1}{1-D} & \text{for } K > K_{crit} \\ \frac{1 + \sqrt{1 + 4D^2 / K}}{2} & \text{for } K < K_{crit} \end{cases}$$

Approximate  $M$  in DCM:

$$M \approx \frac{1}{2} + \frac{D}{\sqrt{K}}$$

---

---

---

---

---

---

---

---

---

---

---

---



## Summary of key points

4. Extra care is required when applying the small-ripple approximation. Some waveforms, such as the output voltage, should have small ripple which can be neglected. Other waveforms, such as one or more inductor currents, may have large ripple that cannot be ignored.
5. The characteristics of a converter changes significantly when the converter enters DCM. The output voltage becomes load-dependent, resulting in an increase in the converter output impedance.

---

---

---

---

---

---

---

---