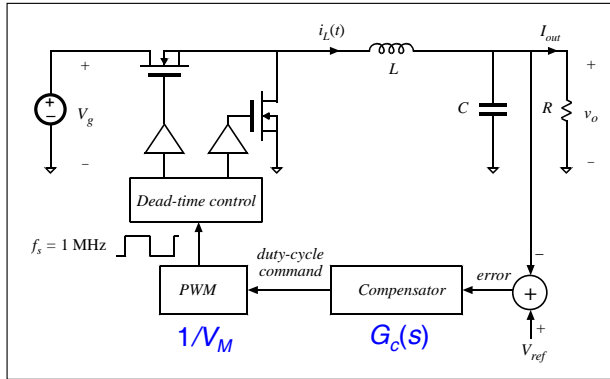


## Another Compensator Design Example




Point-of-Load Synchronous Buck Regulator

### Power stage parameters

- Switching frequency:  
 $f_s = 1\text{ MHz}$
- $V_{ref} = 1.8\text{ V}$
- $I_{out} = 0\text{ to }5\text{ A}$
- $V_g = 5\text{ V}$
- $L = 1\text{ }\mu\text{H}$
- $R_L = 30\text{ m}\Omega$
- $C = 200\text{ }\mu\text{F}$
- $R_{esr} = 0.8\text{ m}\Omega$
- $V_M = 1\text{ V}$
- $H = 1$

ECEN5797

## Buck Averaged Small-Signal Model

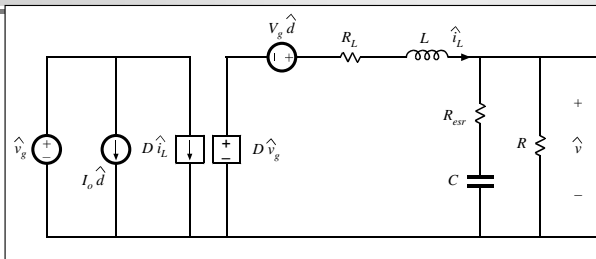

Pair of poles:

$$f_o = \frac{1}{2\pi\sqrt{CL}} = 11\text{ kHz}$$

$$Q_{loss} = \frac{\sqrt{L/C}}{R_{esr} + R_L} = 2.3 \rightarrow 7.2\text{ dB} \quad Q_{load} = \frac{R}{\sqrt{L/C}} > 5$$

$$Q = Q_{loss} \parallel Q_{load} = \frac{Q_{loss} Q_{load}}{Q_{loss} + Q_{load}} < 2.3 \rightarrow 7.2\text{ dB}$$

$$G_{vd}(s) = \frac{\hat{v}_o}{\hat{d}}$$

$$G_{vd}(s) = V_g \frac{1 + \frac{s}{\omega_{esr}}}{1 + \frac{1}{Q} \frac{s}{\omega_o} + \left(\frac{s}{\omega_o}\right)^2}$$

Low-frequency gain (including PWM gain):


$$G_{vdo} \frac{1}{V_M} = 5 \rightarrow 14\text{ dB}$$

ESR zero:

$$f_{esr} = \frac{1}{2\pi C R_{esr}} = 1\text{ MHz}$$

ECEN5797

### Uncompensated loop gain $T_u$

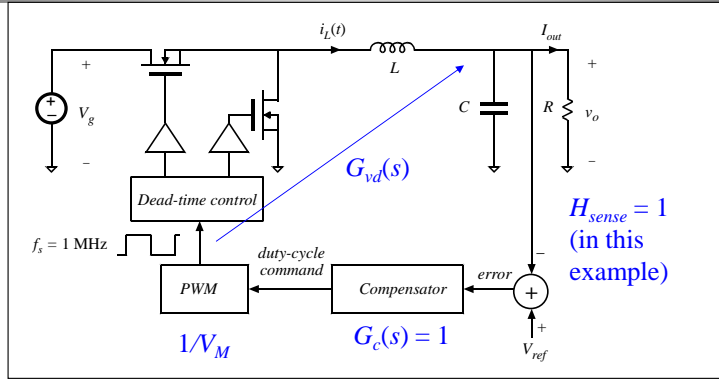


$$T_u(s) = H_{sense}(1/V_M)G_{vd}(s)$$

Plot magnitude and phase responses of  $T_u(s)$  to plan how to design  $G_c(s)$


ECEN5797

### Magnitude and phase Bode plots of $T_u$

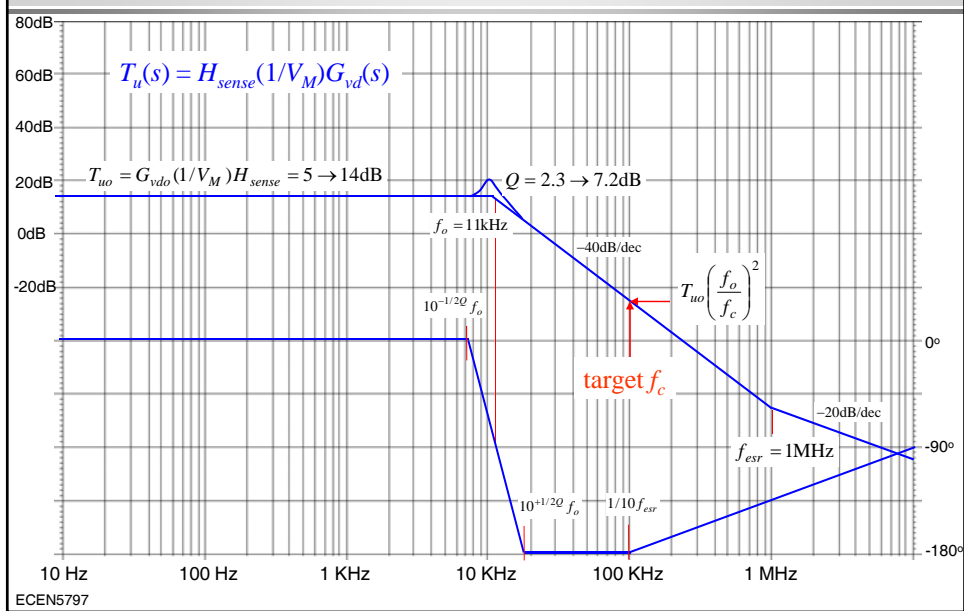

ECEN5797
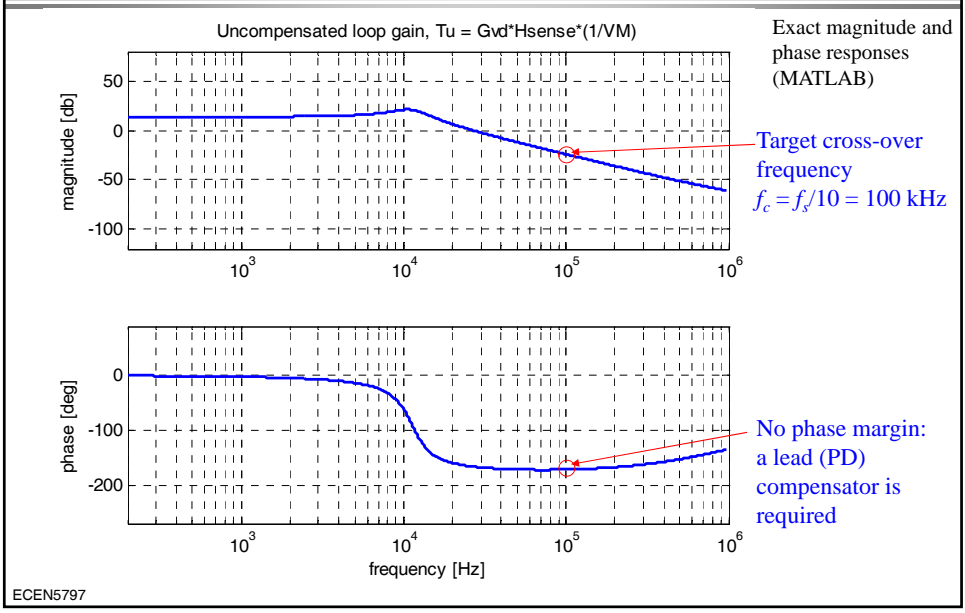
### Magnitude and phase Bode plots of $T_u$




### Lead (PD) compensator design

1. Choose:  $f_c = 100 \text{ kHz}$   
 $\theta = \varphi_m = 53^\circ$

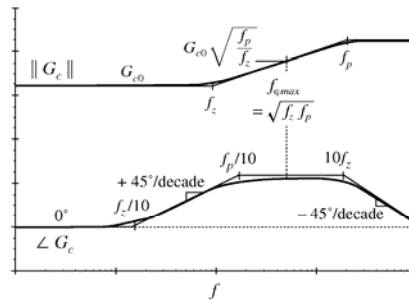2. Compute:

$$f_z = f_c \sqrt{\frac{1 - \sin(\theta)}{1 + \sin(\theta)}} = 33 \text{ kHz}$$

$$f_p = f_c \sqrt{\frac{1 + \sin(\theta)}{1 - \sin(\theta)}} = 300 \text{ kHz}$$



3. Find  $G_{co}$  to position the crossover frequency:

$$\underbrace{T_{uo} \left( \frac{f_o}{f_c} \right)^2}_{\text{Magnitude of } T_u \text{ at } f_c} \underbrace{G_{co} \sqrt{\frac{f_p}{f_z}}}_{\text{Magnitude of } G_c \text{ at } f_c} = 1 \quad \rightarrow \quad G_{co} = \frac{1}{T_{uo}} \left( \frac{f_c}{f_o} \right)^2 \sqrt{\frac{f_p}{f_z}} = 5.45 \rightarrow 15 \text{ dB}$$

Magnitude of  $T_u$  at  $f_c$     Magnitude of  $G_c$  at  $f_c$

### Lead (PD) compensator summary

$$G_c(s) = G_{co} \underbrace{\left(1 + \frac{s}{\omega_z}\right)}_{\text{Lead compensator}} \underbrace{\frac{1}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}}_{\text{HF pole}}$$

$$\begin{aligned} G_{co} &= 5.45 \rightarrow 15 \text{ dB} \\ f_z &= 33 \text{ kHz} \\ f_{p1} &= 300 \text{ kHz} \\ f_c &= 100 \text{ kHz} \quad (=1/10 \text{ of } f_s) \end{aligned}$$


High-frequency gain of the lead compensator:  $G_{co}f_{p1}/f_z = 49$  (34 dB)

Added high-frequency pole:  $f_{p2} = 1 \text{ MHz}$  ( $=f_{esr} = f_s$  in this example)

Practical implementation would require an op-amp with a gain bandwidth product of at least  $49 * f_{p2} = 49 \text{ MHz}$

ECEN5797


### Loop gain with lead (PD) compensator

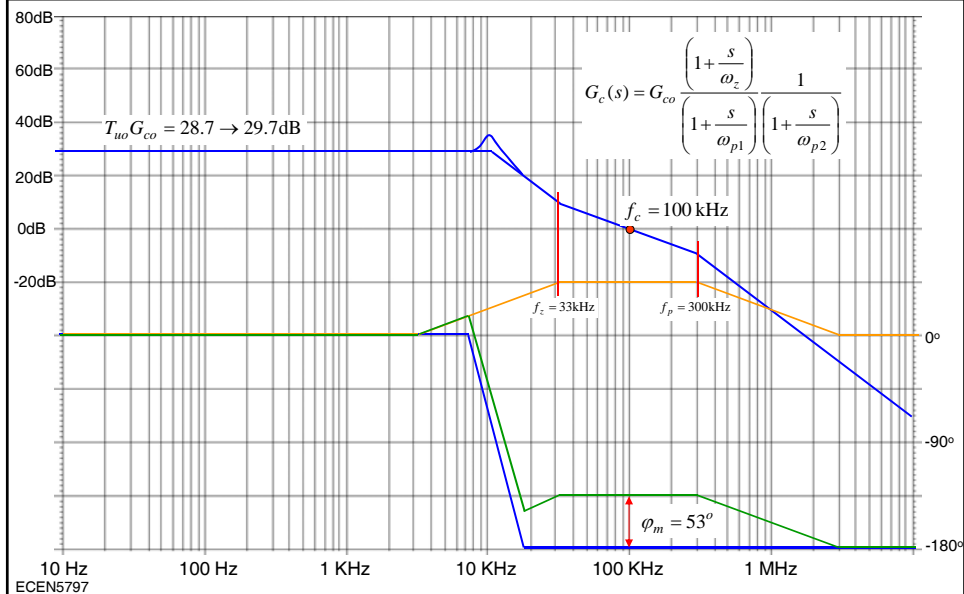
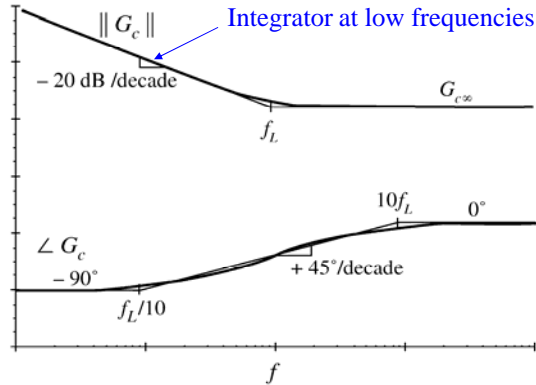
### Add lag (PI) compensator

$$G_c(s) = G_{c\infty} \left( 1 + \frac{\omega_L}{s} \right)$$


Improves low-frequency loop gain and regulation



Choose  $10f_L < f_c$  so that phase margin stays approximately the same:  $f_L = 8 \text{ kHz}$   
 Keep the same cross-over frequency:  $G_{c\infty} = G_{co} = G_{cm} = 5.45 \rightarrow 15 \text{ dB}$


ECEN5797

### Adding PI Compensator

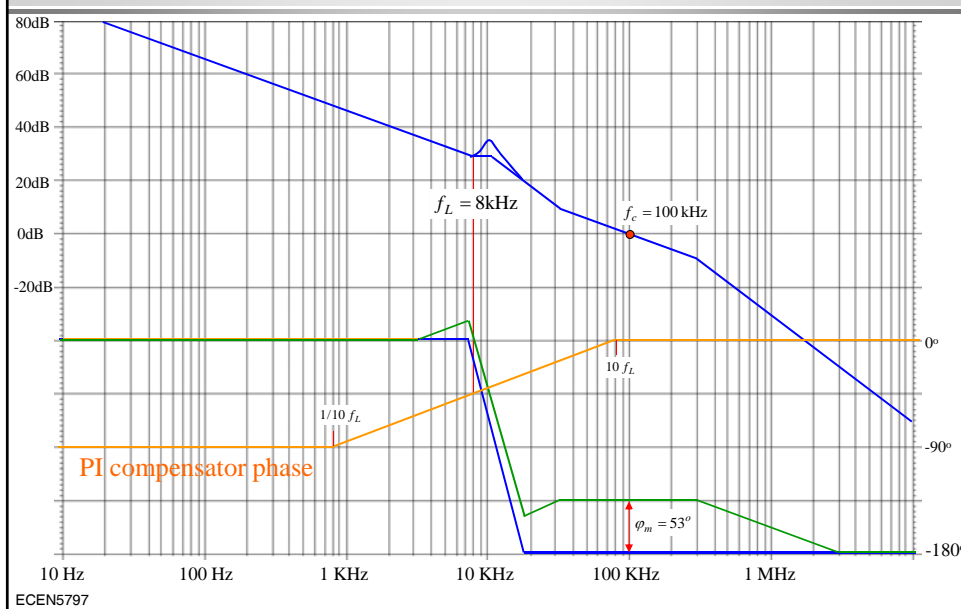

ECEN5797
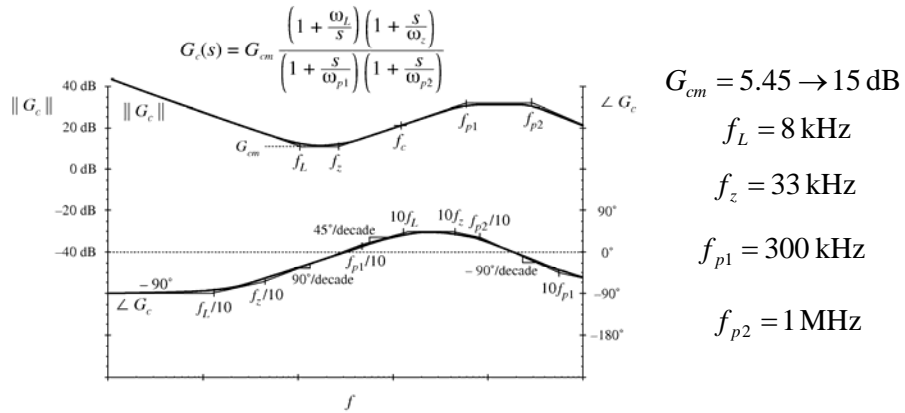
### Complete analog PID compensator: summary




Crossover frequency:  $f_c = 100 \text{ kHz}$  ( $=1/10$  of  $f_s$ )

Phase margin:  $\varphi_m = 53^\circ$


ECEN5797

### Magnitude and phase Bode plots of $T$

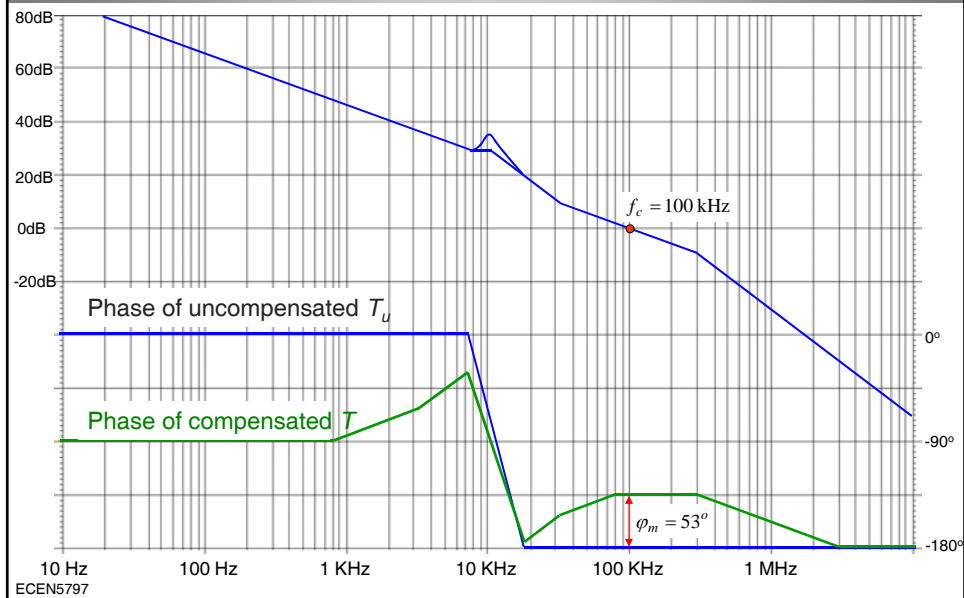


ECEN5797

### Verification: exact loop gain magnitude and phase responses (MATLAB)

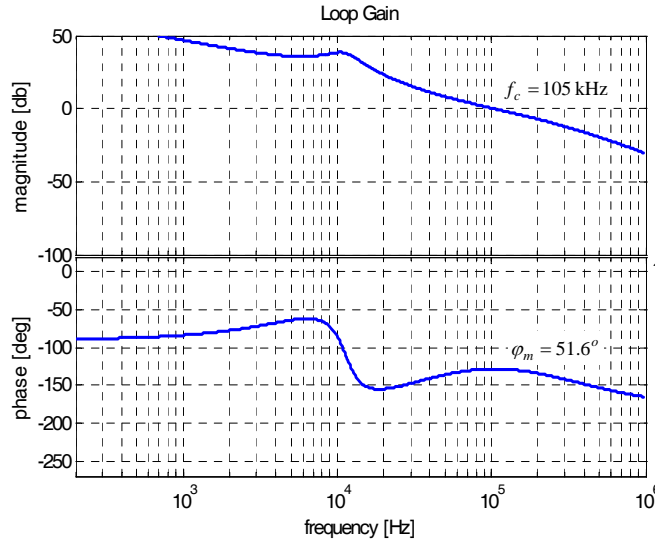

ECEN5797
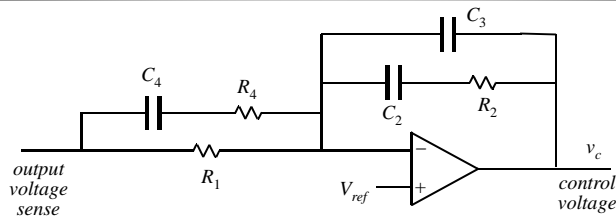
### Analog PID compensator implementation



Design equations (approximate)

$$G_c(s) = G_{cm} \frac{\left(1 + \frac{\omega_L}{s}\right) \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

$$G_{cm} = \frac{R_2}{R_1} \quad f_L = \frac{1}{2\pi R_2 C_2}$$

$$f_z = \frac{1}{2\pi(R_1 + R_4)C_4} \quad f_{p1} = \frac{1}{2\pi R_4 C_4}$$

$$f_{p2} = \frac{1}{2\pi R_2 C_3}$$

ECEN5797

## Verification of closed-loop responses

Closed-loop reference-to-output response

Closed-loop transfer function from  $\hat{v}_{ref}$  to  $\hat{v}(s)$  is:

$$\left. \frac{\hat{v}(s)}{\hat{v}_{ref}(s)} \right|_{\substack{v_g=0 \\ i_{load}=0}} = \frac{1}{H(s)} \frac{T(s)}{1+T(s)}$$


Closed-loop output impedance

$$\left. \frac{\hat{v}(s)}{-\hat{i}_{load}(s)} \right|_{\substack{v_{ref}=0 \\ v_g=0}} = \frac{Z_{out}(s)}{1+T(s)}$$

and step-load transient response


ECEN5797

## Construction of closed-loop $T/(1+T)$ response

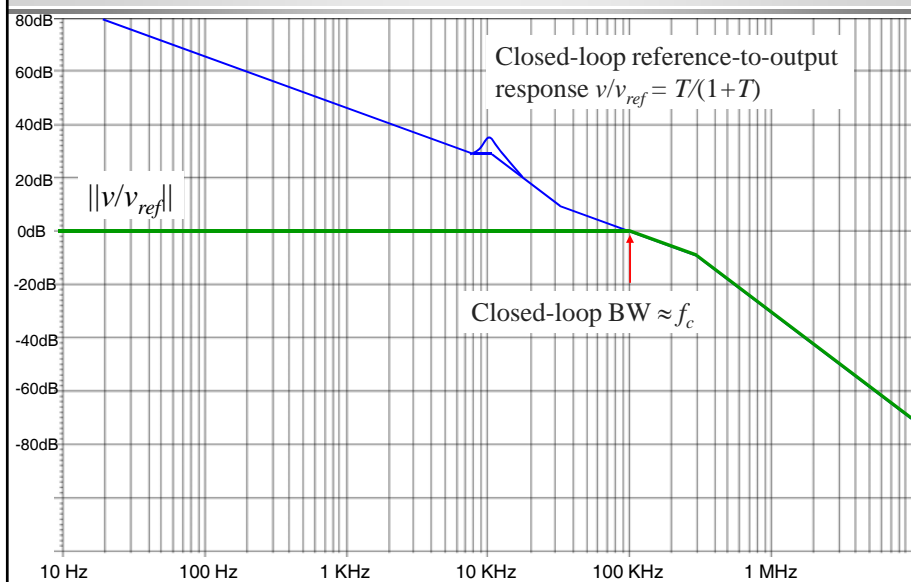


ECEN5797

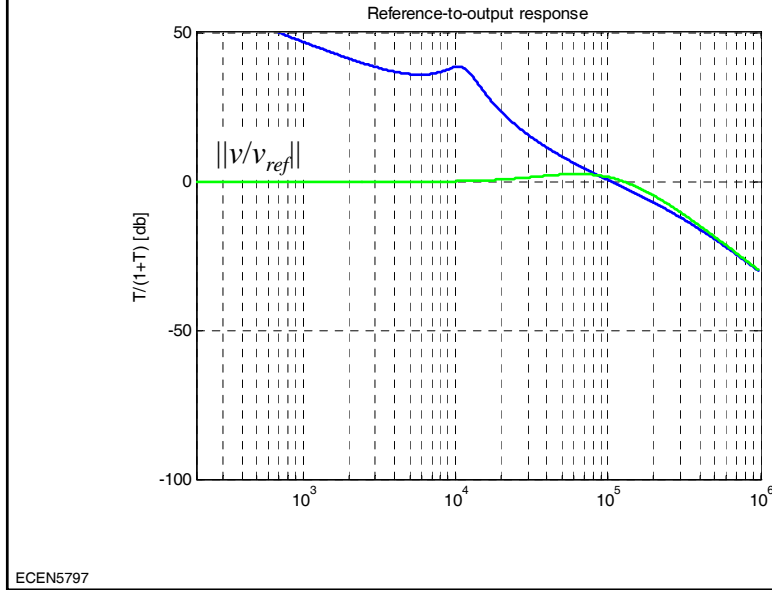
### Closed-loop reference-to-output response



### Small-signal step-reference response

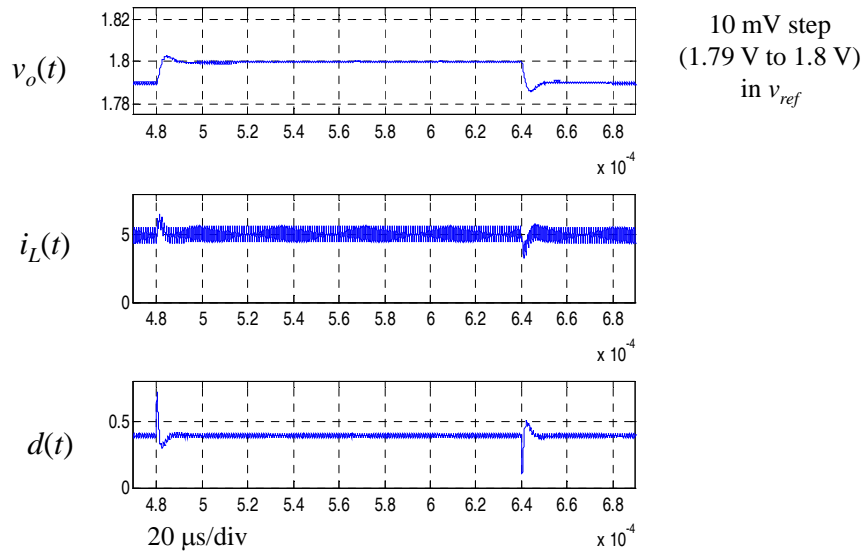


### Small-signal step-reference response

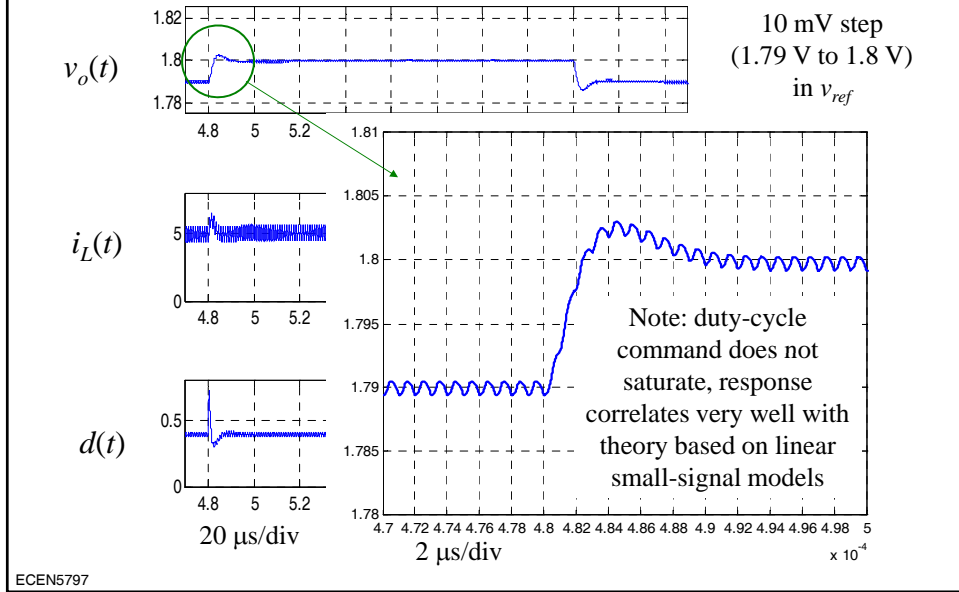
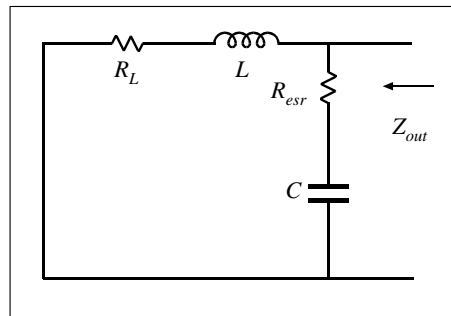
### Output impedance

Synchronous buck open-loop output impedance




$$Z_{out}(s) = \left( R_{esr} + \frac{1}{sC} \right) \parallel (R_L + sL)$$


- $L = 1 \mu\text{H}$
- $R_L = 30 \text{ m}\Omega$
- $C = 200 \mu\text{F}$
- $R_{esr} = 0.8 \text{ m}\Omega$

ECEN5797

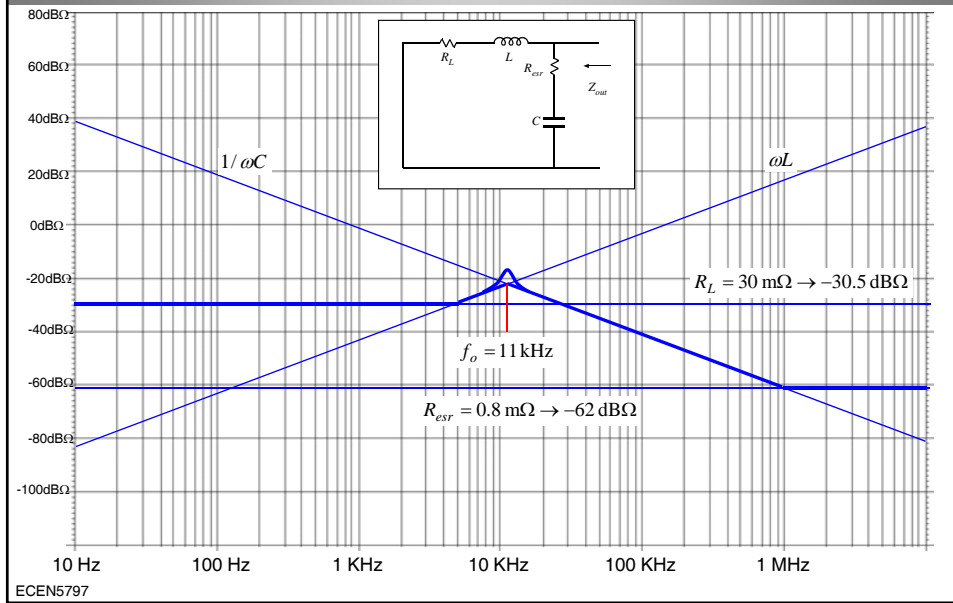
### Open-loop output impedance: algebra on the graph




### Construction of $1/(1+T)$

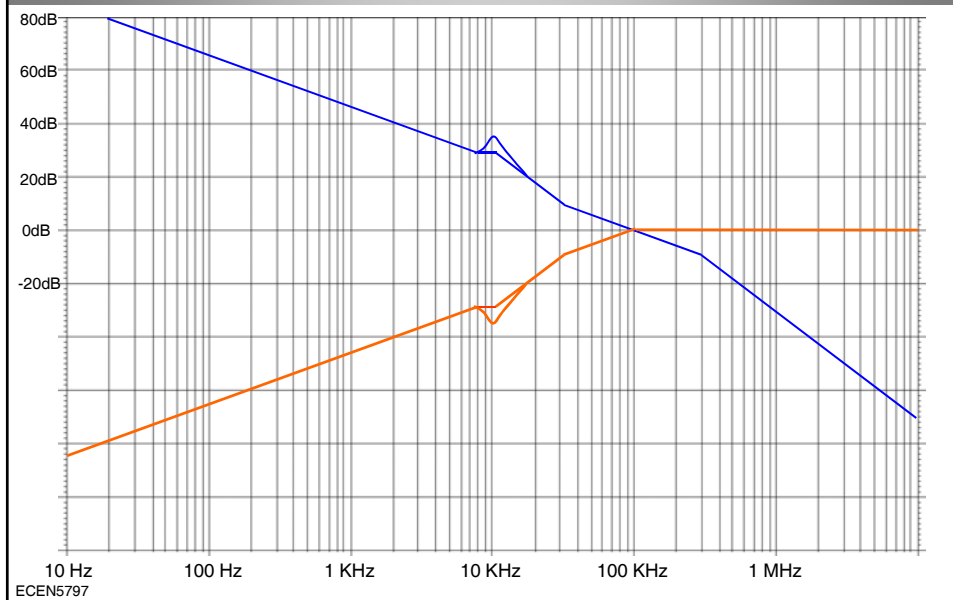

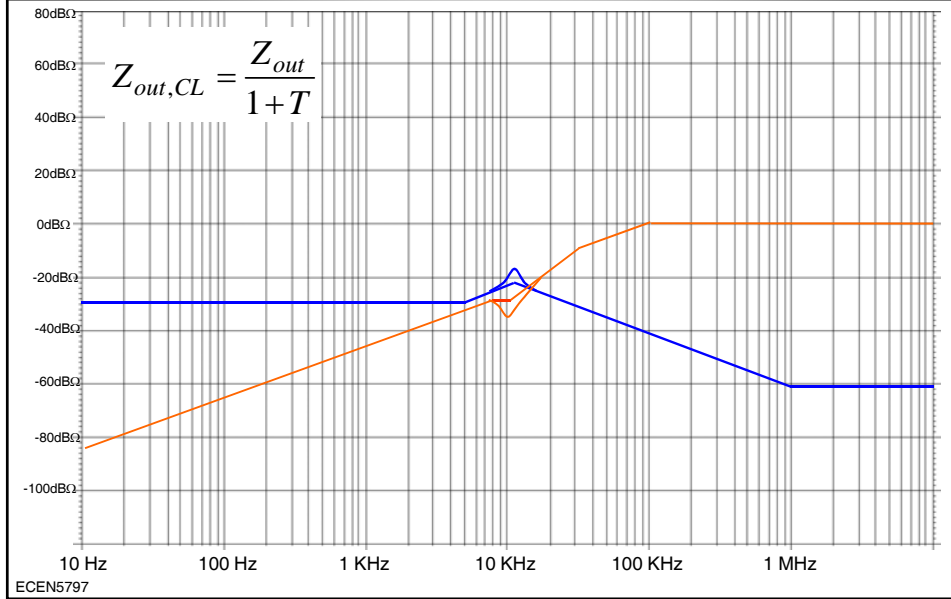
### Construction of closed-loop output impedance



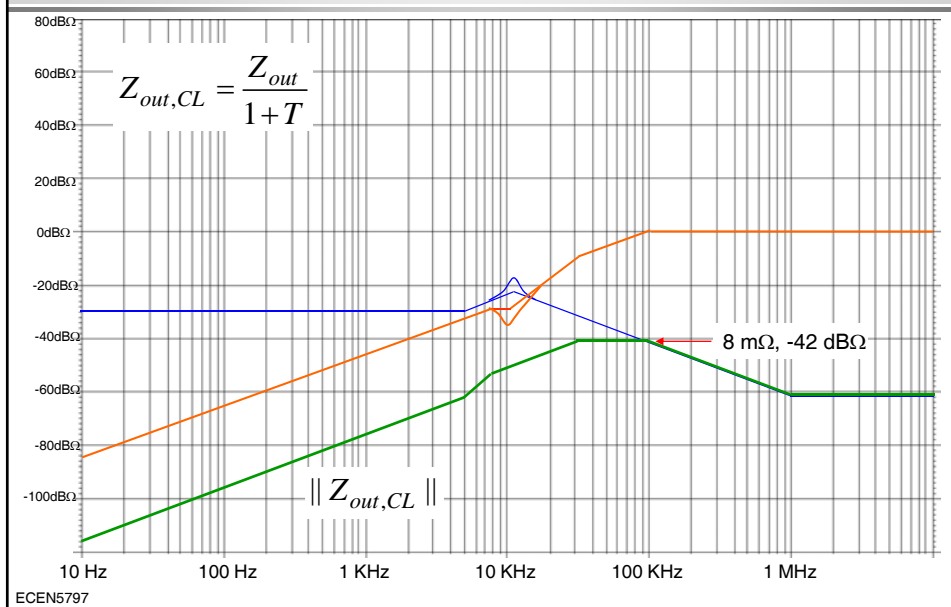
### Closed-loop output impedance $Z_{out,CL}$


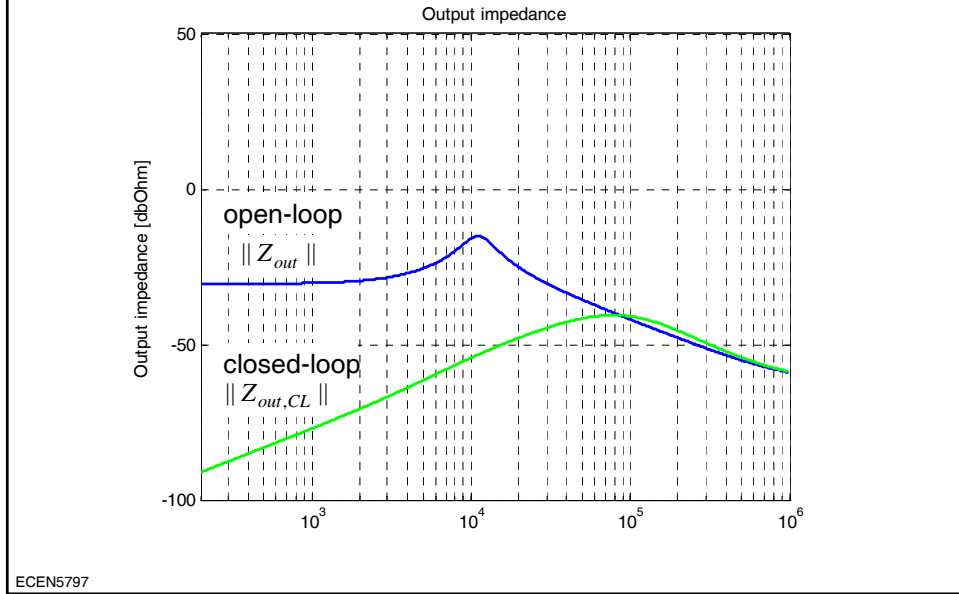
### Verification: closed-loop output impedance



### Step-load transient responses

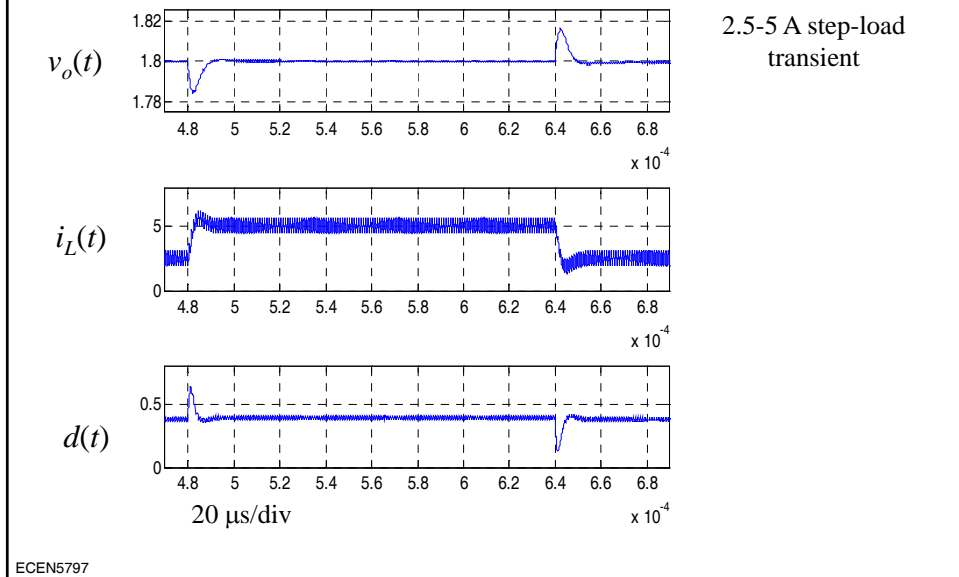

### Step-load transient responses

