

ECEN 4797/5797

Introduction to Power Electronics

Lecture #12

Monday, September 21, 2009





Discontinuous Conduction Mode

Chapter 5 ✓


Prof. Regan Zane

SPST


HW #2: Text Prob. 3.7

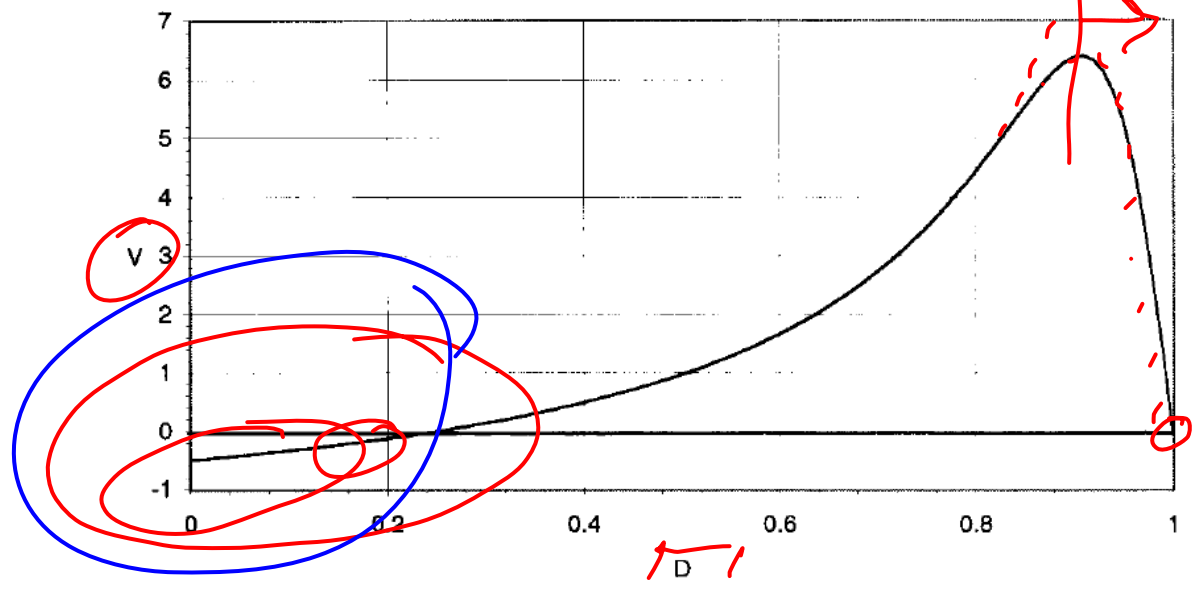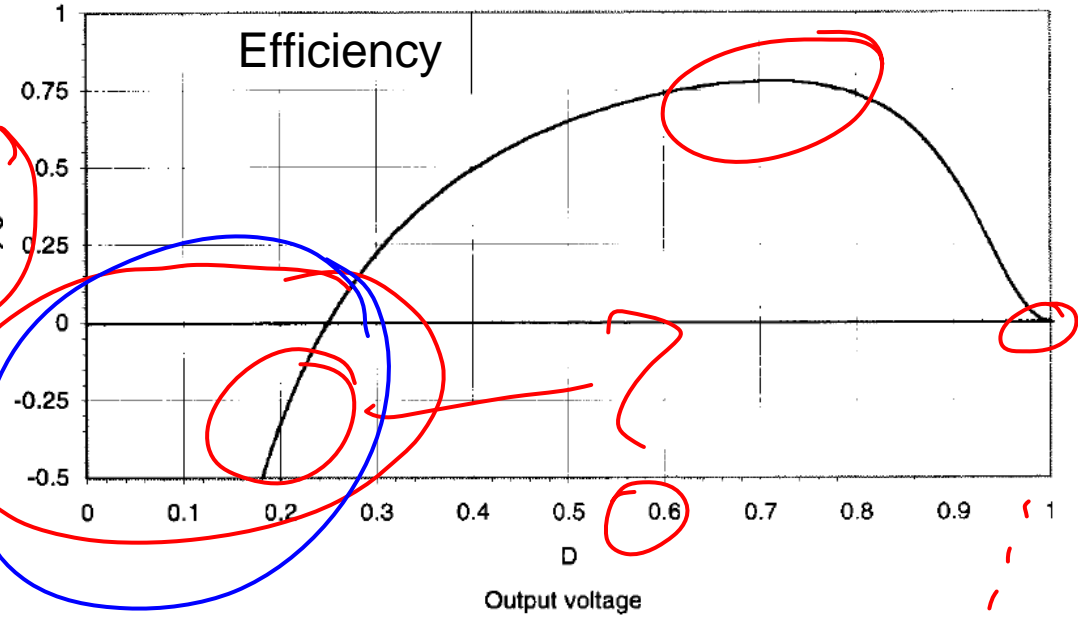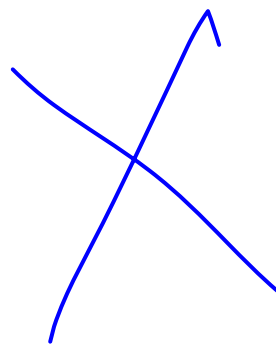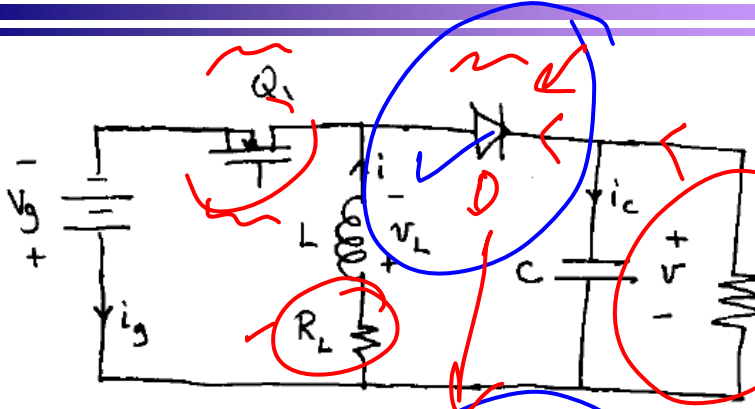

Buck Converter: switch realization

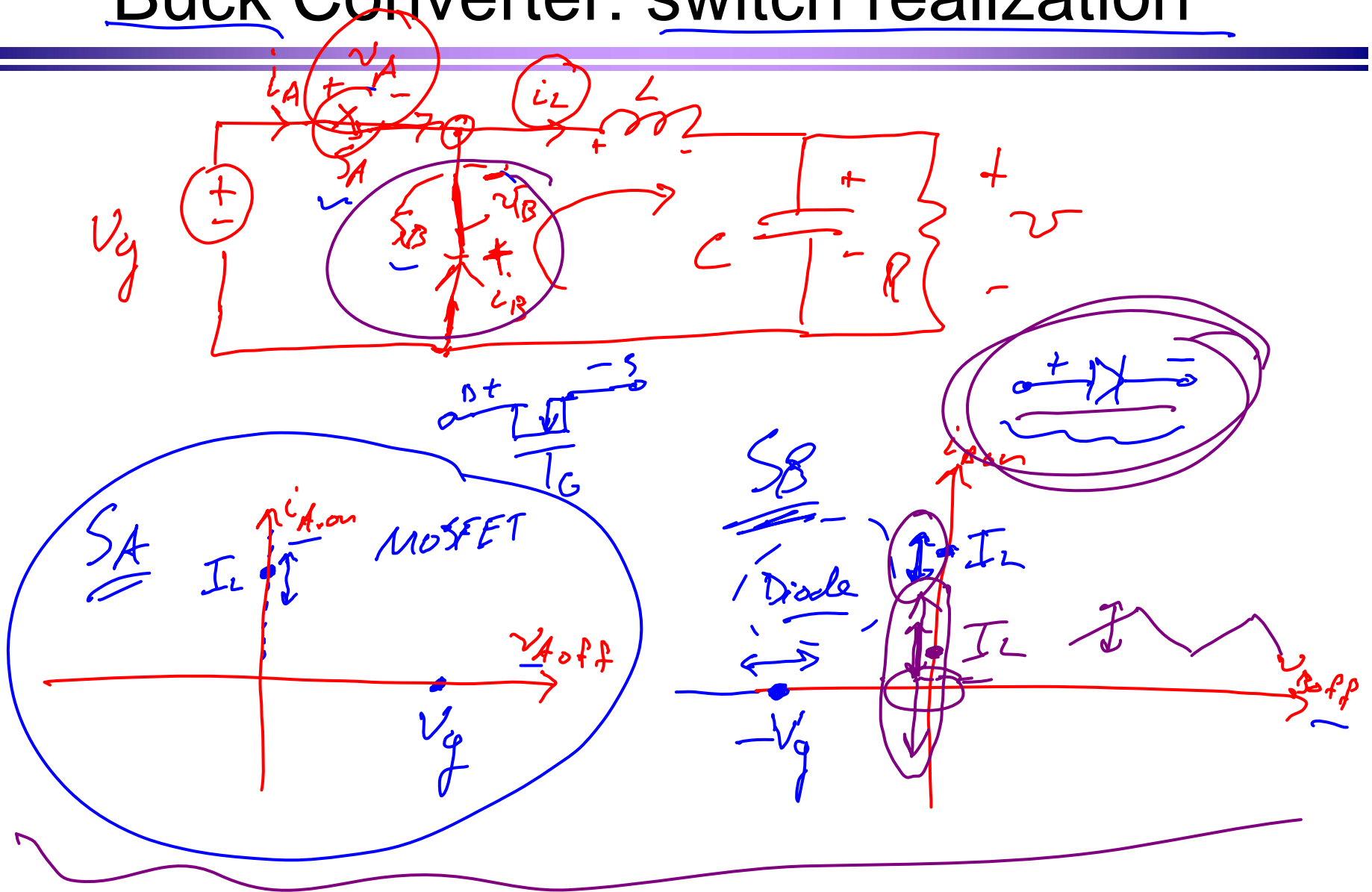

Buck Converter: CCM "ideal"

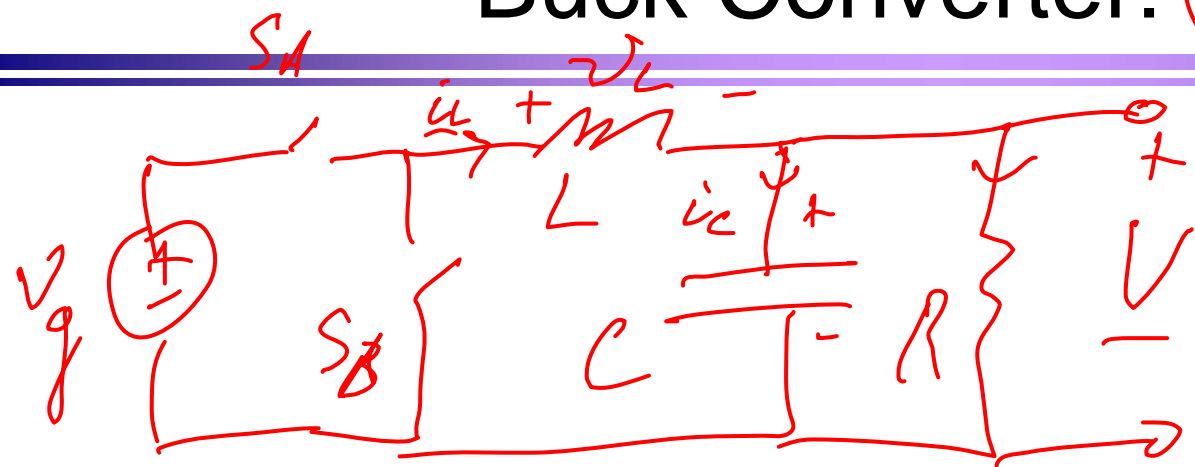

steady state:

$$V = D \cdot V_g$$

$$i_L \approx I_L = \frac{V}{R} = \frac{D V_g}{R}$$




$$D'T_s V = 2 \cdot \Delta i_L$$

$$\Delta i_L = \frac{D \cdot D' T_s V_g}{2L}$$

↑ not f(R)

$$\Delta i_L = \frac{D'T_s V}{2L} = \frac{D D' T_s V_g}{2L}$$

Buck Converter: Inductor current

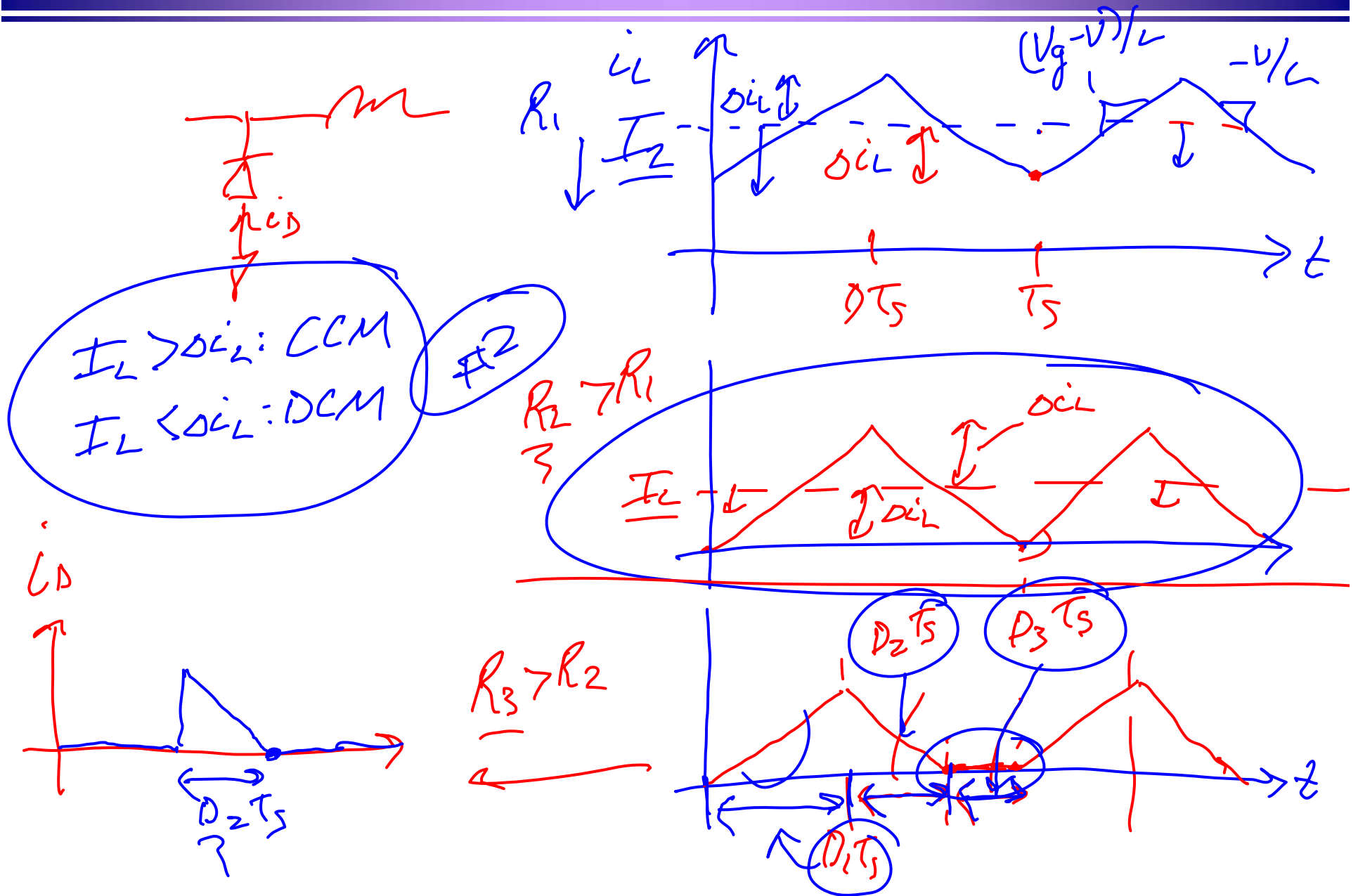

Mode boundary

$$I > \Delta i_L \text{ for CCM} \checkmark$$

$$I < \Delta i_L \text{ for DCM} \checkmark$$

Insert buck converter expressions for I and Δi_L :

$$I_L \quad \frac{DV_g}{R} < \frac{DD'T_s V_g}{2L} \quad \Delta i_L$$

Simplify:

$$L, R, T_s$$

$$\frac{2L}{RT_s} < D' \quad \leftarrow f(\text{CO})$$

This expression is of the form

$$K < K_{crit}(D) \text{ for DCM}$$


where $K = \frac{2L}{RT_s}$ and $K_{crit}(D) = D'$

$$K = \frac{2L}{RT_s}$$


$$K_{crit} = D' = 1 - D \Rightarrow 0 \leq K_{crit} \leq 1$$

K and K_{crit} vs. D

for $K < 1$:

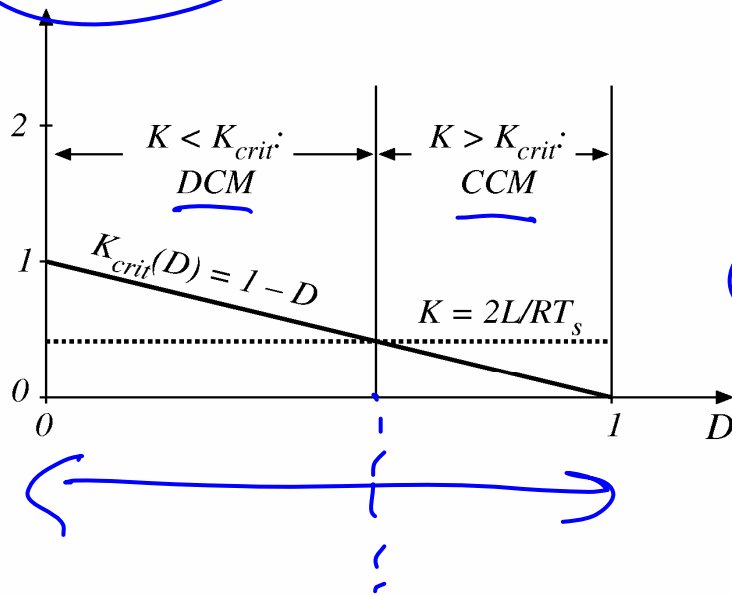

for $K > 1$:

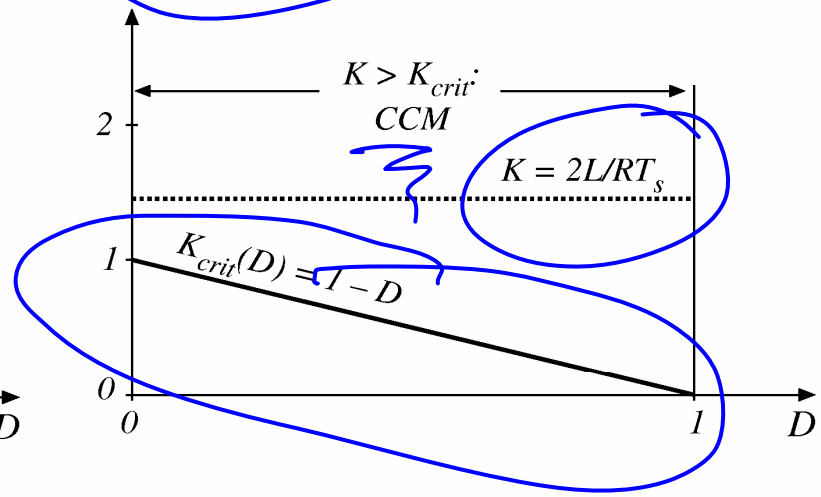

Critical load resistance R_{crit}

Solve K_{crit} equation for load resistance R :

where

$$R < R_{crit}(D) \quad \text{for CCM}$$
$$R > R_{crit}(D) \quad \text{for DCM}$$
$$R_{crit}(D) = \frac{2L}{D'T_s}$$

Book

Summary: mode boundary

$$\begin{array}{l}
 K > K_{crit}(D) \quad \text{or} \quad R < R_{crit}(D) \quad \text{for CCM} \\
 K < K_{crit}(D) \quad \text{or} \quad R > R_{crit}(D) \quad \text{for DCM}
 \end{array}$$

Table 5.1. CCM-DCM mode boundaries for the buck, boost, and buck-boost converters

Converter	$K_{crit}(D)$	$\max_{0 \leq D \leq 1} (K_{crit})$	$R_{crit}(D)$	$\min_{0 \leq D \leq 1} (R_{crit})$
Buck	$(1 - D)$	1	$\frac{2L}{(1 - D)T_s}$	$2 \frac{L}{T_s}$
Boost	$D(1 - D)^2$	$\frac{4}{27}$	$\frac{2L}{D(1 - D)^2 T_s}$	$\frac{27}{2} \frac{L}{T_s}$
Buck-boost	$(1 - D)^2$	1	$\frac{2L}{(1 - D)^2 T_s}$	$2 \frac{L}{T_s}$

$$V/V_g = M(D, R_{on}, R_L, V_o, Q_R, t_{on}, t_s, R) \quad \text{(with } R \text{ circled in red)}$$

5.2. Analysis of the conversion ratio $M(D, K)$


Analysis techniques for the discontinuous conduction mode:

Inductor volt-second balance

$$\langle v_L \rangle = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = 0$$

Capacitor charge balance

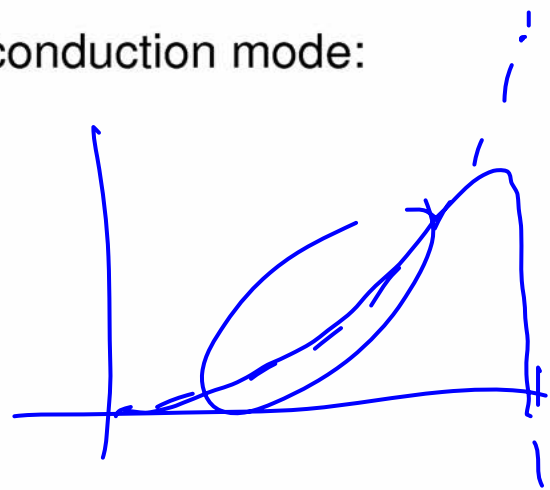
$$\langle i_C \rangle = \frac{1}{T_s} \int_0^{T_s} i_C(t) dt = 0$$



Small ripple approximation sometimes applies:


$$v(t) \approx V \quad \text{because} \quad \Delta v \ll V$$
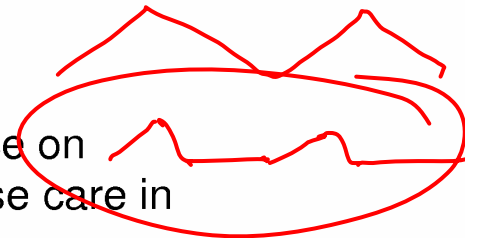
$$i(t) \approx I \quad \text{is a poor approximation when} \quad \Delta i > I$$



Converter steady-state equations obtained via charge balance on each capacitor and volt-second balance on each inductor. Use care in applying small ripple approximation.

Example: Analysis of DCM buck converter $M(D,K)$

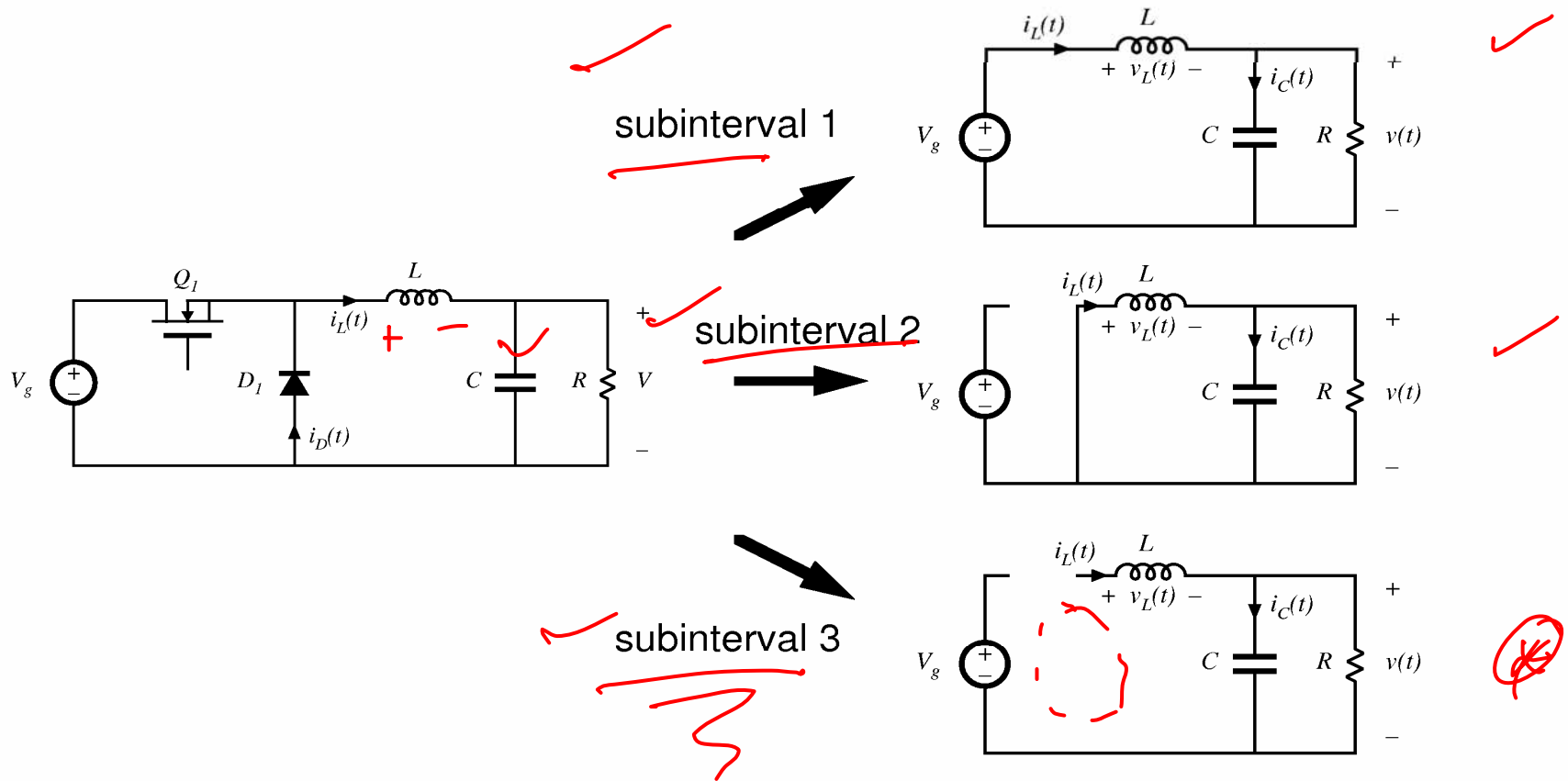

Subinterval 1


DC \approx DC

$$v_L = V_g - v(t)$$

$$v_L \approx V_g - V$$

$$i_C = i_L(t) - v/R$$

$$i_C \approx i_L - v/R$$

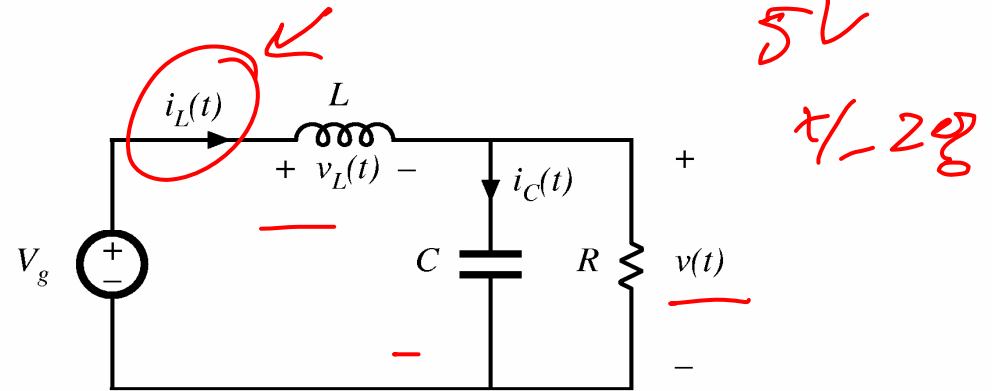


Subinterval 2

$$v_L = -v \approx -V$$

$$i_C = i_L - v/R$$

$$i_C \approx i_L - \frac{v}{R}$$

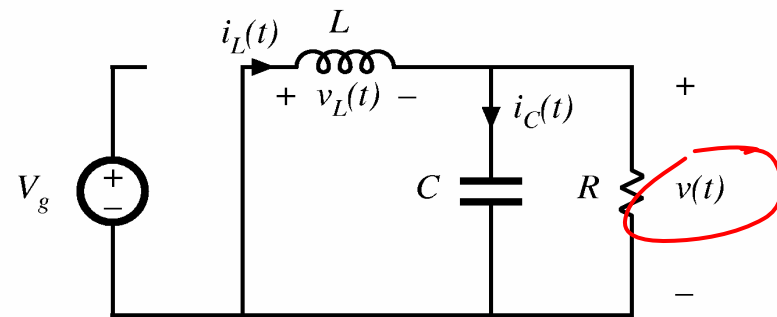


Subinterval 3

$$v_L \rightarrow L \frac{di}{dt}$$


$$v_L = \phi$$

$$i_C = i_L - \frac{v}{R}$$

$$i_C = -\frac{v}{R}$$

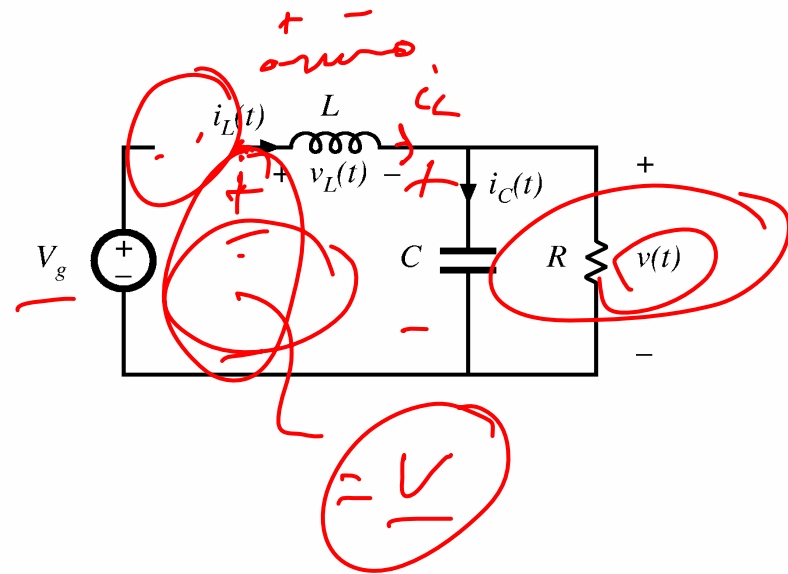

Inductor volt-second balance

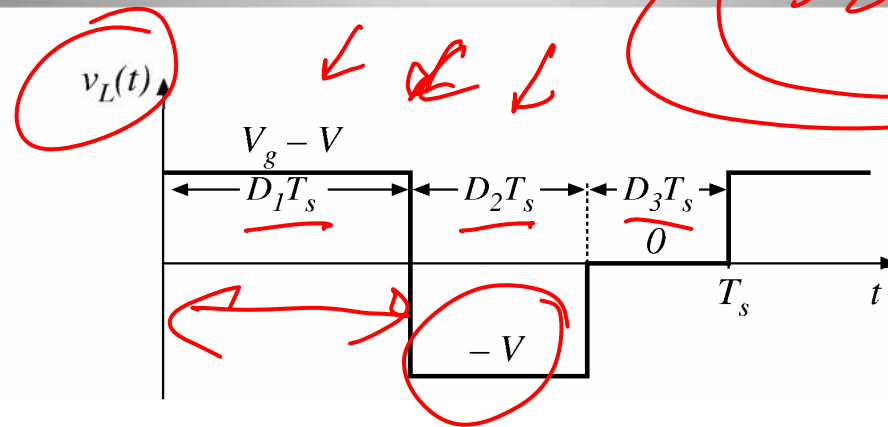

$$D_1 (V_g - V) - D_2 V + D_3 \cdot (0) = 0$$



$$D_1 V_g - (D_1 + D_2) V = 0$$

$$\underline{V = V_g \cdot \frac{D_1}{D_1 + D_2}}$$

Capacitor charge balance

$\langle i_C \rangle = 0$


$\langle i_L \rangle = \frac{V}{R}$

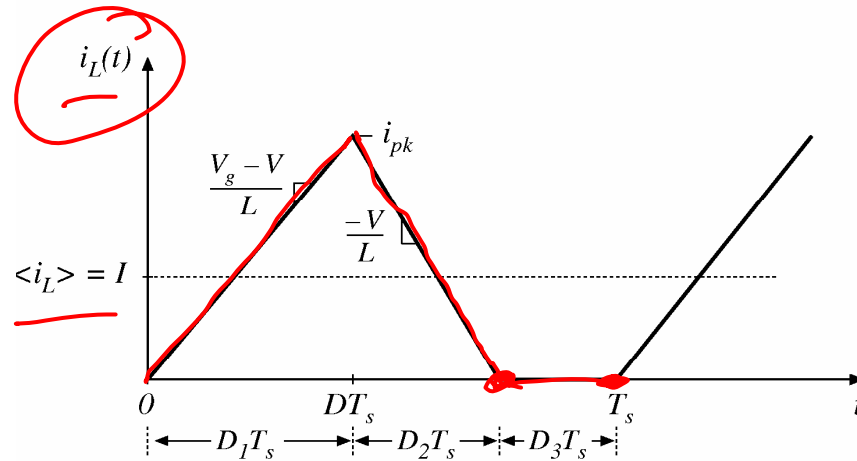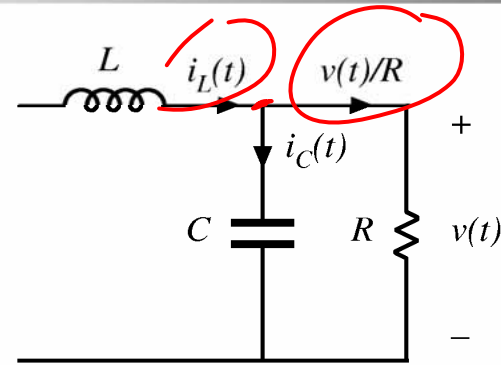

Inductor Current Waveform

$$\langle i_L \rangle = \frac{1}{T_s} \cdot \frac{1}{2} \cdot (D_1 + D_2) T_s \cdot i_{pk}$$
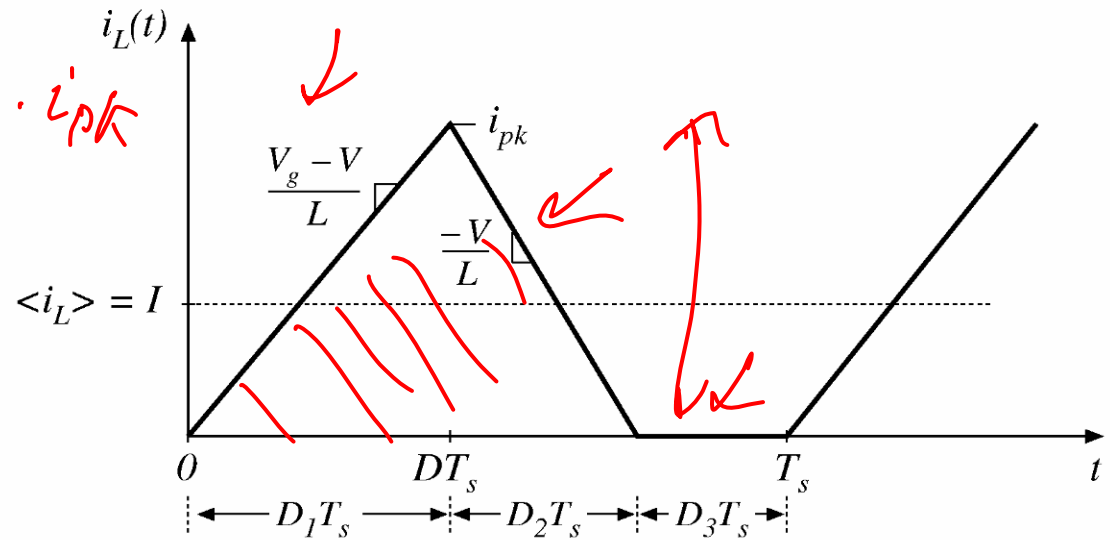
$$i_{pk} = \frac{(V_g - V)}{L} \cdot D_1 T_s$$



$$\langle i_L \rangle = \frac{T_s (D_1 + D_2) (V_g - V) D_1}{2 T_s \cdot L} = \frac{D_1 T_s (D_1 + D_2) (V_g - V)}{2 L} = V/R$$

DCM

Solution for V

Two equations and two unknowns (V and D_2):

✓ $V = V_g \frac{D_1}{D_1 + D_2}$ (from inductor volt-second balance)

✓ $\frac{V}{R} = \frac{D_1 T_s}{2L} (D_1 + D_2) (V_g - V)$ (from capacitor charge balance)

Eliminate D_2 , solve for V :


$$\frac{V}{V_g} = \frac{2}{1 + \sqrt{1 + 4K / D_1^2}}$$

where $K = 2L / RT_s$
valid for $K < K_{crit}$


$$K = \frac{2L}{RT_s}$$

Load dep.!

Buck converter $M(D,K)$

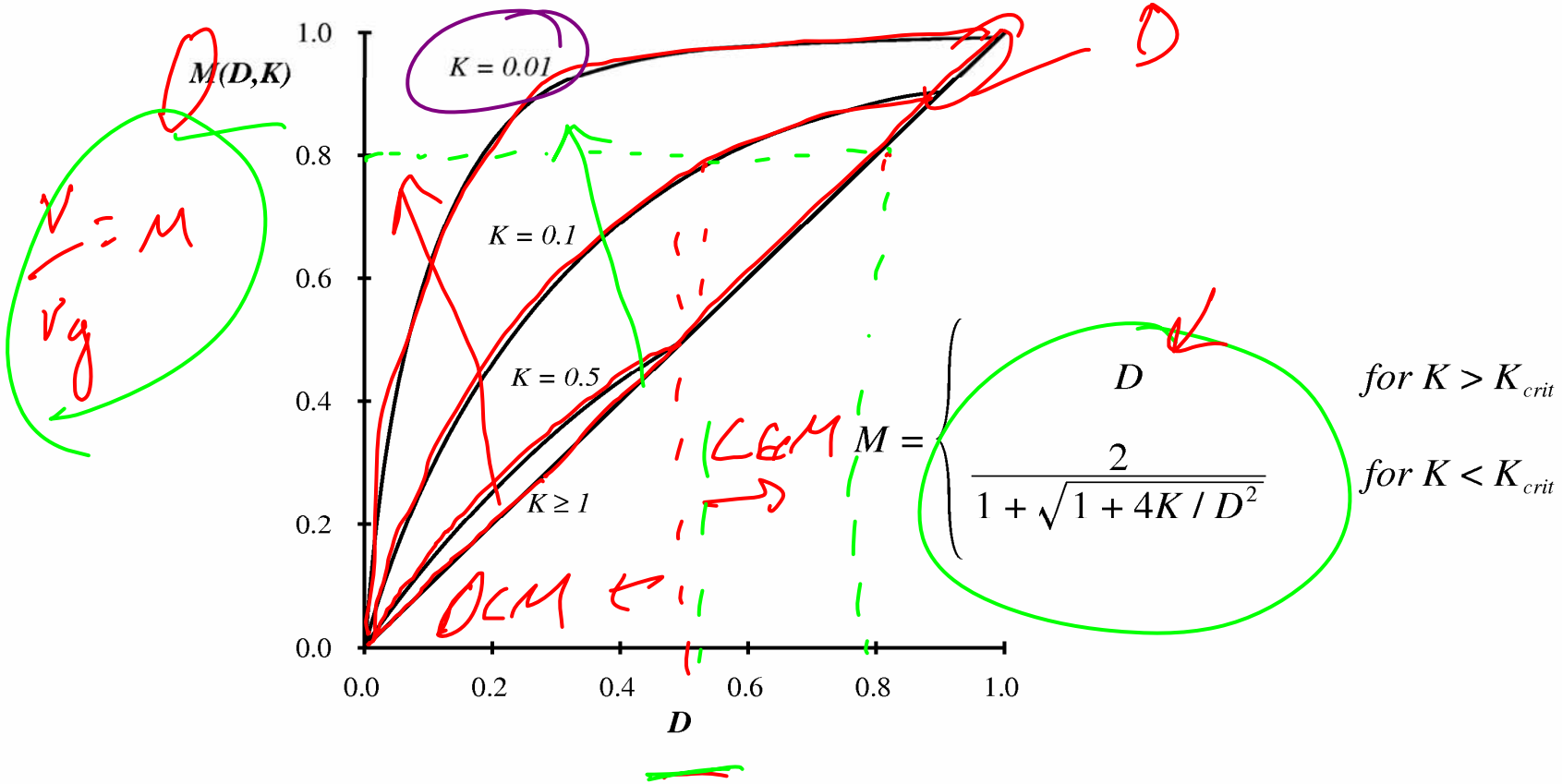

5.3. Boost converter example

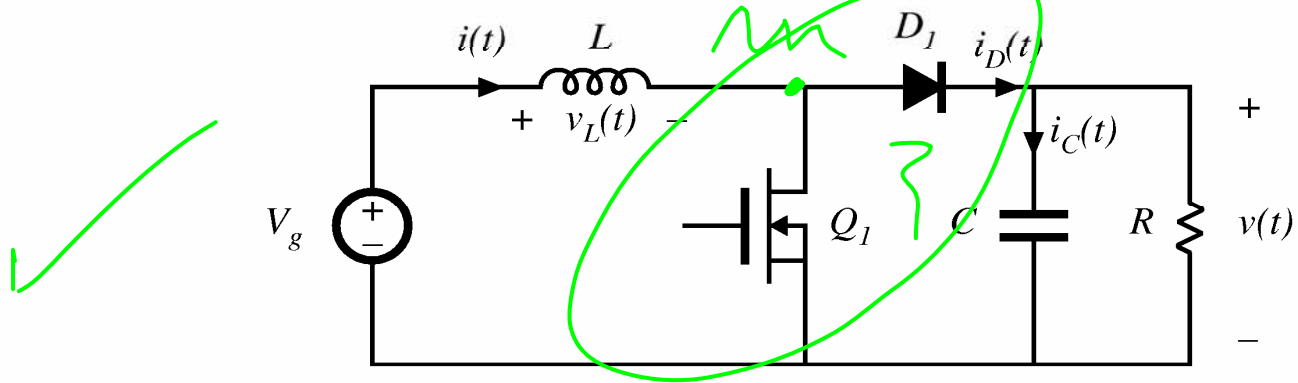

Mode boundary:

$$I > \Delta i_L \text{ for CCM}$$

$$I < \Delta i_L \text{ for DCM}$$

Previous CCM soln:

$$I = \frac{V_g}{D'^2 R} \quad \Delta i_L = \frac{V_g}{2L} DT_s$$