

ECEN 4797/5797

Introduction to Power Electronics

Lecture #18


Monday, October 5, 2009

Ch. 6: Transformer Isolation ✓

(Cont.)

Prof. Regan Zane

The “flyback transformer”

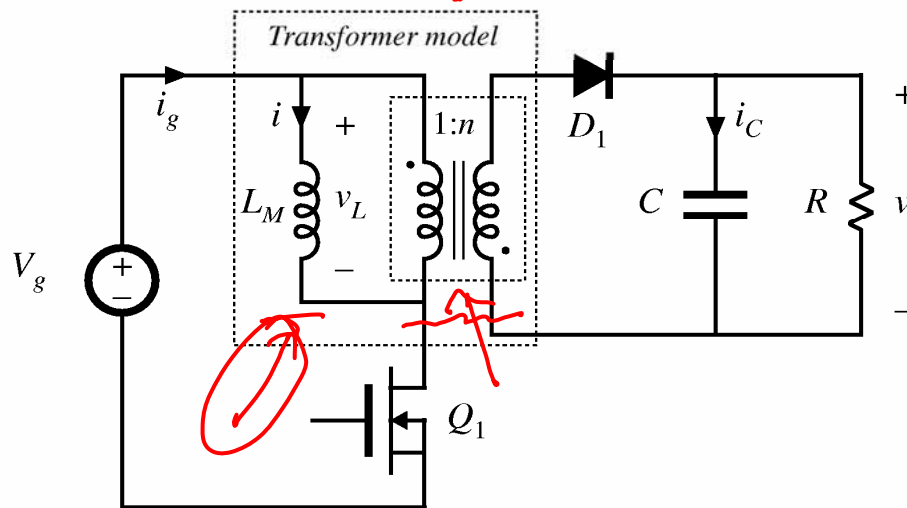

- A two-winding inductor
- Symbol is same as transformer, but function differs significantly from ideal transformer
- Energy is stored in magnetizing inductance
- Magnetizing inductance is relatively small



- Current does not simultaneously flow in primary and secondary windings
- Instantaneous winding voltages follow turns ratio
- Instantaneous (and rms) winding currents do not follow turns ratio
- Model as (small) magnetizing inductance in parallel with ideal transformer

Equivalent circuit model: CCM Flyback

$$\langle v_L \rangle = D(V_g) + D'(-\frac{V}{n}) = 0$$

$$\langle i_C \rangle = D(-\frac{V}{R}) + D'(\frac{I}{n} - \frac{V}{R}) = 0$$
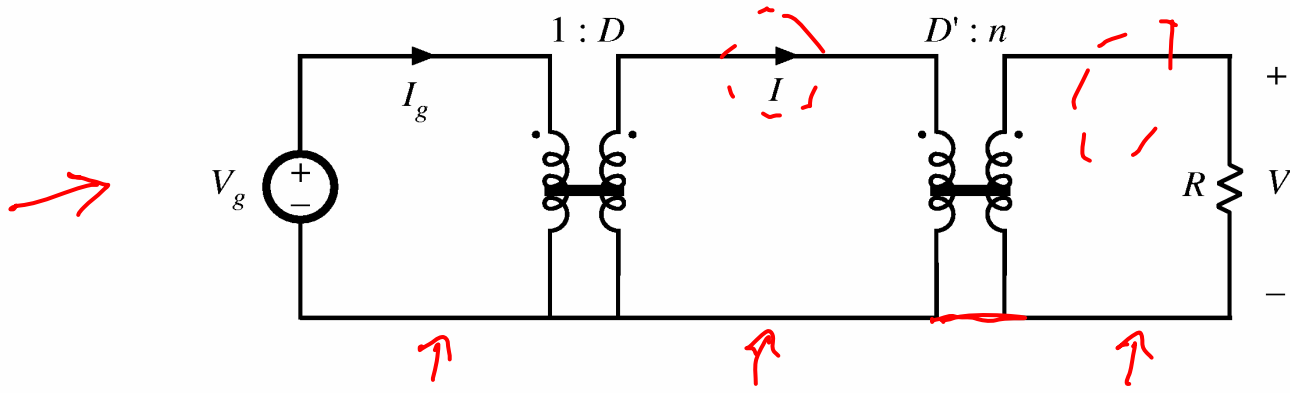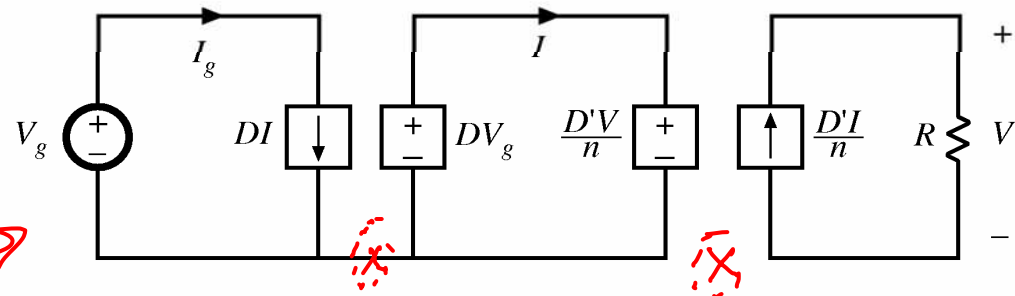
$$I_g = \langle i_g \rangle = D(I) + D'(0)$$




Discussion: Flyback converter

- Widely used in low power and/or high voltage applications
- ⇒ Low parts count → 1 core, 1 diode, 1 FET
- Multiple outputs are easily obtained, with minimum additional parts
- Cross regulation is inferior to buck-derived isolated converters
- ⇒ Often operated in discontinuous conduction mode
- DCM analysis: DCM buck-boost with turns ratio





Fundamentals of Power Electronics

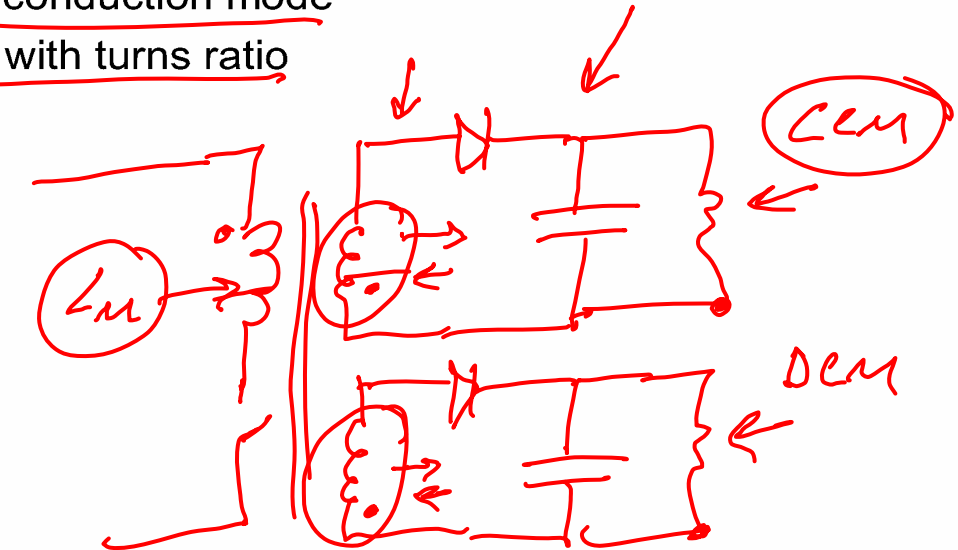

2-Transistor Flyback

→ Text. 6.4 Prob.

$R_1 + R_2$
gate drive

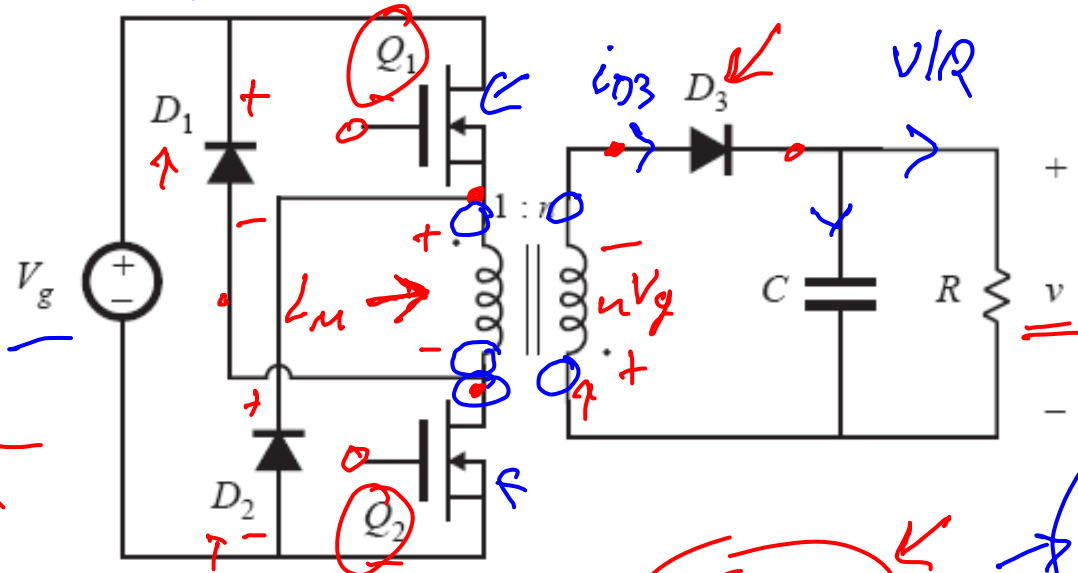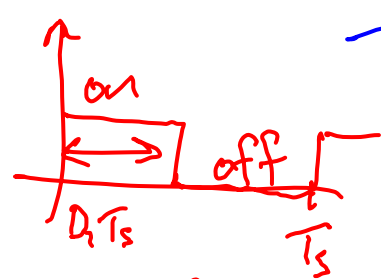


$$\frac{v}{V_g} < n$$





$$\frac{v}{n} < V_g$$

Leakage C
 L_L
Time 1

Time 2

Time 3: D_3 off

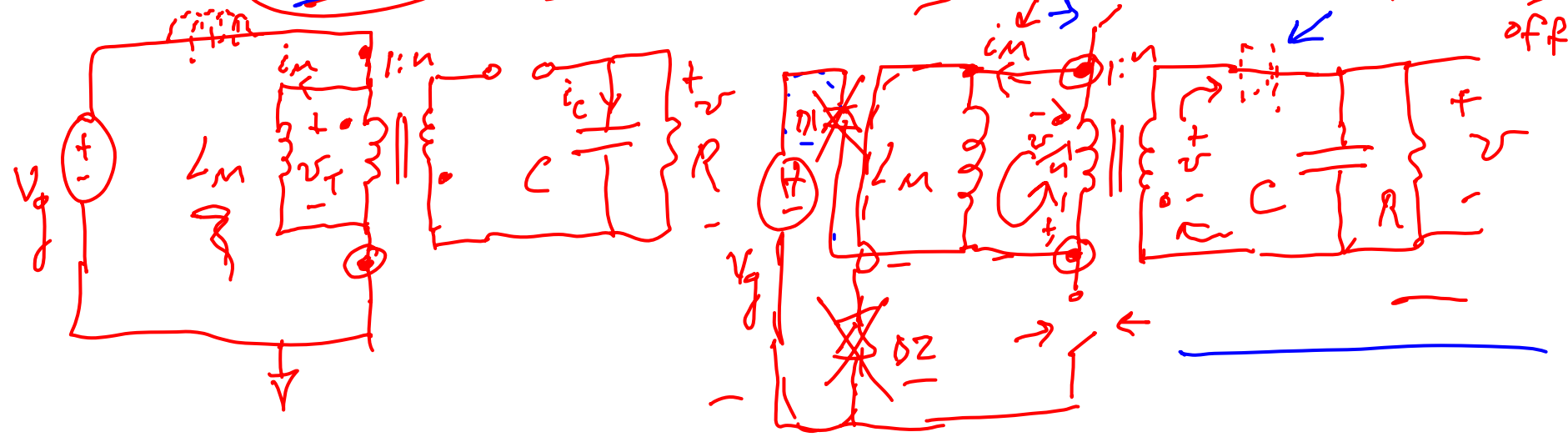

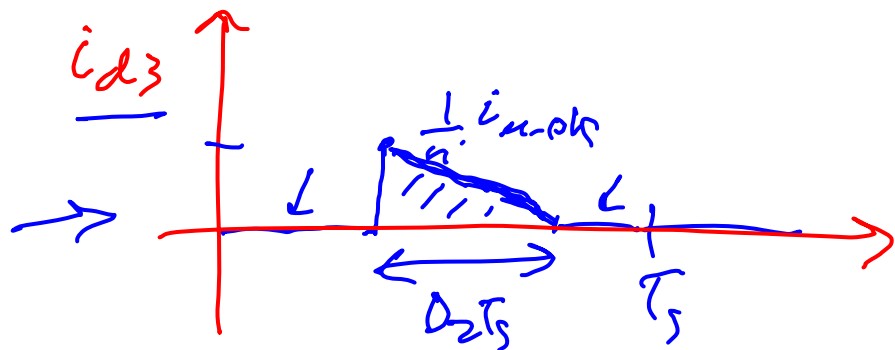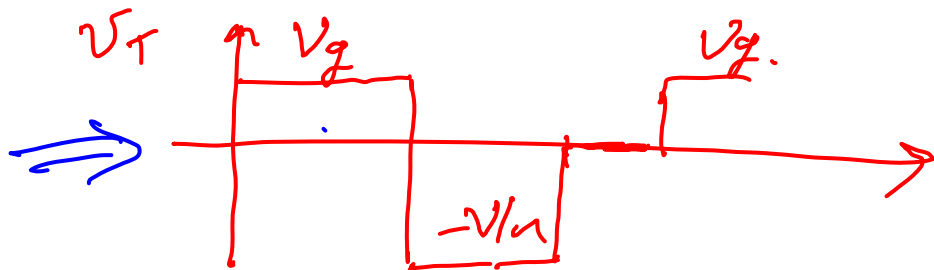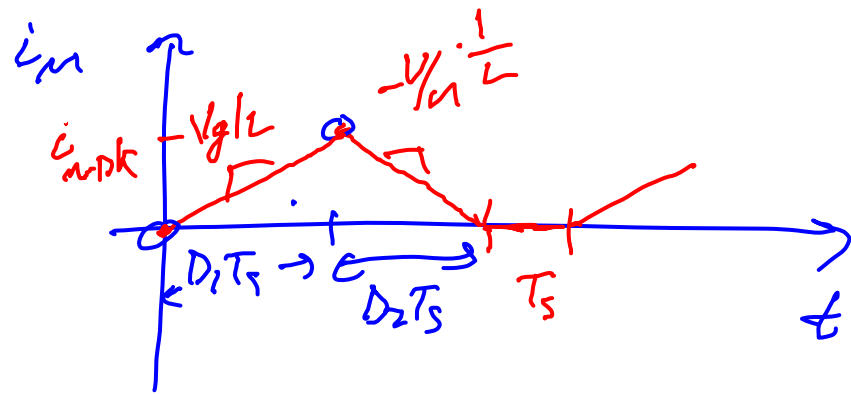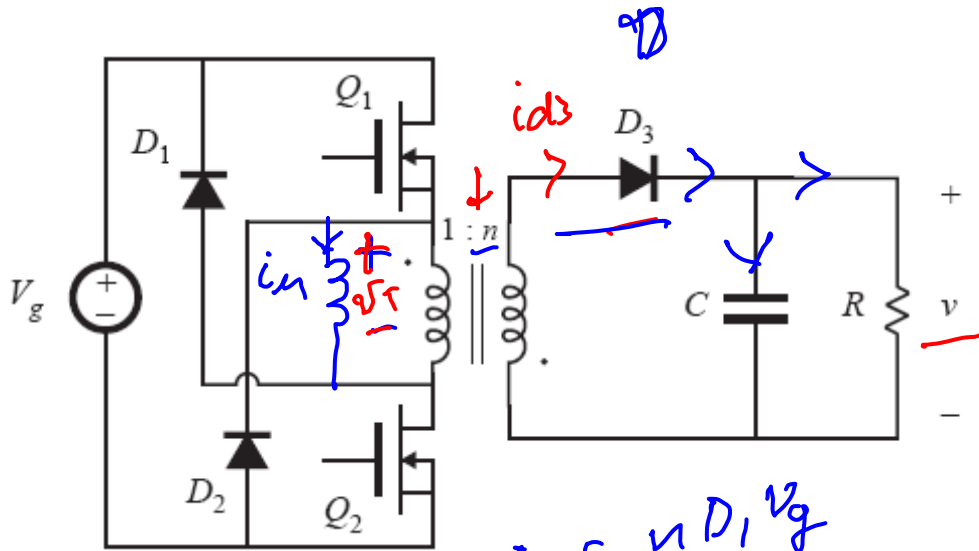


DCM:

$$D_1 V_g - \frac{D_2 V}{n} = 0 \rightarrow \frac{D_2}{n} = \frac{D_1 V_g}{V}$$

$$\begin{aligned} \langle i_{d3} \rangle &= \frac{1}{T_s} \cdot \frac{1}{2} \cdot D_2 \cdot T_s \cdot \frac{i_{inpk}}{n} \\ &= \frac{D_2}{2n} \cdot \frac{D_1 T_s V_g}{L} = \frac{V}{R} \end{aligned}$$
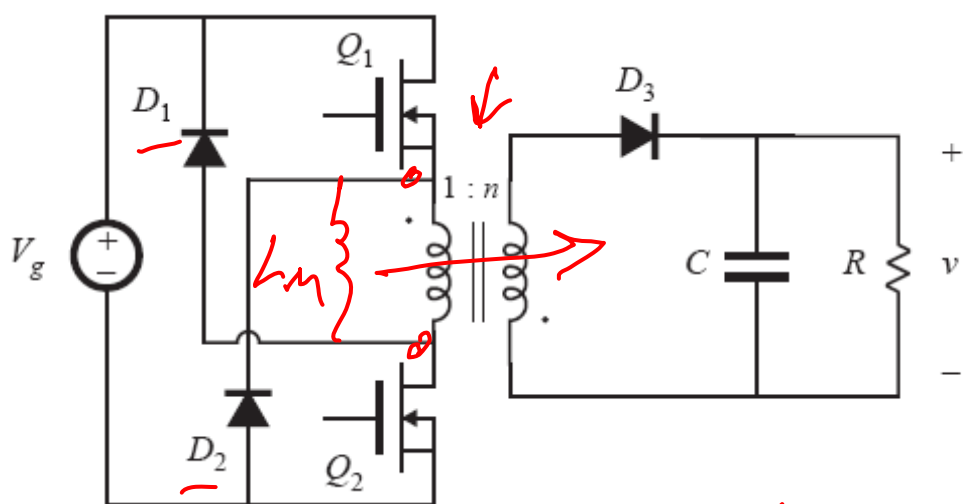
$$\frac{n D_1 V_g}{2L} \cdot \frac{D_2 T_s V_g}{L} = \frac{V}{R}$$



DCM



$$K = \frac{2L}{RT_s} \leftarrow$$

$$\frac{V}{V_g} = D_1 \sqrt{\frac{RT_s}{2L_m}} = n D_1 \sqrt{\frac{RT_s}{2n^2 L_m}} \leftarrow$$

$$\frac{V}{V_g} = n D_1 \cdot \frac{1}{\sqrt{K}} < n$$

$$\frac{V}{V_g} < n \rightarrow D_1 < \sqrt{K}$$

Forward converter w/ active reset (P6.9)

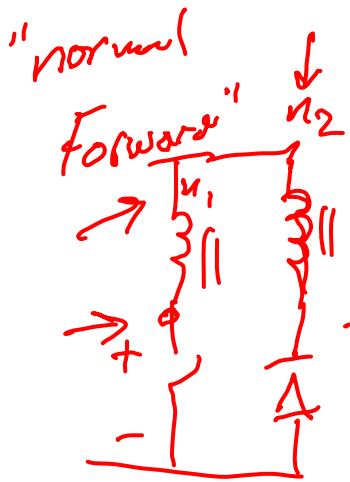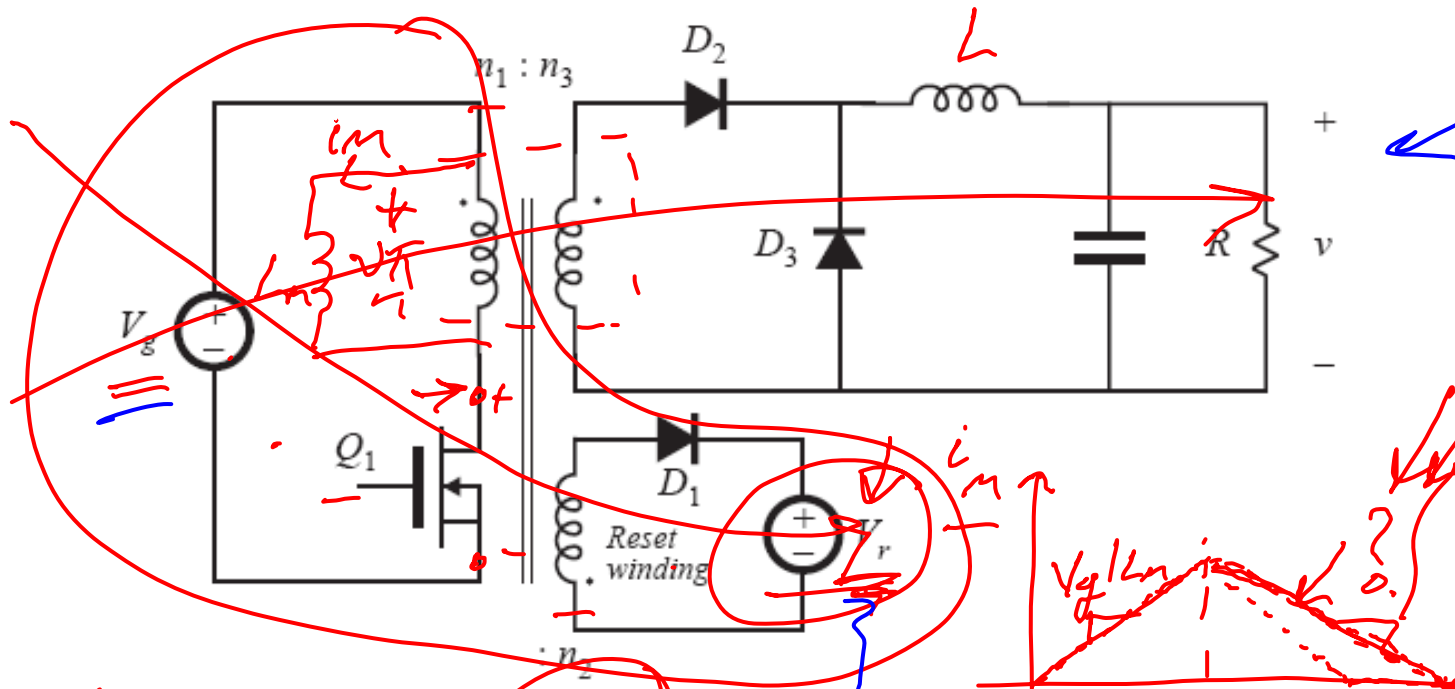

$n_1 = n_2$

$D < 0.5$

$$D V_g - \frac{n_1}{n_2} D' V_r = 0$$

$$V_r = \frac{n_2}{n_1} \frac{D}{D'} V_g$$

