

ECEN 4797/5797

Introduction to Power Electronics

Lecture #22

Wednesday, October 14, 2009


Part II: Converter Dynamics & Control

→ State-Space Averaging

Sections 7.3

Prof. Regan Zane

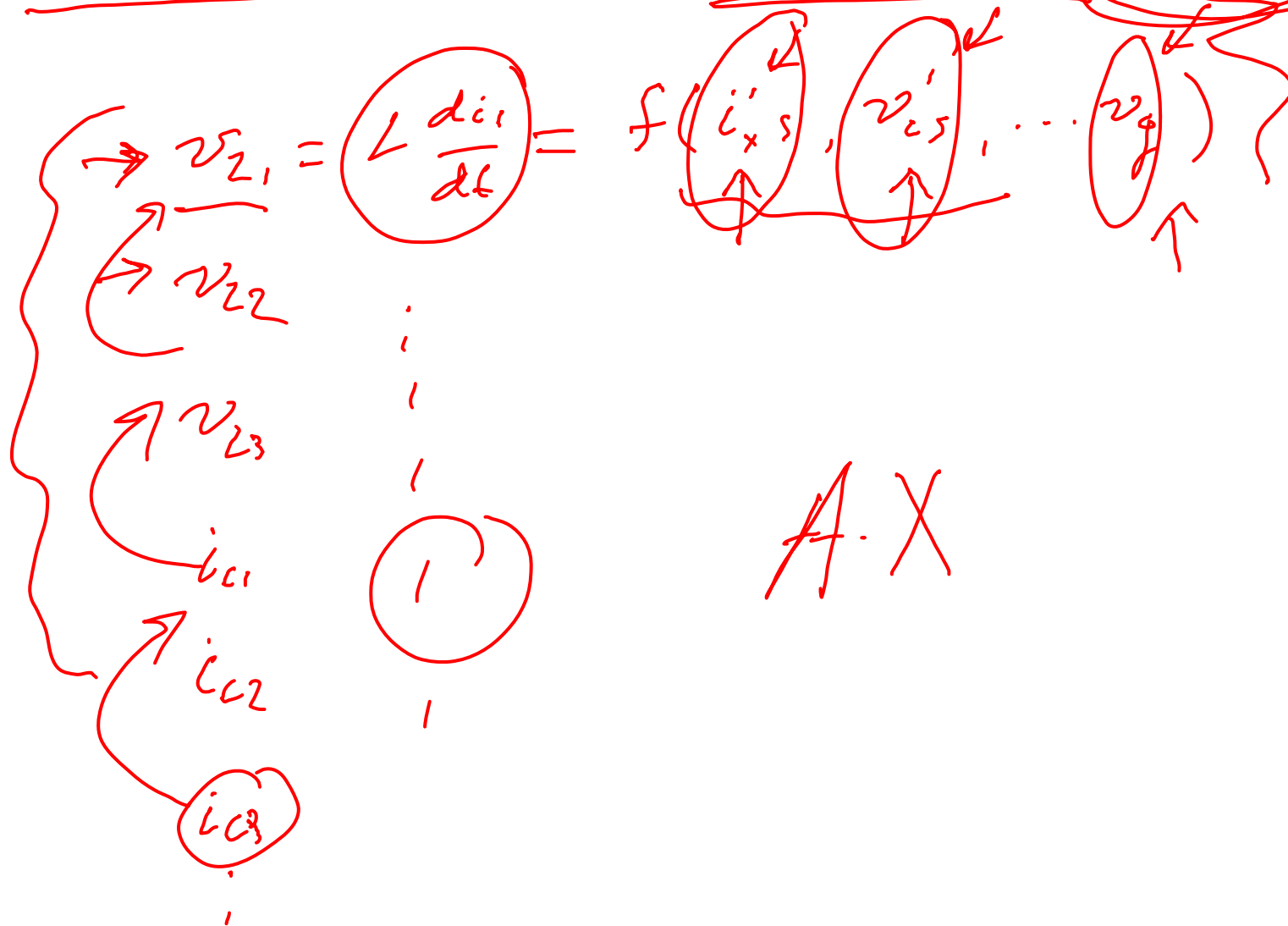System of Equations: State-space matrix form



State equations of a linear system, in matrix form

A canonical matrix form:


$$\underline{\mathbf{K}} \frac{d\mathbf{x}(t)}{dt} = \underline{\mathbf{A}} \mathbf{x}(t) + \underline{\mathbf{B}} \mathbf{u}(t)$$

$$\mathbf{y}(t) = \underline{\mathbf{C}} \mathbf{x}(t) + \underline{\mathbf{E}} \mathbf{u}(t)$$

State vector $\mathbf{x}(t)$ contains inductor currents, capacitor voltages, etc.:

$$\mathbf{x}(t) = \begin{bmatrix} x_1(t) \\ x_2(t) \\ \vdots \end{bmatrix},$$
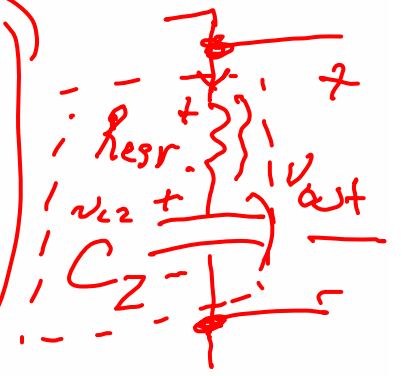
$$\frac{d\mathbf{x}(t)}{dt} = \begin{bmatrix} \frac{dx_1(t)}{dt} \\ \frac{dx_2(t)}{dt} \\ \vdots \end{bmatrix}$$




Input vector $\mathbf{u}(t)$ contains independent sources such as $v_g(t)$

Output vector $\mathbf{y}(t)$ contains other dependent quantities to be computed, such as $i_g(t)$

Matrix \mathbf{K} contains values of capacitance, inductance, and mutual inductance, so that $\mathbf{K} d\mathbf{x}/dt$ is a vector containing capacitor currents and inductor winding voltages. These quantities are expressed as linear combinations of the independent inputs and state variables. The matrices \mathbf{A} , \mathbf{B} , \mathbf{C} , and \mathbf{E} contain the constants of proportionality.

$$K \frac{dx}{dt} = \begin{bmatrix} C_1 & 0 & 0 \\ 0 & C_2 & 0 \\ 0 & 0 & L \end{bmatrix} \cdot \begin{bmatrix} v_1 \\ v_2 \\ i \end{bmatrix} = \begin{bmatrix} C_1 \frac{dv_1}{dt} + 0 + 0 \\ C_2 \frac{dv_2}{dt} \\ L \frac{di}{dt} \end{bmatrix} = \begin{bmatrix} C \frac{dv_1}{dt} \\ \vdots \end{bmatrix}$$

Example

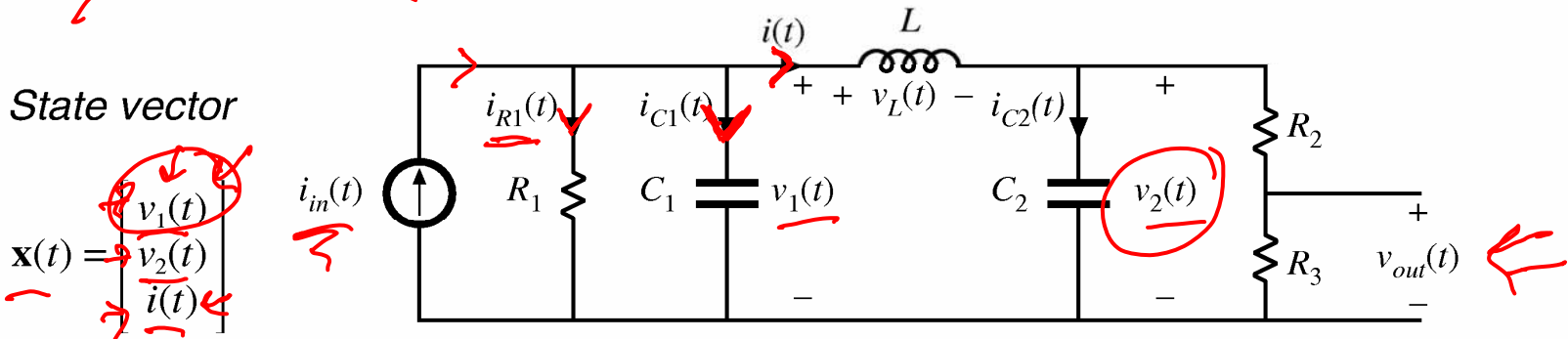

Matrix \mathbf{K}

$$\mathbf{K} = \begin{bmatrix} C_1 & 0 & 0 \\ 0 & C_2 & 0 \\ 0 & 0 & L \end{bmatrix}$$

Input vector

$$\mathbf{u}(t) = \begin{bmatrix} i_{in}(t) \end{bmatrix}$$

Choose output vector as


$$\mathbf{y}(t) = \begin{bmatrix} v_{out}(t) \\ i_{R1}(t) \end{bmatrix}$$

To write the state equations of this circuit, we must express the inductor voltages and capacitor currents as linear combinations of the elements of the $\mathbf{x}(t)$ and $\mathbf{u}(t)$ vectors.

$$K \frac{dx}{dt} = Ax + Bu$$

$$\begin{bmatrix} -\frac{1}{R_1} & 0 & -1 \\ \vdots & \vdots & \vdots \end{bmatrix} i$$

Circuit equations

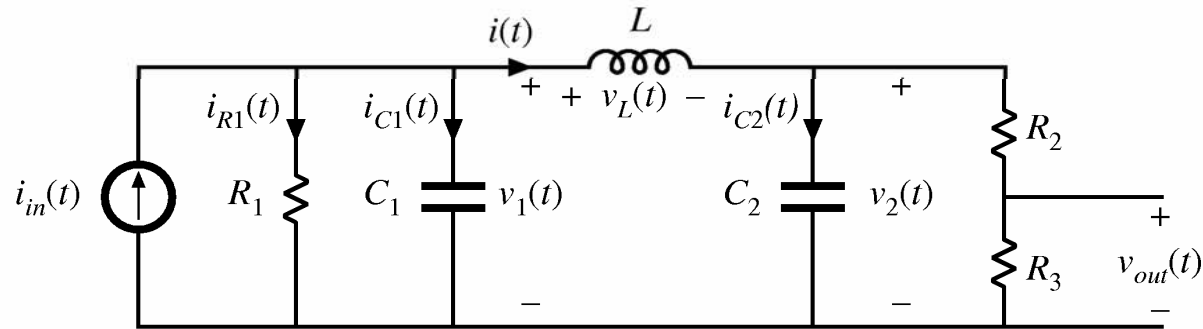

✓ Find $\underline{i_{C1}}$ via node equation:
$$i_{C1}(t) = C_1 \frac{dv_1(t)}{dt} = \underline{i_{in}(t)} - \frac{v_1(t)}{R} - i(t)$$

✓ Find $\underline{i_{C2}}$ via node equation:
$$i_{C2}(t) = C_2 \frac{dv_2(t)}{dt} = i(t) - \frac{v_2(t)}{R_2 + R_3}$$

✓ Find $\underline{v_L}$ via loop equation:
$$v_L(t) = L \frac{di(t)}{dt} = v_1(t) - v_2(t)$$

Equations in matrix form

The same equations:

$$i_{C1}(t) = C_1 \frac{dv_1(t)}{dt} = i_{in}(t) - \frac{v_1(t)}{R} - i(t)$$

$$i_{C2}(t) = C_2 \frac{dv_2(t)}{dt} = i(t) - \frac{v_2(t)}{R_2 + R_3}$$

$$v_L(t) = L \frac{di(t)}{dt} = v_1(t) - v_2(t)$$


Express in matrix form:

$$\underbrace{\begin{bmatrix} \dot{C}_1 & 0 & 0 \\ 0 & C_2 & 0 \\ 0 & 0 & L \end{bmatrix}}_{\mathbf{K}} \underbrace{\begin{bmatrix} \frac{dv_1(t)}{dt} \\ \frac{dv_2(t)}{dt} \\ \frac{di(t)}{dt} \end{bmatrix}}_{\frac{d\mathbf{x}(t)}{dt}} = \underbrace{\begin{bmatrix} -\frac{1}{R_1} & 0 & -1 \\ 0 & -\frac{1}{R_2 + R_3} & 1 \\ 1 & -1 & 0 \end{bmatrix}}_{\mathbf{A}} \underbrace{\begin{bmatrix} v_1(t) \\ v_2(t) \\ i(t) \end{bmatrix}}_{\mathbf{x}(t)} + \underbrace{\begin{bmatrix} 1 \\ 0 \\ 0 \end{bmatrix}}_{\mathbf{B}} \underbrace{[i_{in}(t)]}_{\mathbf{u}(t)}$$

$$\mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A} \mathbf{x}(t) + \mathbf{B} \mathbf{u}(t)$$

Output (dependent signal) equations
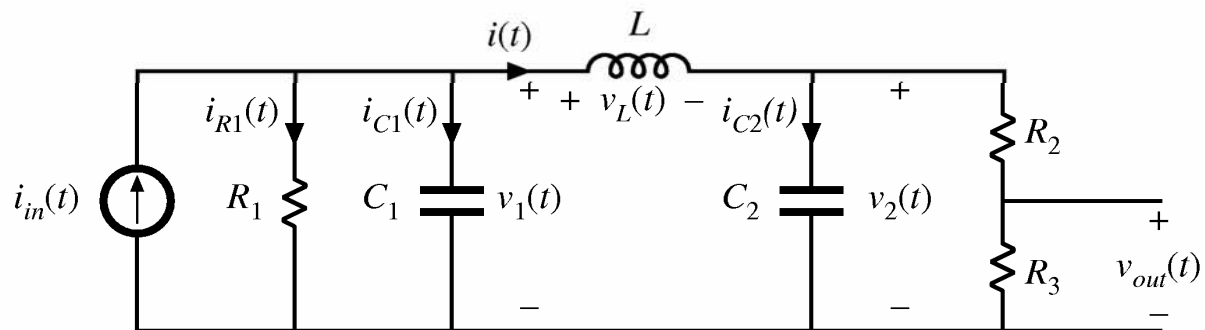
$$\mathbf{y}(t) = \begin{bmatrix} v_{out}(t) \\ i_{R1}(t) \end{bmatrix}$$



Express elements of the vector \mathbf{y} as linear combinations of elements of \mathbf{x} and \mathbf{u} :

$$v_{out}(t) = v_2(t) \frac{R_3}{R_2 + R_3}$$

$$i_{R1}(t) = \frac{v_1(t)}{R_1}$$

Express in matrix form

The same equations:

$$v_{out}(t) = v_2(t) \frac{R_3}{R_2 + R_3}$$

$$i_{R1}(t) = \frac{v_1(t)}{R_1}$$

Express in matrix form:

$$\underbrace{\begin{bmatrix} v_{out}(t) \\ i_{R1}(t) \end{bmatrix}}_{\mathbf{y}(t)} = \underbrace{\begin{bmatrix} 0 & \frac{R_3}{R_2 + R_3} & 0 \\ \frac{1}{R_1} & 0 & 0 \end{bmatrix}}_{\mathbf{C}} \underbrace{\begin{bmatrix} v_1(t) \\ v_2(t) \\ i(t) \end{bmatrix}}_{\mathbf{x}(t)} + \underbrace{\begin{bmatrix} 0 \\ 0 \end{bmatrix}}_{\mathbf{E}} \underbrace{\begin{bmatrix} i_{in}(t) \end{bmatrix}}_{\mathbf{u}(t)}$$

7.3.2 The basic state-space averaged model


Given: a PWM converter, operating in continuous conduction mode, with two subintervals during each switching period.

During subinterval 1, when the switches are in position 1, the converter reduces to a linear circuit that can be described by the following state equations:

$$\begin{aligned} \mathbf{K} \frac{d\mathbf{x}(t)}{dt} &= \mathbf{A}_1 \mathbf{x}(t) + \mathbf{B}_1 \mathbf{u}(t) \\ \mathbf{y}(t) &= \mathbf{C}_1 \mathbf{x}(t) + \mathbf{E}_1 \mathbf{u}(t) \end{aligned}$$

During subinterval 2, when the switches are in position 2, the converter reduces to another linear circuit, that can be described by the following state equations:
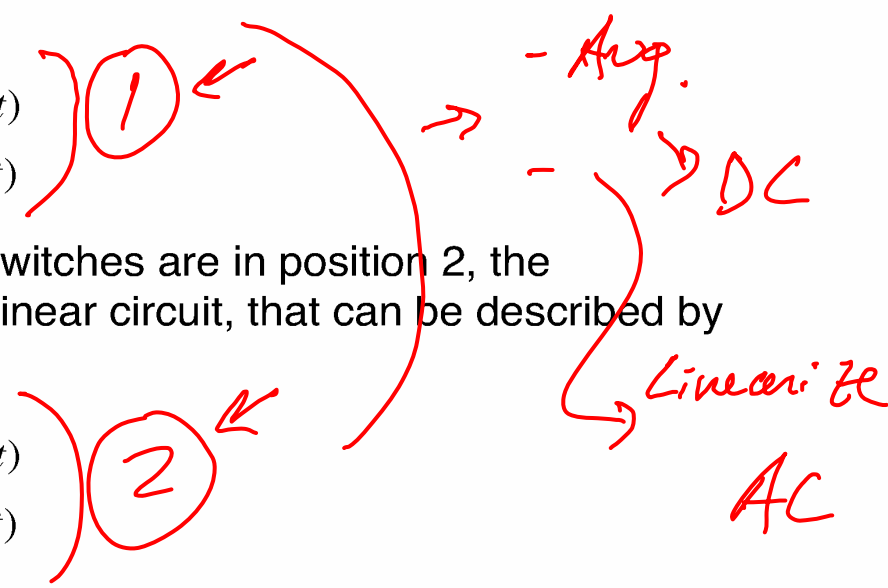
$$\begin{aligned} \mathbf{K} \frac{d\mathbf{x}(t)}{dt} &= \mathbf{A}_2 \mathbf{x}(t) + \mathbf{B}_2 \mathbf{u}(t) \\ \mathbf{y}(t) &= \mathbf{C}_2 \mathbf{x}(t) + \mathbf{E}_2 \mathbf{u}(t) \end{aligned}$$



$$1) \rightarrow \begin{cases} \mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_1 \mathbf{x}(t) + \mathbf{B}_1 \mathbf{u}(t) \\ \mathbf{y}(t) = \mathbf{C}_1 \mathbf{x}(t) + \mathbf{E}_1 \mathbf{u}(t) \end{cases}$$

$$2) \rightarrow \begin{cases} \mathbf{K} \frac{d\mathbf{x}(t)}{dt} = \mathbf{A}_2 \mathbf{x}(t) + \mathbf{B}_2 \mathbf{u}(t) \\ \mathbf{y}(t) = \mathbf{C}_2 \mathbf{x}(t) + \mathbf{E}_2 \mathbf{u}(t) \end{cases}$$

Aug-nonlineari:

$$\left\{ \begin{aligned} \mathbf{K} \frac{d\langle \mathbf{x} \rangle}{dt} &= \mathbf{A}(t) \cdot \langle \mathbf{x} \rangle + \mathbf{B}(t) \langle \mathbf{u} \rangle \\ \langle \mathbf{y} \rangle &= \mathbf{C}(t) \langle \mathbf{x} \rangle + \mathbf{E}(t) \langle \mathbf{u} \rangle \end{aligned} \right.$$

$$\mathbf{A}(t) = \frac{d(t) \cdot \mathbf{A}_1 + d'(t) \mathbf{A}_2}{\vdots \quad \quad \quad \vdots}$$

DC:

$$0 = \overbrace{\mathbf{A} \mathbf{X} + \mathbf{B} \mathbf{U}}^{d(t)=D} \rightarrow \mathbf{Y} = \mathbf{C} \mathbf{X} + \mathbf{E} \mathbf{U}$$


$$\mathbf{X} = -\mathbf{A}^{-1} \mathbf{B} \mathbf{U}$$

$$\mathbf{Y} = (-\mathbf{C} \mathbf{A}^{-1} \mathbf{B} + \mathbf{E}) \mathbf{U}$$

AC:

$$\begin{aligned} \mathbf{K} \frac{d\hat{\mathbf{x}}}{dt} &= \mathbf{A} \hat{\mathbf{x}} + \mathbf{B} \hat{\mathbf{u}} + ((\mathbf{A}_1 - \mathbf{A}_2) \mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2) \mathbf{U}) \cdot \hat{d} \\ \hat{\mathbf{y}} &= \mathbf{C} \hat{\mathbf{x}} + \mathbf{E} \hat{\mathbf{u}} + ((\mathbf{C}_1 - \mathbf{C}_2) \mathbf{X} + (\mathbf{E}_1 - \mathbf{E}_2) \mathbf{U}) \hat{d} \end{aligned}$$

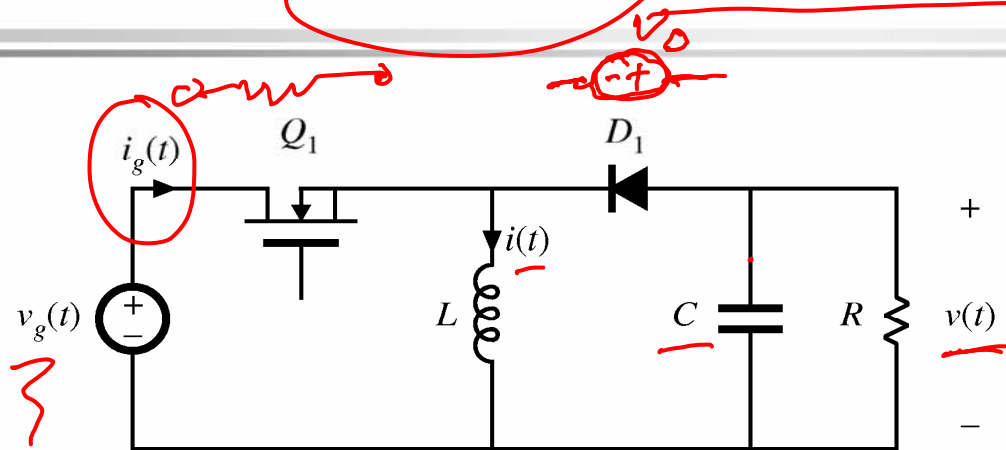7.3.4 Example: State-space averaging of a nonideal buck-boost converter



Model nonidealities:

- MOSFET on-resistance R_{on}
- Diode forward voltage drop V_D

state vector

$$\mathbf{x}(t) = \begin{bmatrix} i(t) \\ v(t) \end{bmatrix}$$

input vector

$$\mathbf{u}(t) = \begin{bmatrix} v_g(t) \\ V_D \end{bmatrix}$$

output vector


$$\mathbf{y}(t) = [i_g(t)]$$

Interval #1

$$\rightarrow v_L = v_g - i_L R_{on}$$

$$i_C = -v/R$$

$$i_g = i_L$$

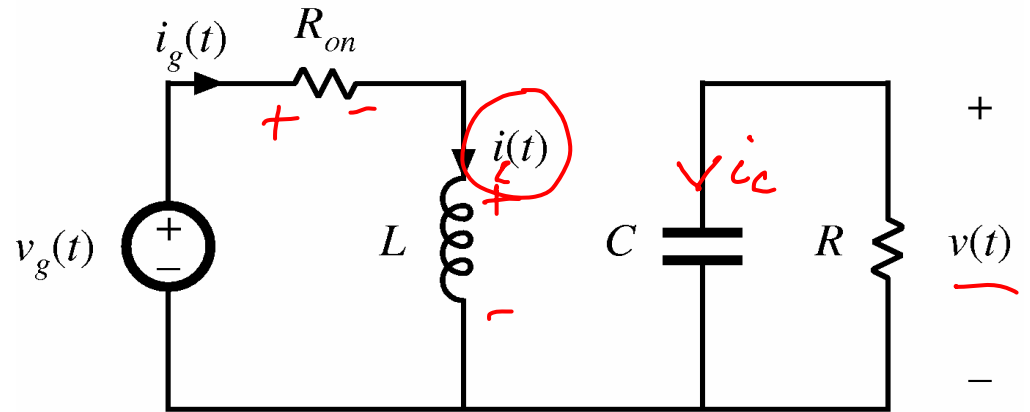

$$\begin{bmatrix} v_L \\ i_C \end{bmatrix} = \begin{bmatrix} L \frac{di_L}{dt} \\ C \frac{dv}{dt} \end{bmatrix} = \begin{bmatrix} -R_{on} & 0 \\ 0 & -\frac{1}{R} \end{bmatrix} \begin{bmatrix} i_L \\ v \end{bmatrix} + \begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_g \\ v_s \end{bmatrix}$$

A_1 B_1


$$\begin{bmatrix} i_g \end{bmatrix} = \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v \end{bmatrix} + \begin{bmatrix} 0 & 0 \end{bmatrix} \begin{bmatrix} v_g \\ v_s \end{bmatrix}$$

#2

$$v_c = v - V_D$$

$$i_c = -i_2 - v/R$$

$$i_g = 0$$

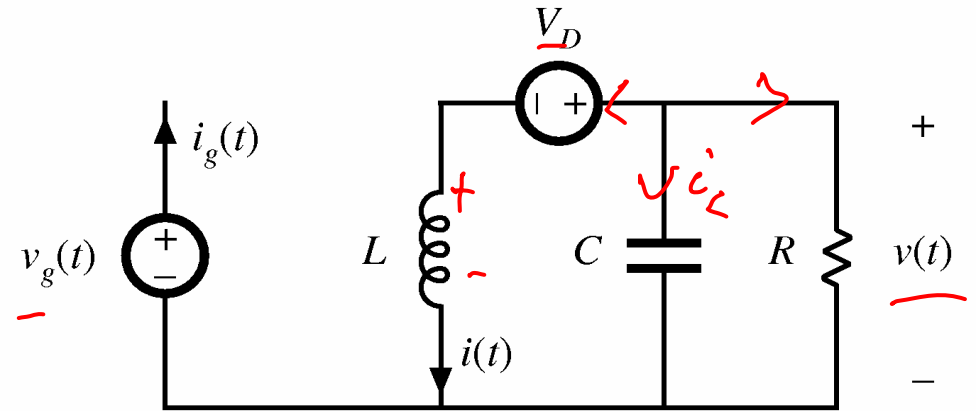

$$A_2 = \begin{bmatrix} 0 & 1 \\ -1 & -1/R \end{bmatrix}$$

$$B_2 = \begin{bmatrix} 0 & -1 \\ 0 & 0 \end{bmatrix}$$

$$C_2 = \begin{bmatrix} 0 & 0 \end{bmatrix}$$

~~$$E_2 = 0$$~~

$$\underbrace{\begin{bmatrix} -R_{on} & 0 \\ 0 & -\frac{1}{R} \end{bmatrix}}_{\mathbf{A}_1} \quad \underbrace{\begin{bmatrix} 0 & 1 \\ -1 & -\frac{1}{R} \end{bmatrix}}_{\mathbf{A}_2} \quad \left. \vphantom{\begin{bmatrix} -R_{on} & 0 \\ 0 & -\frac{1}{R} \end{bmatrix}} \right\} \mathbf{A} = \begin{bmatrix} -DR_{on} & D' \\ -D' & \frac{1}{R} \end{bmatrix}, \quad \mathbf{A}_1 - \mathbf{A}_2 = \begin{bmatrix} -R_{on} & -1 \\ 1 & 0 \end{bmatrix}$$

$$\underbrace{\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix}}_{\mathbf{B}_1} \quad \underbrace{\begin{bmatrix} 0 & -1 \\ 0 & 0 \end{bmatrix}}_{\mathbf{B}_2} \quad \left. \vphantom{\begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix}} \right) \mathbf{B} = \begin{bmatrix} D & -D' \\ 0 & 0 \end{bmatrix} \dots$$

$$\underbrace{\begin{bmatrix} 1 & 0 \end{bmatrix}}_{\mathbf{C}_1} \quad \underbrace{\begin{bmatrix} 0 & 0 \end{bmatrix}}_{\mathbf{C}_2} \quad \left. \vphantom{\begin{bmatrix} 1 & 0 \end{bmatrix}} \right) \mathbf{C} = \begin{bmatrix} D & 0 \end{bmatrix} \dots$$

DC state equations

$$\begin{aligned} \mathbf{0} &= \mathbf{A} \mathbf{X} + \mathbf{B} \mathbf{U} \\ \mathbf{Y} &= \mathbf{C} \mathbf{X} + \mathbf{E} \mathbf{U} \end{aligned}$$

or,

$$\begin{bmatrix} 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -DR_{on} & D' \\ -D' & -\frac{1}{R} \end{bmatrix} \begin{bmatrix} I \\ V \end{bmatrix} + \begin{bmatrix} D & -D' \\ 0 & 0 \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix}$$

$$[I_g] = [D \ 0] \begin{bmatrix} I \\ V \end{bmatrix} + [0 \ 0] \begin{bmatrix} V_g \\ V_D \end{bmatrix}$$

DC solution:

$$\begin{bmatrix} I \\ V \end{bmatrix} = \left(\frac{1}{1 + \frac{D}{D'^2} \frac{R_{on}}{R}} \right) \begin{bmatrix} \frac{D}{D'^2 R} & \frac{1}{D' R} \\ -\frac{D}{D'} & 1 \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix}$$

$$[I_g] = \left(\frac{1}{1 + \frac{D}{D'^2} \frac{R_{on}}{R}} \right) \begin{bmatrix} \frac{D^2}{D'^2 R} & \frac{D}{D' R} \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix}$$

Steady-state equivalent circuit

DC state equations:

$$\begin{aligned} \rightarrow \begin{bmatrix} 0 \\ 0 \end{bmatrix} &= \begin{bmatrix} -DR_{on} & D' \\ -D' & -\frac{1}{R} \end{bmatrix} \begin{bmatrix} I \\ V \end{bmatrix} + \begin{bmatrix} D & -D' \\ 0 & 0 \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix} \\ \rightarrow I_g &= \begin{bmatrix} D & 0 \\ \cancel{D'} & \cancel{-\frac{1}{R}} \end{bmatrix} \begin{bmatrix} I \\ V \end{bmatrix} + \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} V_g \\ V_D \end{bmatrix} \end{aligned}$$

Corresponding equivalent circuit:



$$\mathbf{A} = \begin{bmatrix} -DR_{on} & -D' \\ -D' & -1/R \end{bmatrix}, \mathbf{B} = \begin{bmatrix} D & -D' \\ 0 & 0 \end{bmatrix}, \mathbf{C} = [D \quad 0]$$

$$\mathbf{A}_1 - \mathbf{A}_2 = \begin{bmatrix} -R_{on} & -1 \\ 1 & 0 \end{bmatrix}, \mathbf{B}_1 - \mathbf{B}_2 = \begin{bmatrix} 1 & 1 \\ 0 & 0 \end{bmatrix}, \mathbf{C}_1 - \mathbf{C}_2 = [1 \quad 0]$$

$$\mathbf{K} \frac{d\hat{\mathbf{x}}(t)}{dt} = \mathbf{A} \hat{\mathbf{x}}(t) + \mathbf{B} \hat{\mathbf{u}}(t) + \left\{ (\mathbf{A}_1 - \mathbf{A}_2) \mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2) \mathbf{U} \right\} \hat{d}(t)$$

$$\hat{\mathbf{y}}(t) = \mathbf{C} \hat{\mathbf{x}}(t) + \mathbf{E} \hat{\mathbf{u}}(t) + \left\{ (\mathbf{C}_1 - \mathbf{C}_2) \mathbf{X} + (\mathbf{E}_1 - \mathbf{E}_2) \mathbf{U} \right\} \hat{d}(t)$$

$$\begin{bmatrix} L \frac{d\hat{u}}{dt} \\ C \frac{d\hat{v}}{dt} \end{bmatrix} = \begin{bmatrix} -DR_{on} & -D' \\ -D' & -1/R \end{bmatrix} \begin{bmatrix} \hat{u} \\ \hat{v} \end{bmatrix}$$

Small-signal ac equivalent circuit

$$\begin{bmatrix} L \frac{d\hat{i}_L}{dt} \\ C \frac{d\hat{v}}{dt} \end{bmatrix} = \begin{bmatrix} -DR_{on} & D' \\ -D' & -\frac{1}{R} \end{bmatrix} \begin{bmatrix} \hat{i}_L \\ \hat{v} \end{bmatrix} + \begin{bmatrix} D & -D' \\ 0 & 0 \end{bmatrix} \begin{bmatrix} \hat{v}_g \\ \hat{v}_D \end{bmatrix} + \begin{bmatrix} V_g + V_D - I_L R_{on} - V \\ I_L \end{bmatrix} \hat{d}$$

$$\hat{i}_g = \begin{bmatrix} D & 0 \end{bmatrix} \begin{bmatrix} \hat{i}_L \\ \hat{v} \end{bmatrix} + I_L \hat{d}$$

