

ECEN 4797/5797

Introduction to Power Electronics

Lecture #27

Monday, October 26, 2009

Converter Small-signal Transfer Functions

“algebra on the graph”

Sections 8.2 to 8.4

Prof. Regan Zane

Graphical approach: Series RC




$Z(s) \rightarrow$

$$Z(s) = R + \frac{1}{sC}$$

$$\|Z(j\omega)\| = \left\| R + \frac{1}{j\omega C} \right\|$$

high freq.
↓
R


low freq.
↗
 $\frac{1}{\omega C}$

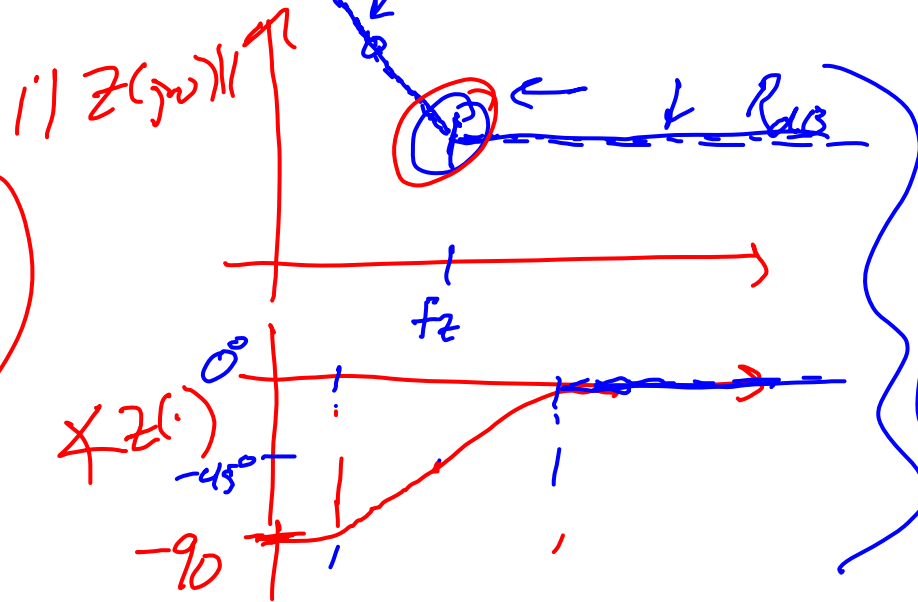

$$\omega_c \frac{1}{RC}$$

$$Z(s) = R \cdot \left(1 + \frac{\omega_c}{s} \right)$$

Graphical approach: Series RL

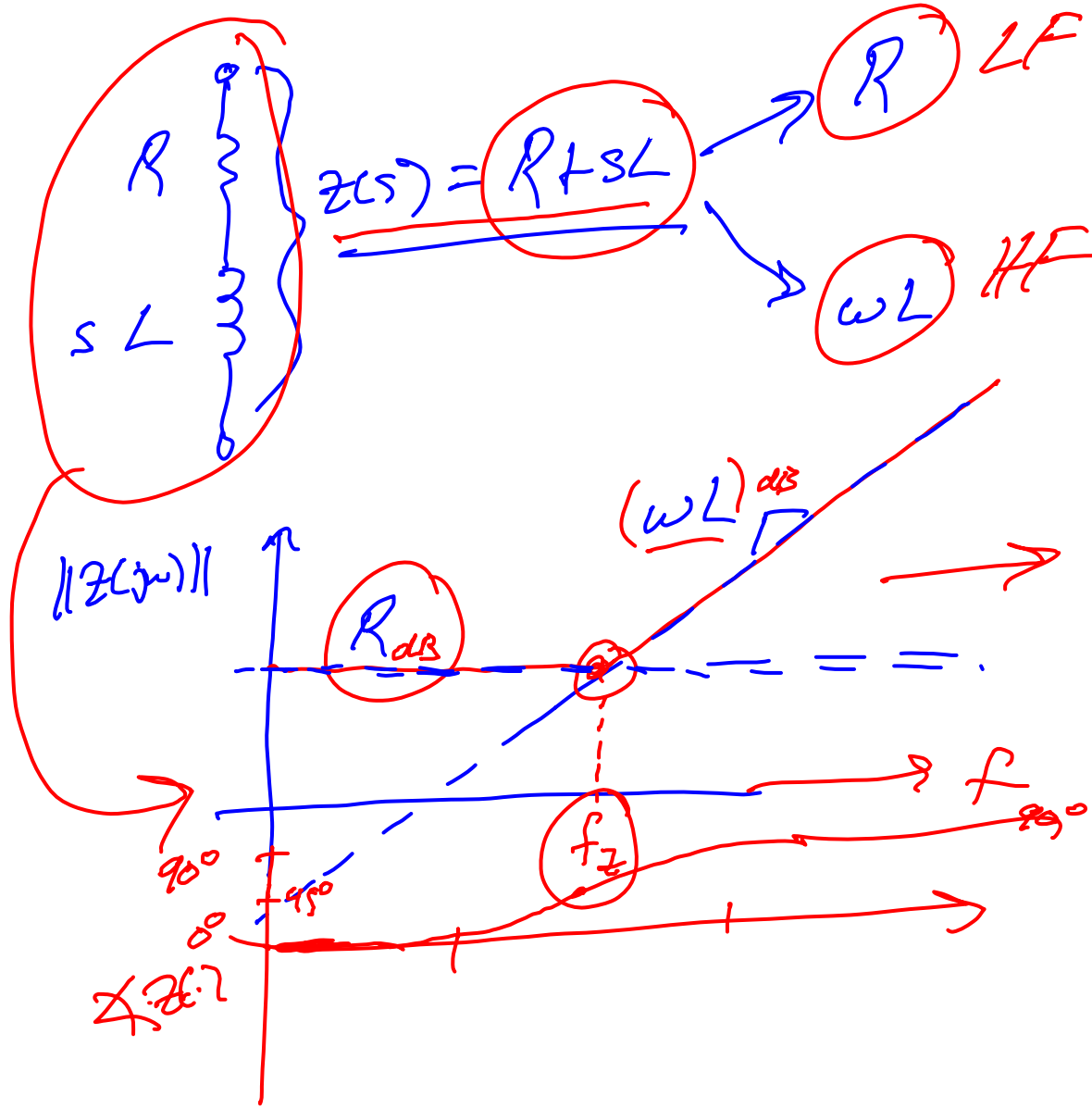


$$z(s) = R \left(1 + \frac{s}{\omega_z} \right)$$

find ω_z :

$$R = \omega_z L$$


$$\omega_z = R/L = 2\pi f_z$$

Series RLC: well damped

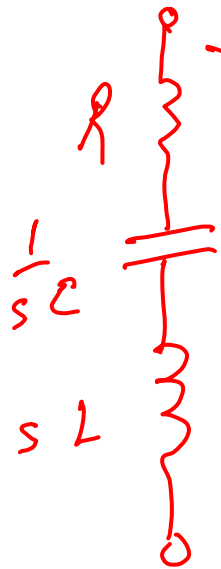

$$Z(s) = R + \frac{1}{sC} + sL$$

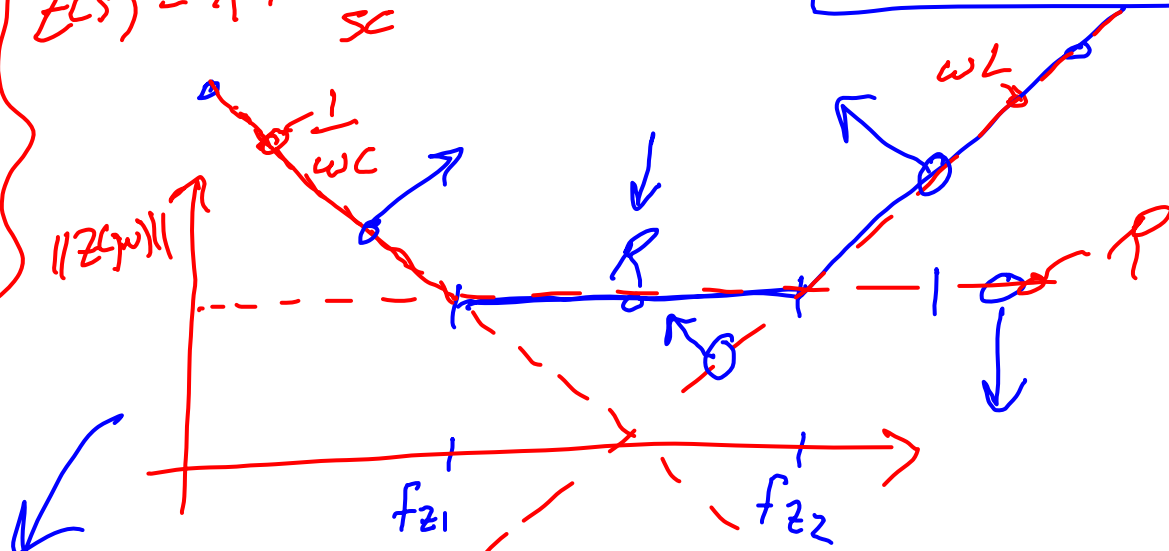
$$f_{z1} = \frac{1}{2\pi RC}$$
$$f_{z2} = \frac{1}{2\pi} \cdot \frac{R}{L}$$



$$Z(s) = R \cdot \left(1 + \frac{\omega_{z1}}{s}\right) \left(1 + \frac{s}{\omega_{z2}}\right)$$

RLC \rightarrow well damped. $R=100m\Omega$

Impedance graph paper

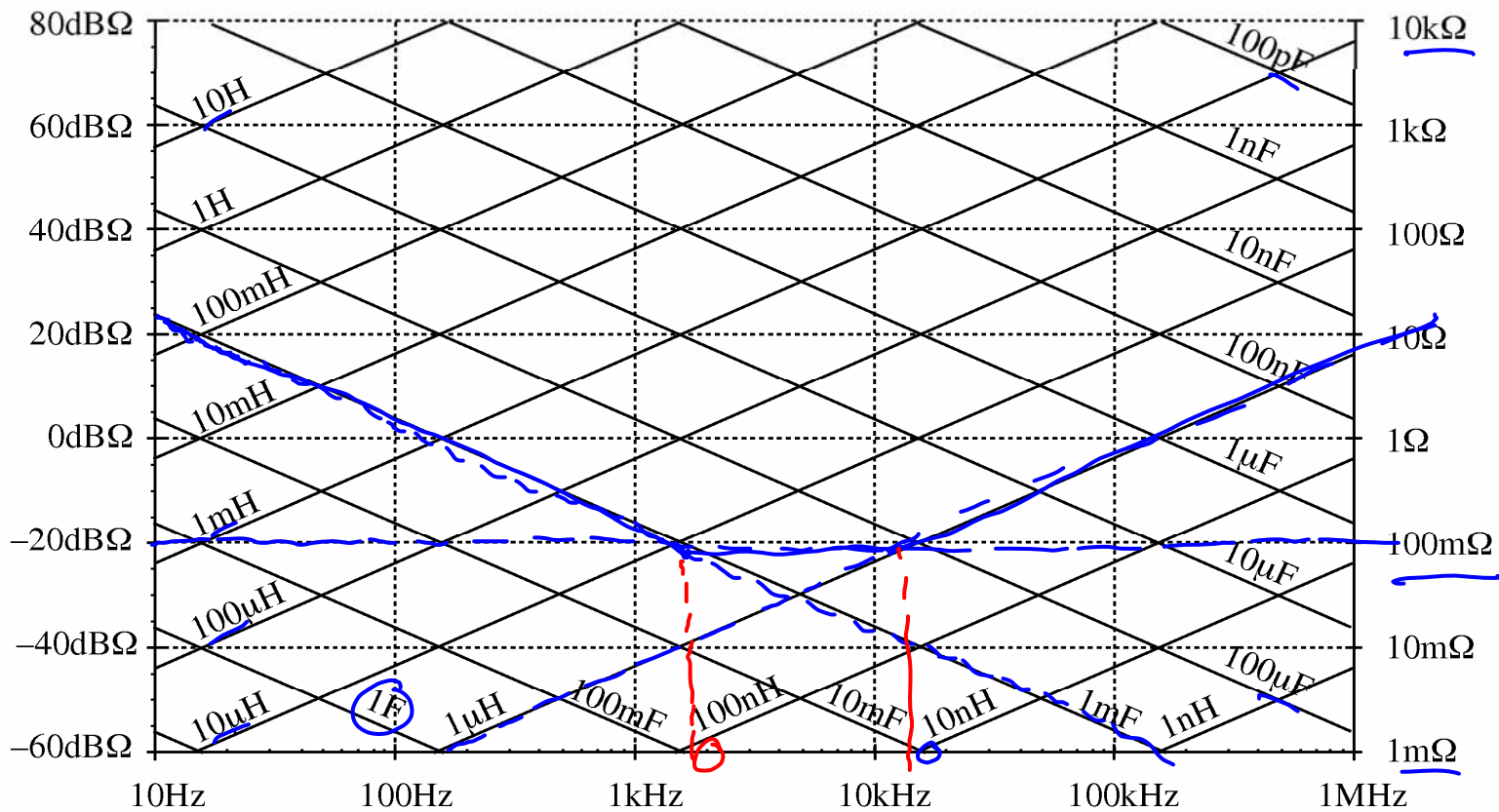


Series RLC: Resonant

$$\frac{1}{\sqrt{LC}} = \sqrt{\frac{L}{C}}$$

$$\left\| \frac{1}{\omega_0 C} \right\| = R_0 = \|\omega_0 L\|$$

$$Z(s) = R + j\omega L + \frac{1}{j\omega C}$$
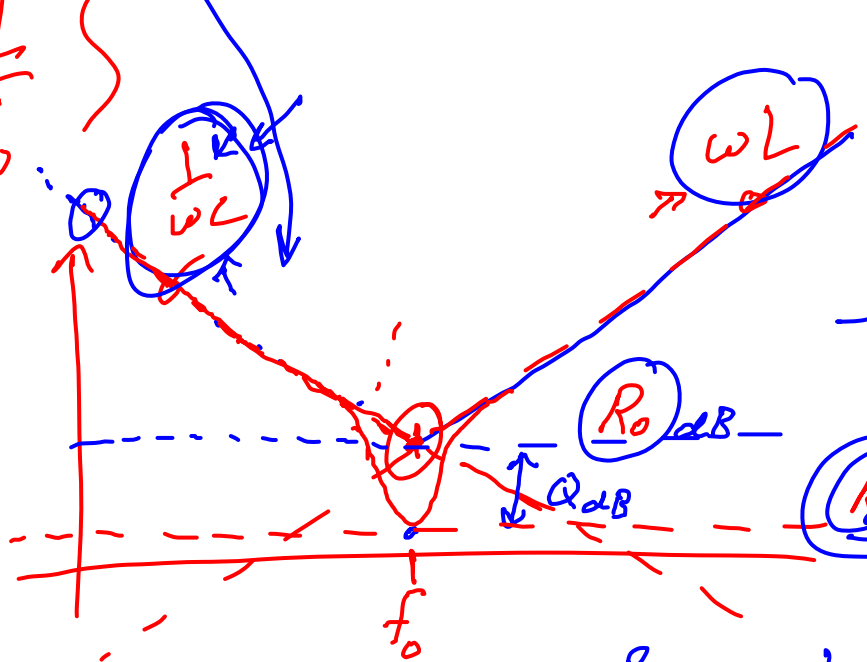
$$= R + \underline{jR_0} + \frac{R_0}{\underline{jR_0}} = R + jR_0 - jR_0 = R$$



$$Z(s) = \frac{1}{sC} \cdot \frac{1 + \frac{s}{\omega_0 Q} + \left(\frac{s}{\omega_0}\right)^2}{1}$$




$$\omega_0: \frac{1}{\omega_0 C} = \omega_0 L$$

$$\omega_0 \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} = 2\pi f_0$$


$$Q = \frac{R_0}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Series Transfer Functions
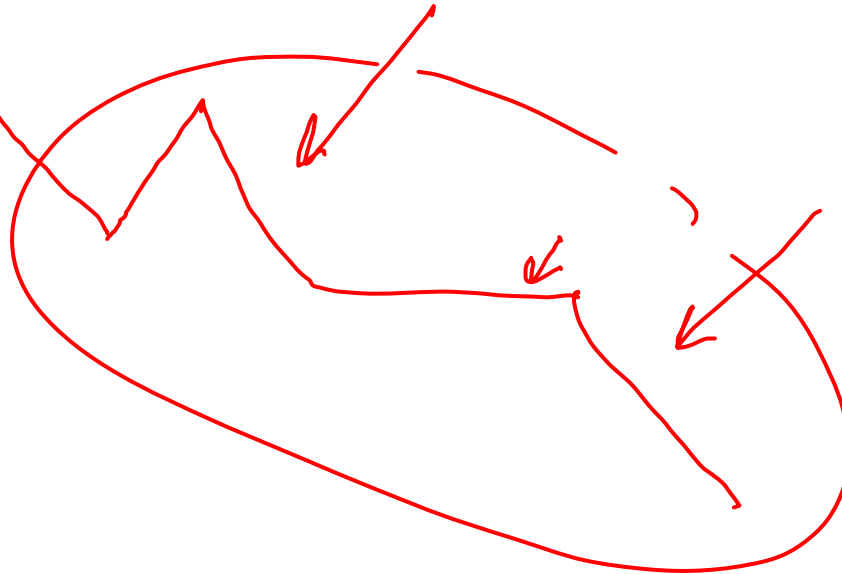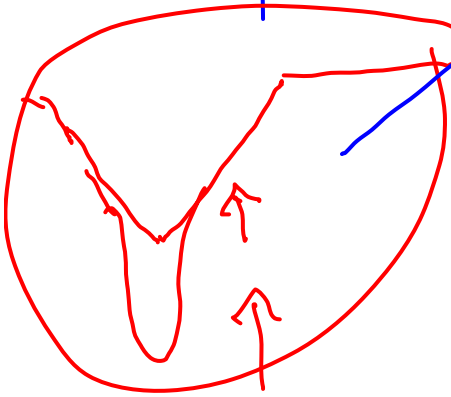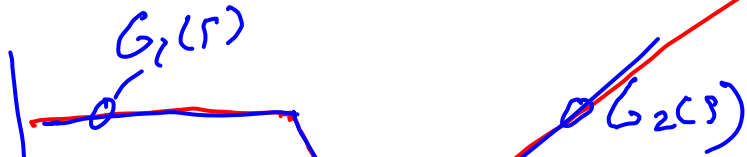
$$G(s) = \underline{G_1(s)} + \underline{G_2(s)}$$




Parallel RLC: well damped

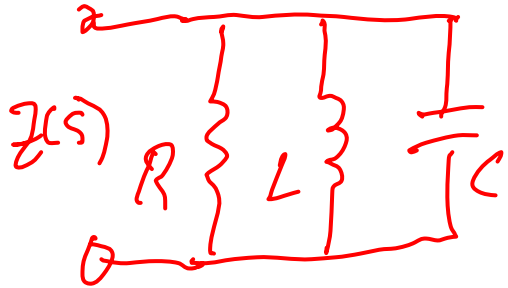

$$f_{p1} = \frac{1}{2\pi} \frac{R}{L}$$


$$f_{p2} = \frac{1}{2\pi RC}$$

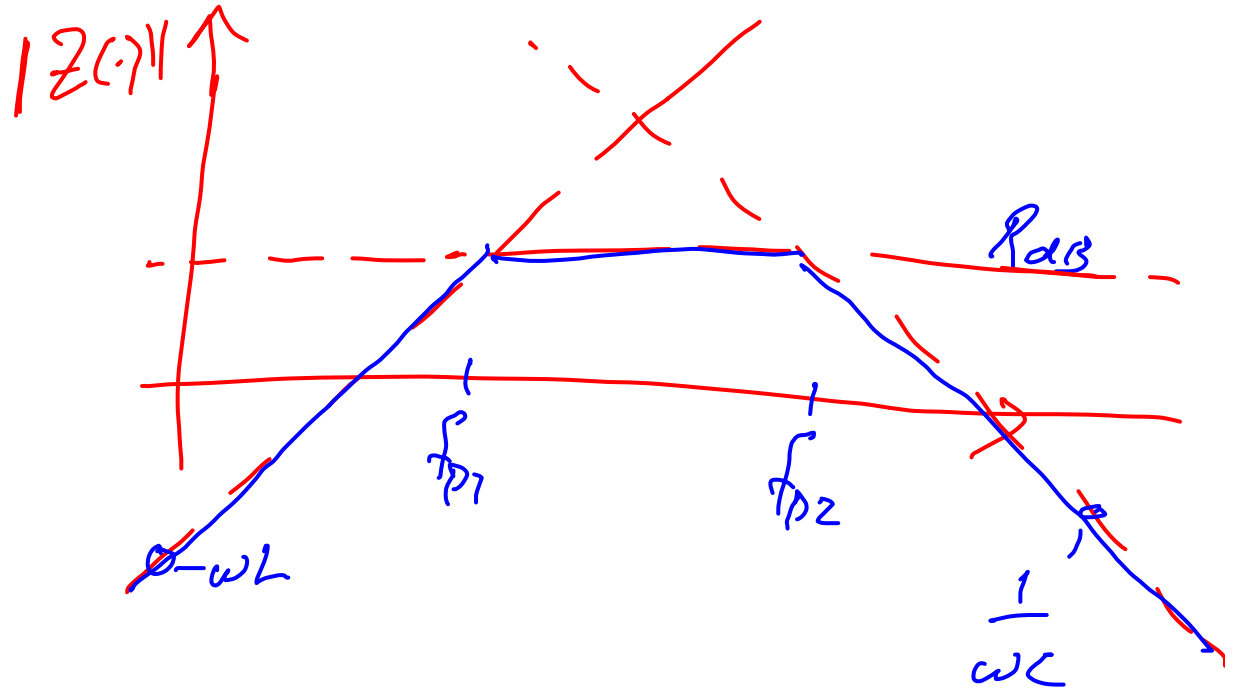

$$z(s) = R \frac{1}{(1 + \frac{\omega_{p1}}{s})(1 + \frac{s}{\omega_{p2}})}$$


Parallel RLC: Resonant

$$Q = \frac{R}{R_0}$$

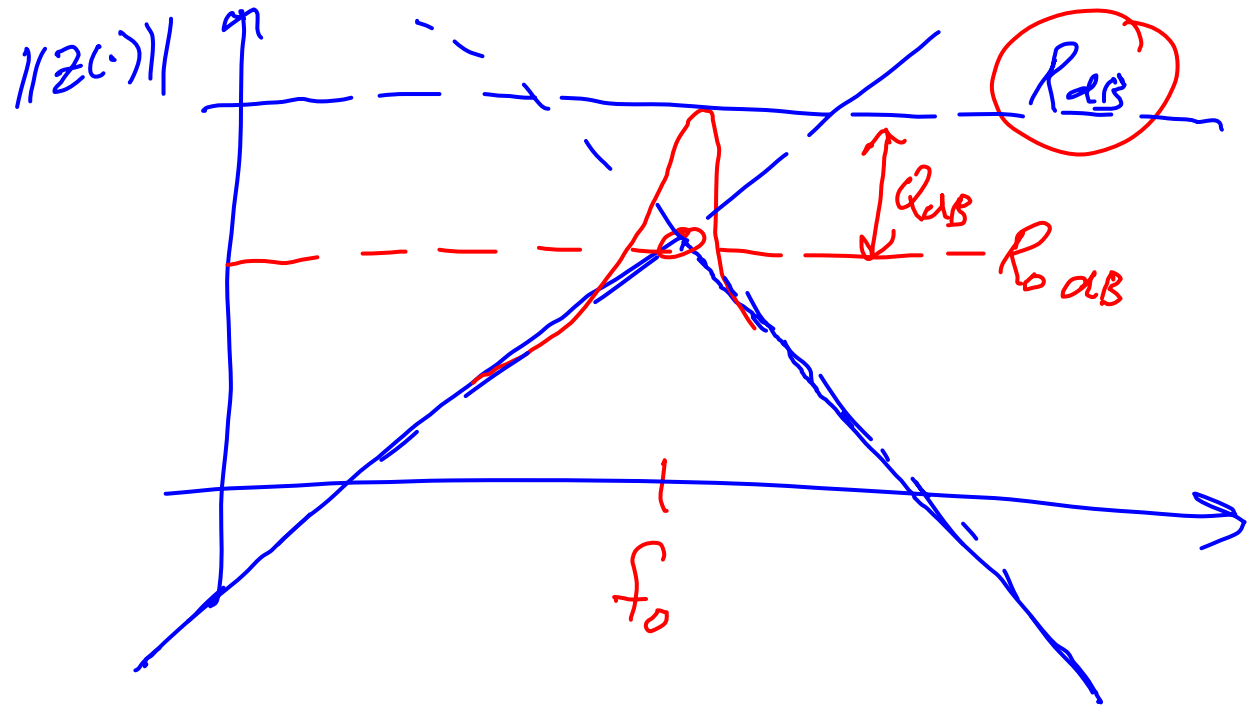


RLC

Impedance graph paper

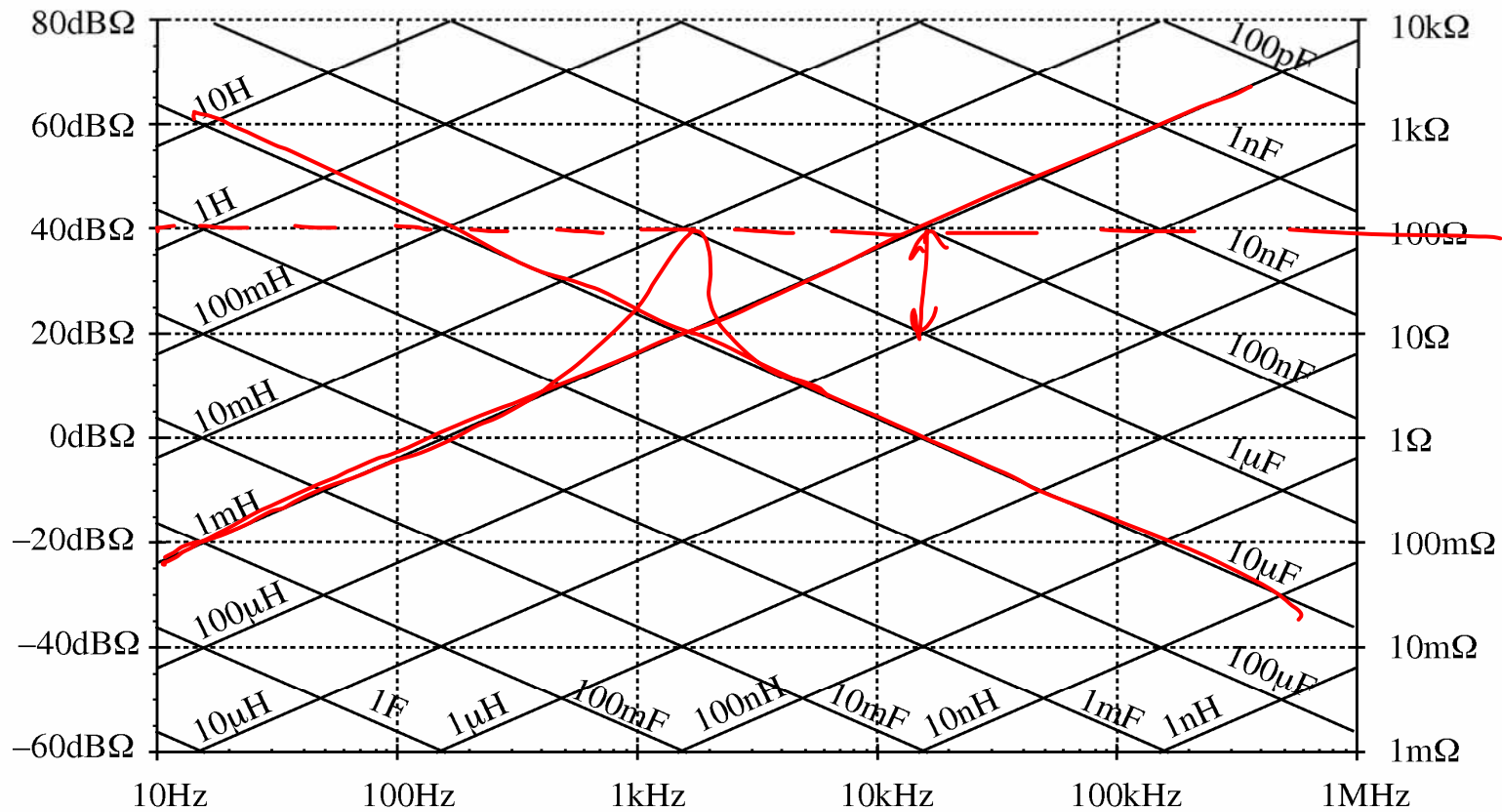

Boost Example

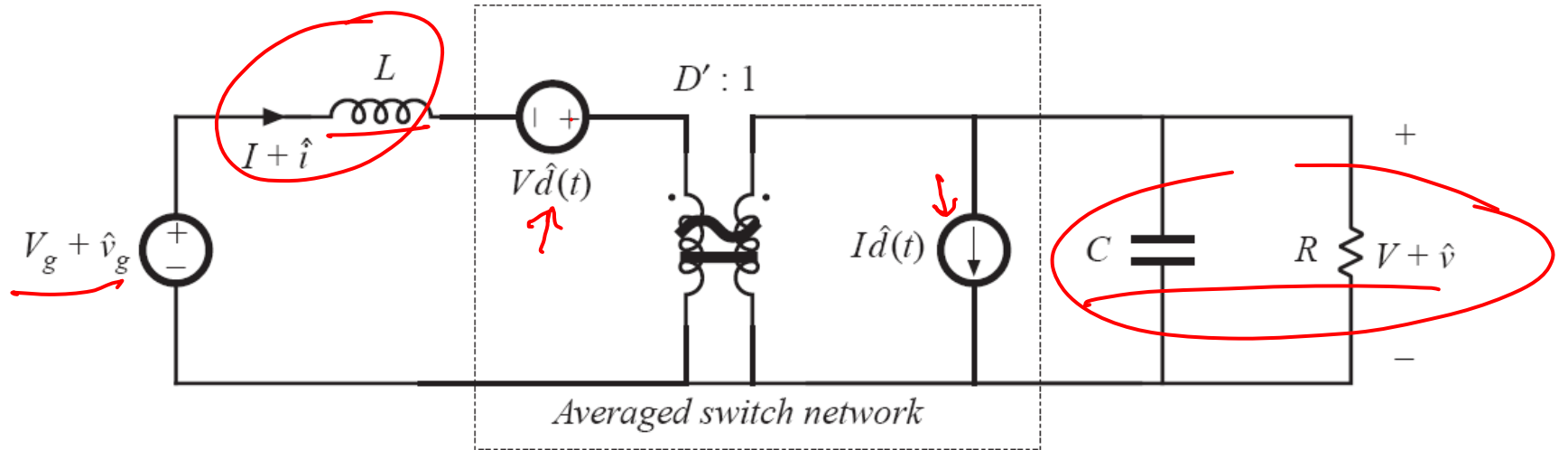

$G_{vd}(s)$