

ECEN 4797/5797

Introduction to Power Electronics


Lecture #29

Friday, October 30, 2009


- “algebra on the graph” example
- Measurement of ac transfer functions ←
- Introduction to converter control systems }
 - Sections 8.4-8.5, 9.1-9.2


Prof. Regan Zane

Boost Example

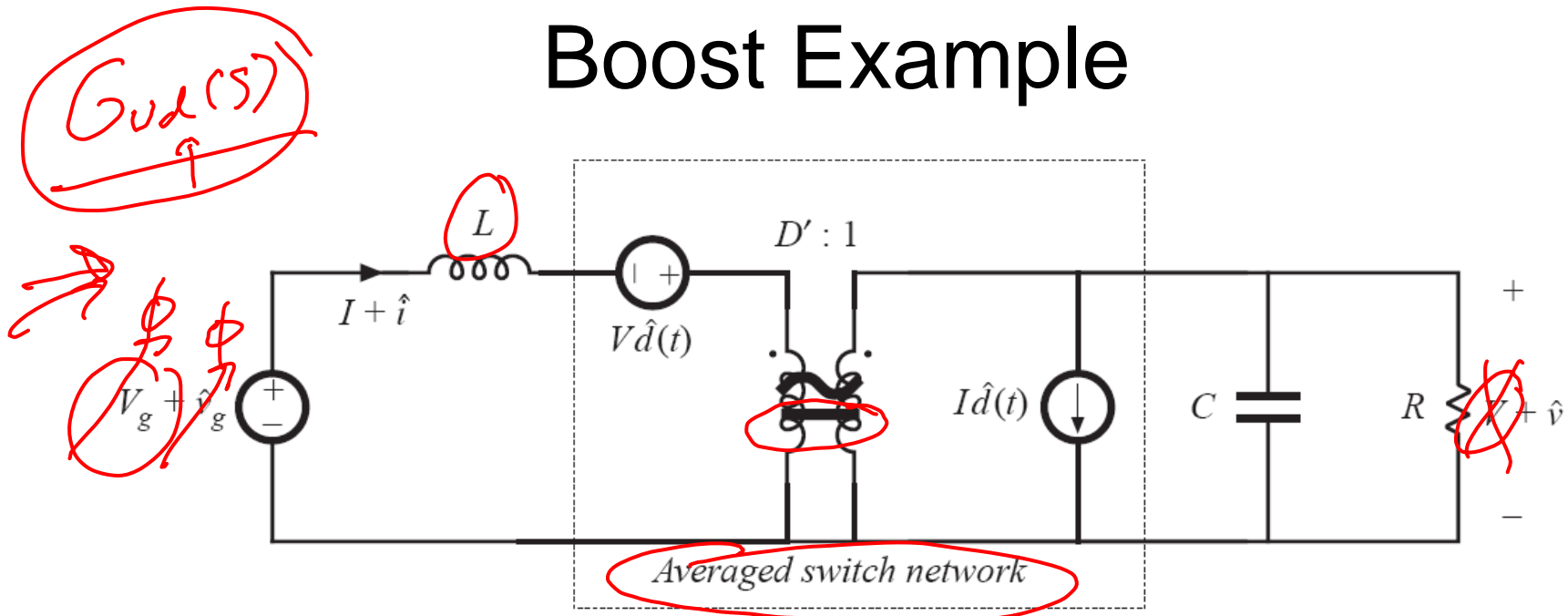

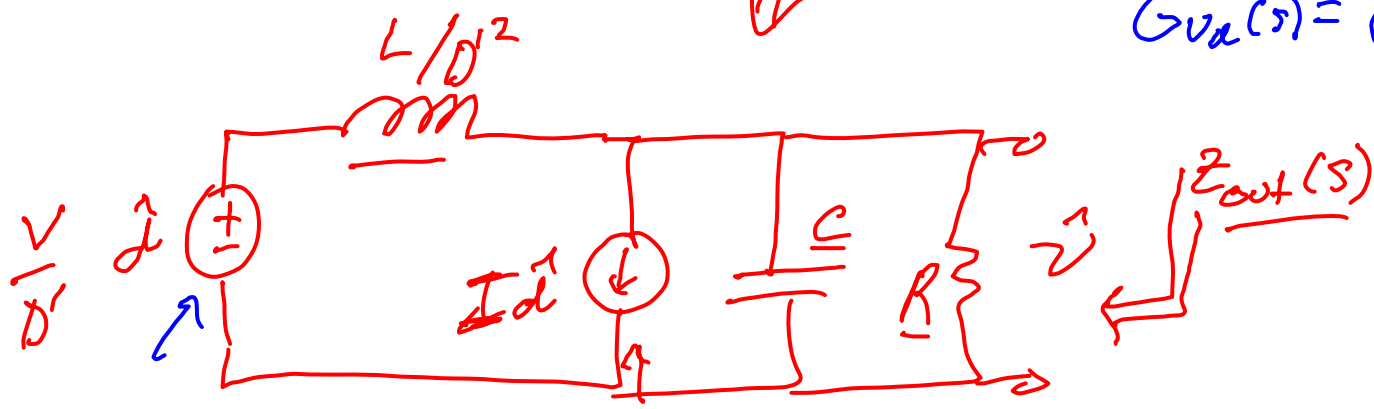
$$G_{vd}(s) = \underline{G_1(s)} + \underline{G_2(s)}$$




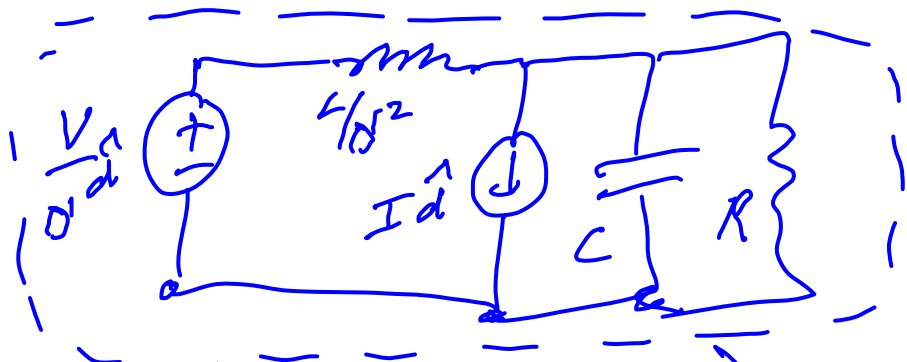

$G_1(s) \downarrow$

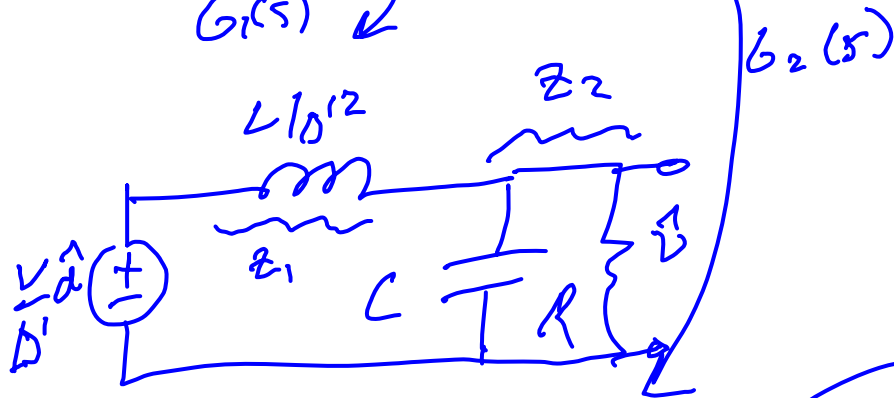

$Z_2(s)$

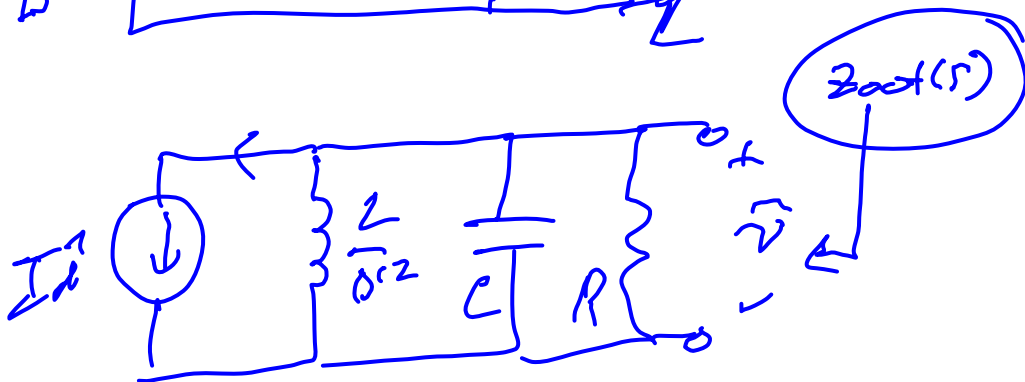

$Z_{out}(s)$

$$G_{out}(s) = G_1(s) + G_2(s) = \frac{v}{\hat{d}} \left(\frac{Z_2}{Z_1 + Z_2} + \frac{1}{Z_1} \right) = \frac{v}{\hat{d}} \frac{Z_{out}}{Z_1}$$



$$G_1(s) = \frac{v}{\hat{d}} \frac{Z_{out}}{Z_1}$$

$$G_2(s) = -\hat{I} \cdot Z_{out}(s)$$

$$Z_{out} = \frac{sL}{s^2} \parallel \frac{1}{sC} \parallel R$$

$$G_{out}(s) = \frac{\hat{v}(s)}{\hat{d}(s)} \Big|_{\hat{v}_g \rightarrow 0} = G_1 + G_2$$

$Z_{out}(s)$:

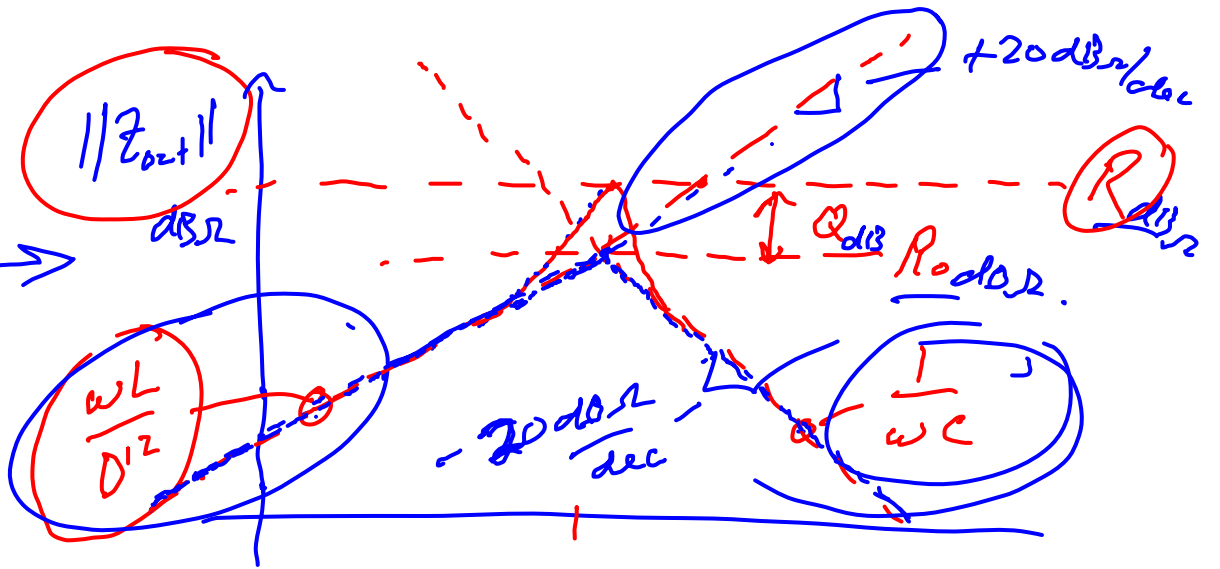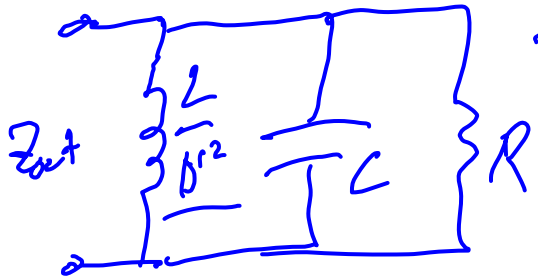


$$f_0 = \frac{D'}{2\pi\sqrt{LC}} = \frac{\omega_0}{2\pi}$$

$$R_0 = \frac{1}{\omega_0 C} = \frac{\sqrt{LC}}{C D'} = \frac{1}{D'} \sqrt{\frac{L}{C}}$$

$$Q = \frac{R}{R_0} = D' R \sqrt{\frac{C}{L}}$$

$$G_1(s) = \frac{Z_{out}}{Z_1}$$


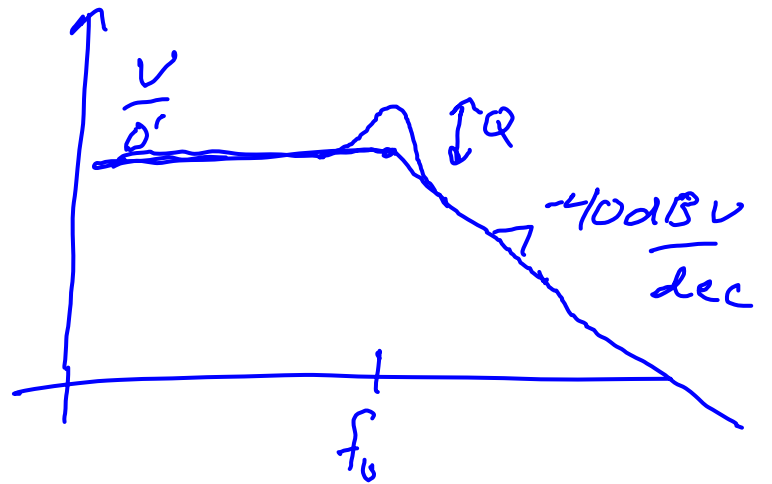



|| G_{out}

G₀
↓
V/D₁

$$G_{out} = G_1 + G_2$$
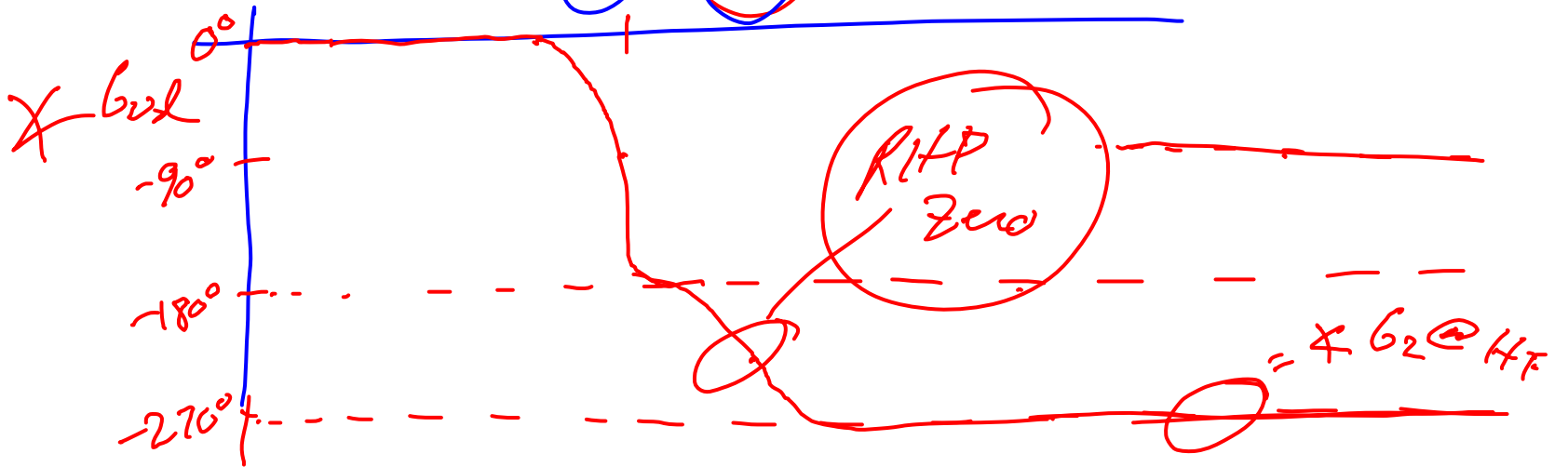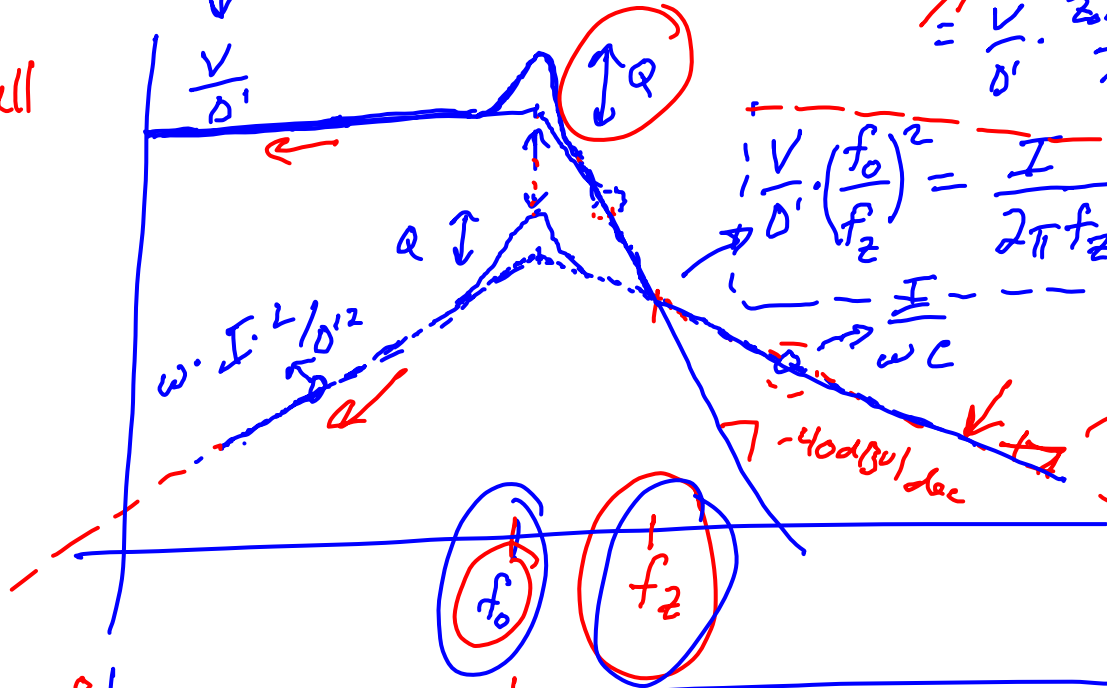
$$= \frac{V}{D_1} \cdot \frac{Z_{out}}{Z_1} + (-I \cdot Z_{out})$$




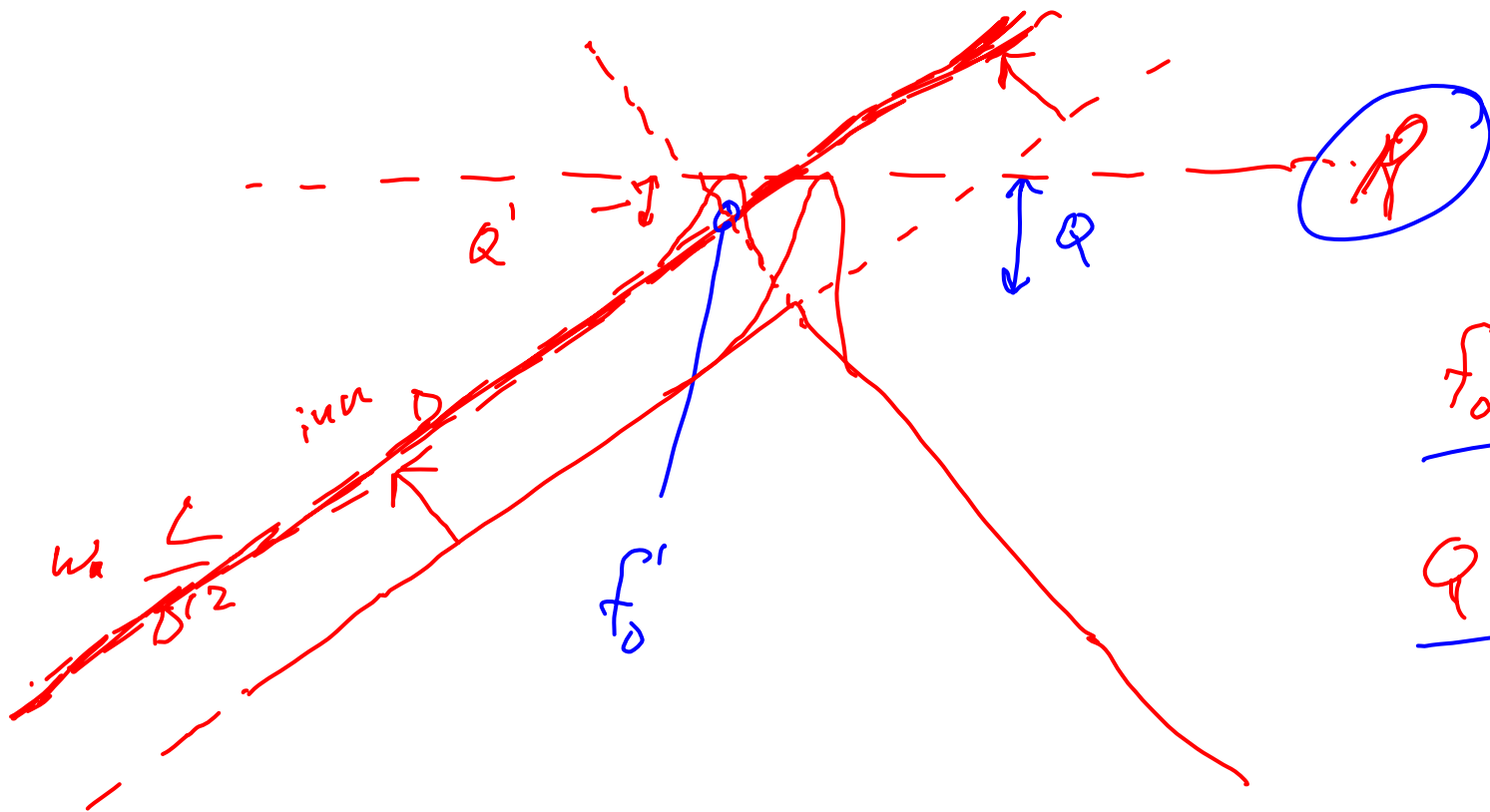

$$\frac{f_0 \rightarrow f_0'}{\quad}$$

$$\frac{Q \rightarrow Q'}{\quad}$$

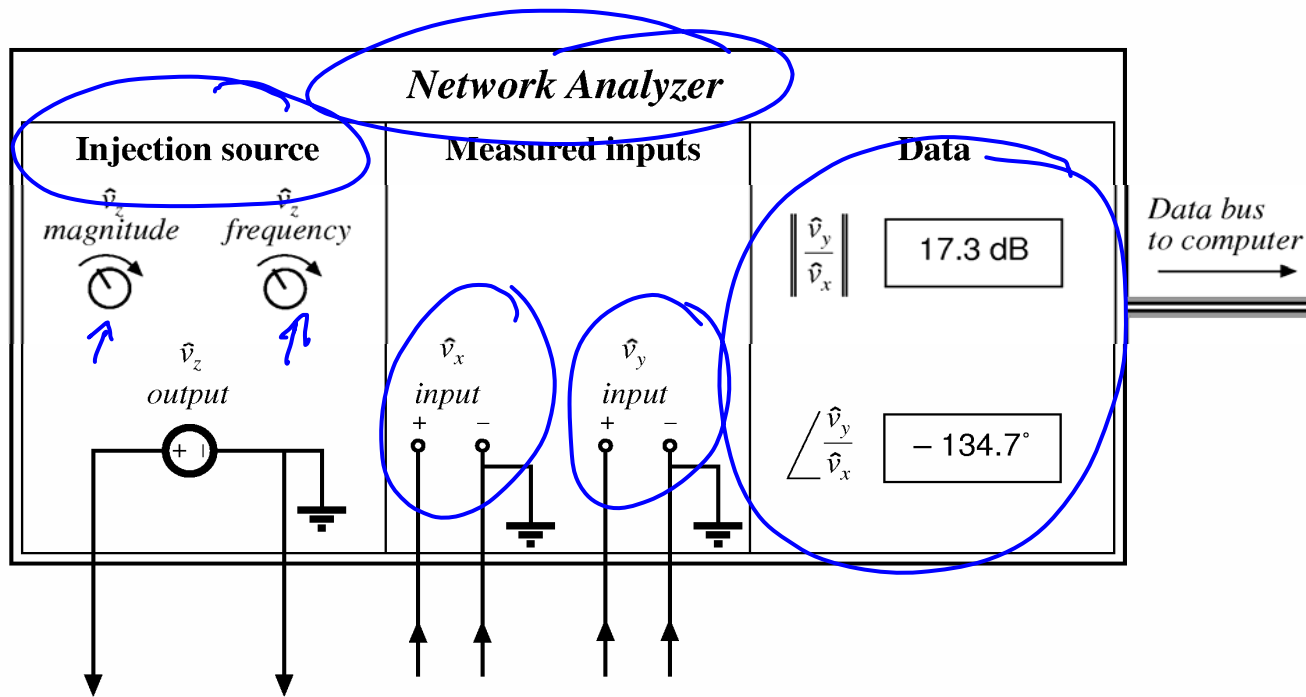8.4. Measurement of ac transfer functions and impedances



Swept sinusoidal measurements

- Injection source produces sinusoid \hat{v}_z of controllable amplitude and frequency
- Signal inputs \hat{v}_x and \hat{v}_y perform function of narrowband tracking voltmeter:


Component of input at injection source frequency is measured

Narrowband function is essential: switching harmonics and other noise components are removed

- Network analyzer measures


$$\left\| \frac{\hat{v}_y}{\hat{v}_x} \right\| \quad \text{and} \quad \angle \frac{\hat{v}_y}{\hat{v}_x}$$

Measurement of an ac transfer function

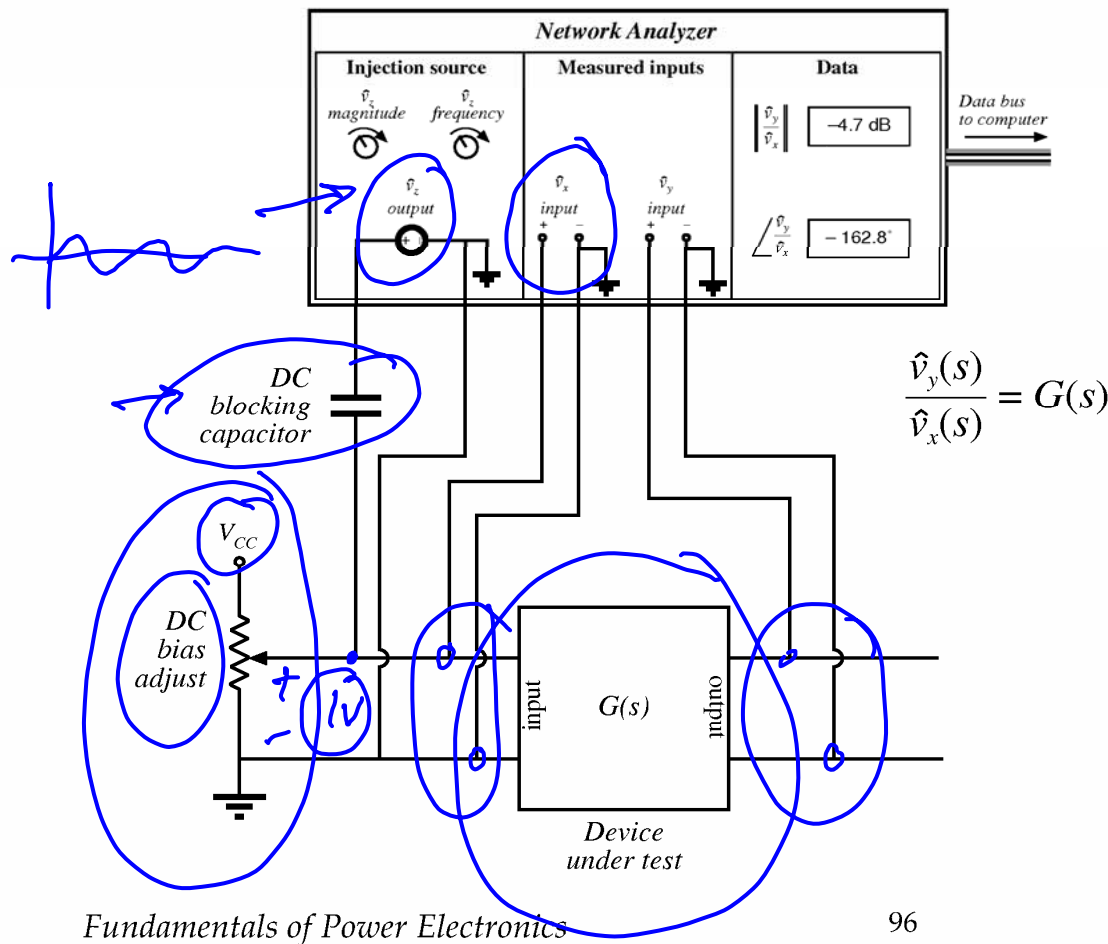

- Potentiometer establishes correct quiescent operating point
- Injection sinusoid coupled to device input via dc blocking capacitor
- Actual device input and output voltages are measured as \hat{v}_x and \hat{v}_y
- Dynamics of blocking capacitor are irrelevant

Measurement of an output impedance

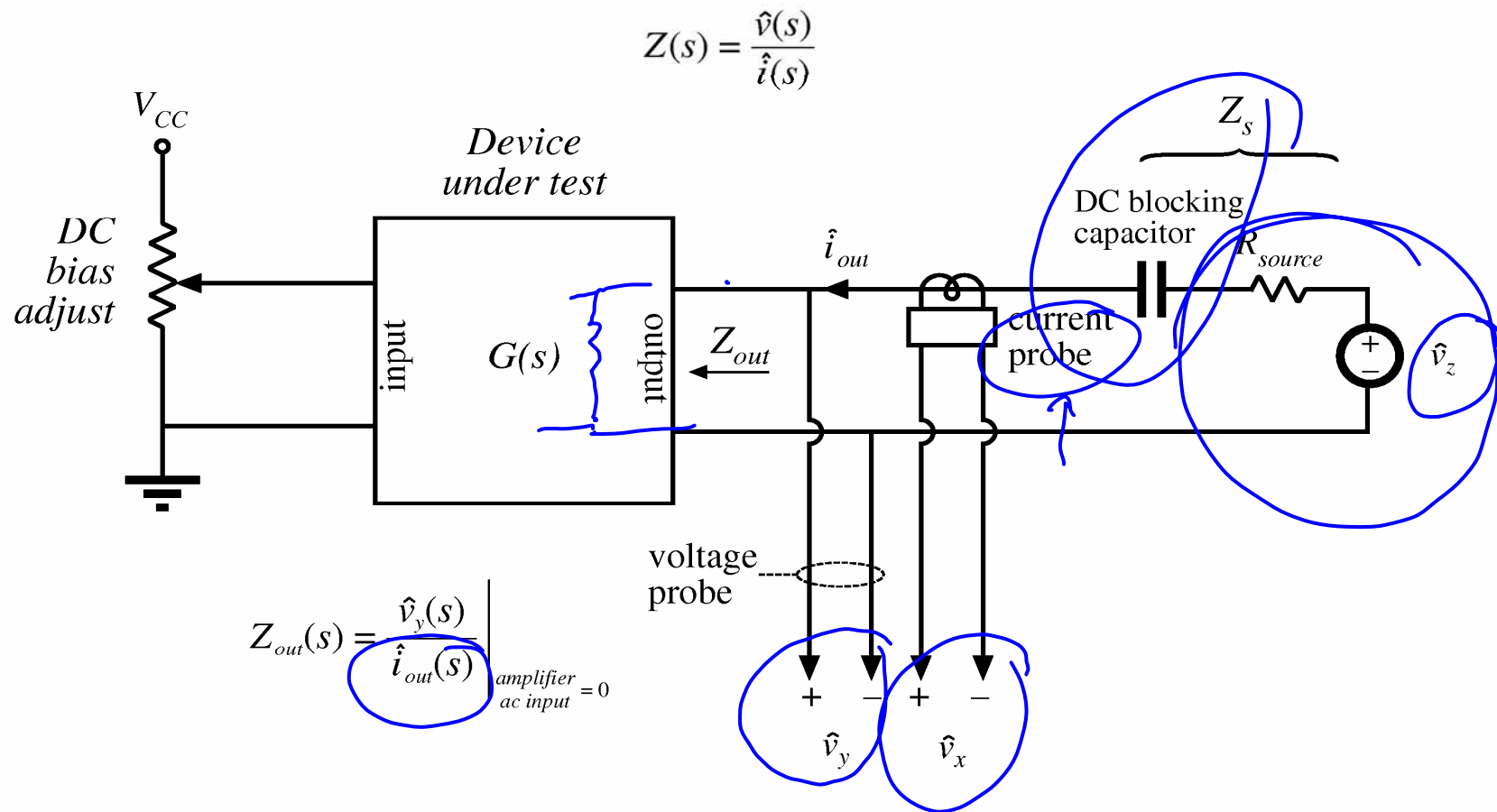

Measurement of output impedance

- Treat output impedance as transfer function from output current to output voltage:

$$Z(s) = \frac{\hat{v}(s)}{\hat{i}(s)} \qquad Z_{out}(s) = \frac{\hat{v}_y(s)}{\hat{i}_{out}(s)} \Bigg|_{\substack{\text{amplifier} \\ \text{ac input} = 0}}$$

- Potentiometer at device input port establishes correct quiescent operating point
- Current probe produces voltage proportional to current; this voltage is connected to network analyzer channel \hat{v}_x
- Network analyzer result must be multiplied by appropriate factor, to account for scale factors of current and voltage probes

Measurement of small impedances


Grounding problems cause measurement to fail:

Injection current can return to analyzer via two paths. Injection current which returns via voltage probe ground induces voltage drop in voltage probe, corrupting the measurement. Network analyzer measures

$$Z + (1 - k) Z_{probe} = Z + Z_{probe} \parallel Z_{rz}$$

For an accurate measurement, require

$$\|Z\| \gg \|(Z_{probe} \parallel Z_{rz})\|$$

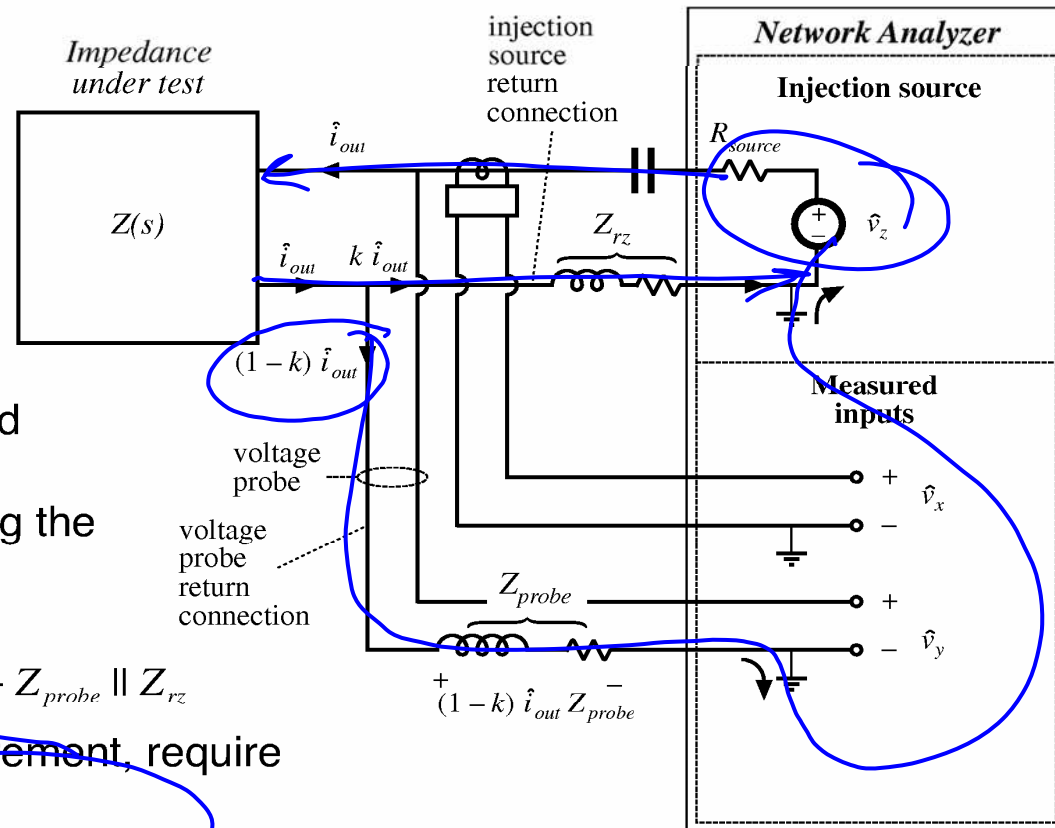

Improved measurement: add isolation transformer

Injection current must now return entirely through transformer. No additional voltage is induced in voltage probe ground connection

