

ECEN 4797/5797

Introduction to Power Electronics

Lecture #6

~~Friday~~ Wednesday, September 4, 2009

Steady State Converter Analysis: ✓

Conduction Losses & Equivalent Circuit Modeling


(Finish examples)

✓ Introduce Chapter 4: Switch Realization

Prof. Regan Zane




$i_{L1} = I_{L1} + i_{L1}$ ripple

Cuk Converter Example

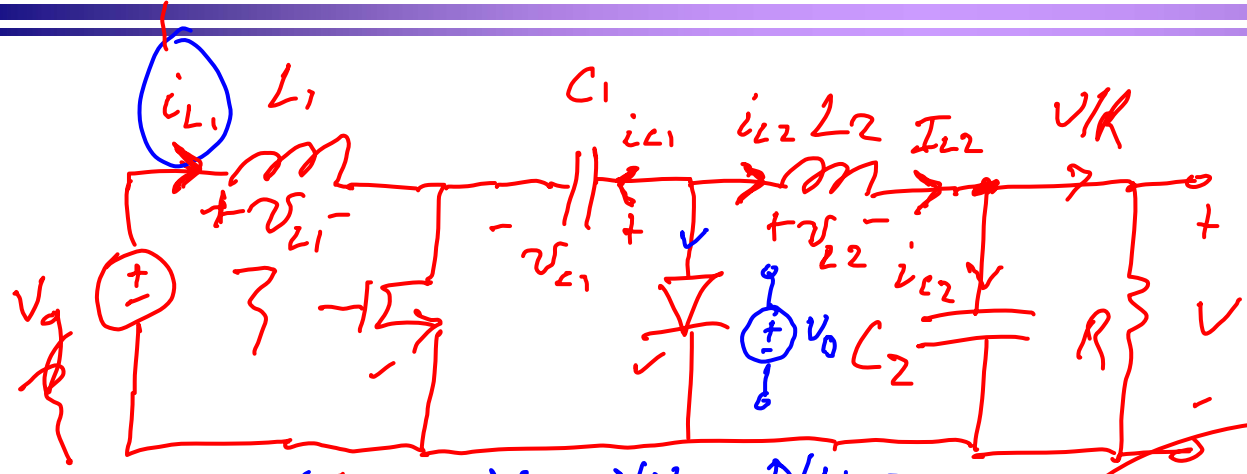


$i_{L1} \approx I_{L1}$
 $i_{L2} \approx I_{L2}$
 $v_{C1} \approx V_{C1}$
 $v = V$
 $\langle i_{L1} \rangle = -D'I_{L2}$
 $-D'I_{L1}$

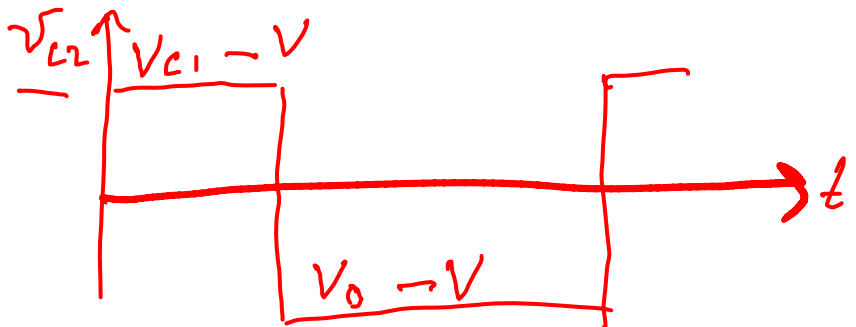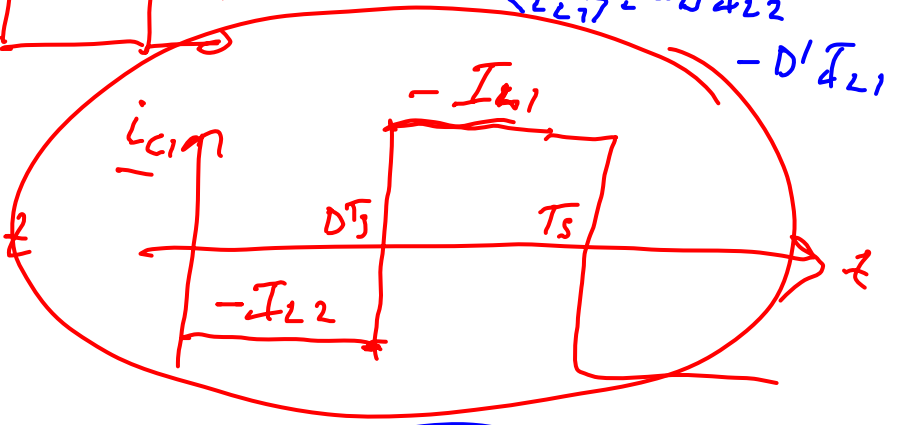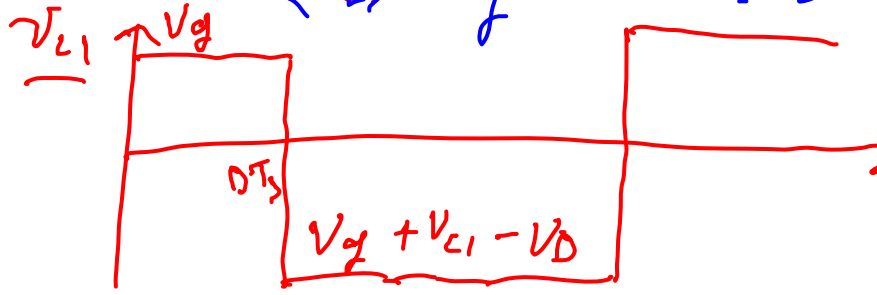$\langle v_{L1} \rangle = Vg + D'V_{C1} - D'V_D = 0$





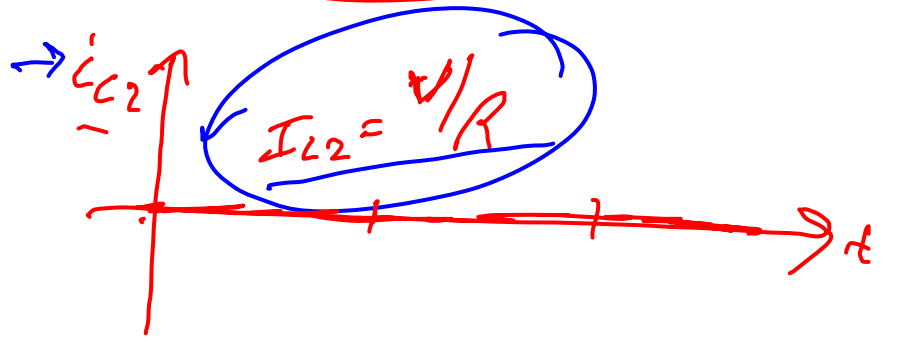$\langle v_{L2} \rangle = DV_{C1} + D'V_D - V = 0$





$$\langle v_{L1} \rangle_{T_s} = V_g + D'V_{c1} - DV_D = 0 \quad \langle i_{C1} \rangle_{T_s} = -DI_{L2} - D'I_{L1} = 0$$
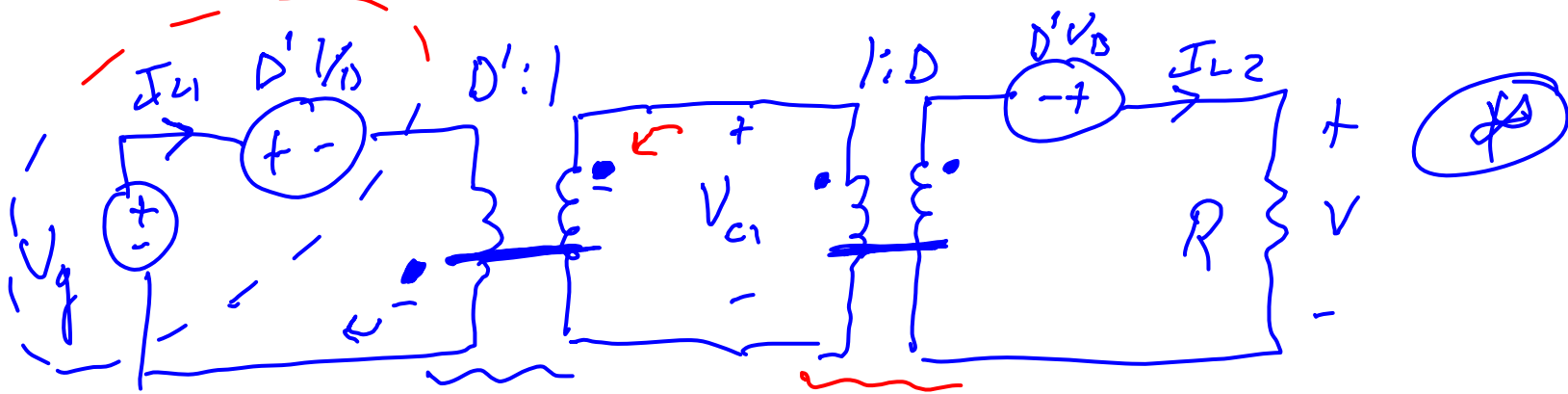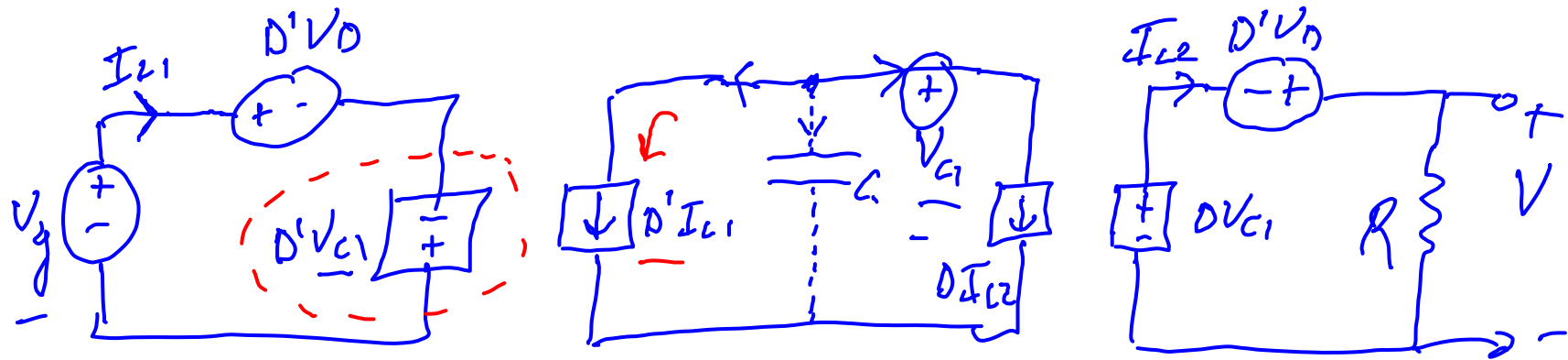
$$\langle v_{L2} \rangle_{T_s} = DV_{c1} + D'V_D - V = 0 \quad \langle i_{C2} \rangle_{T_s} = I_{L2} - \frac{V}{R} = 0$$



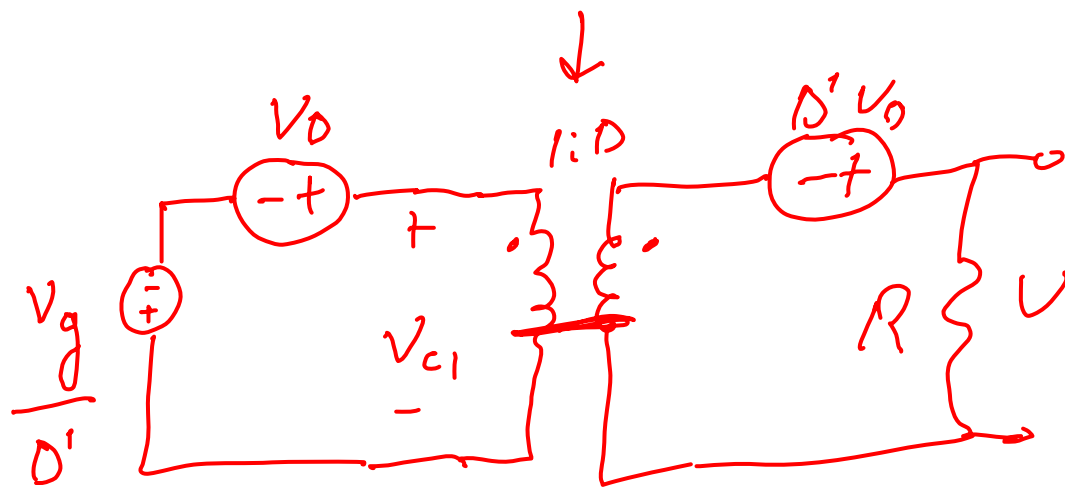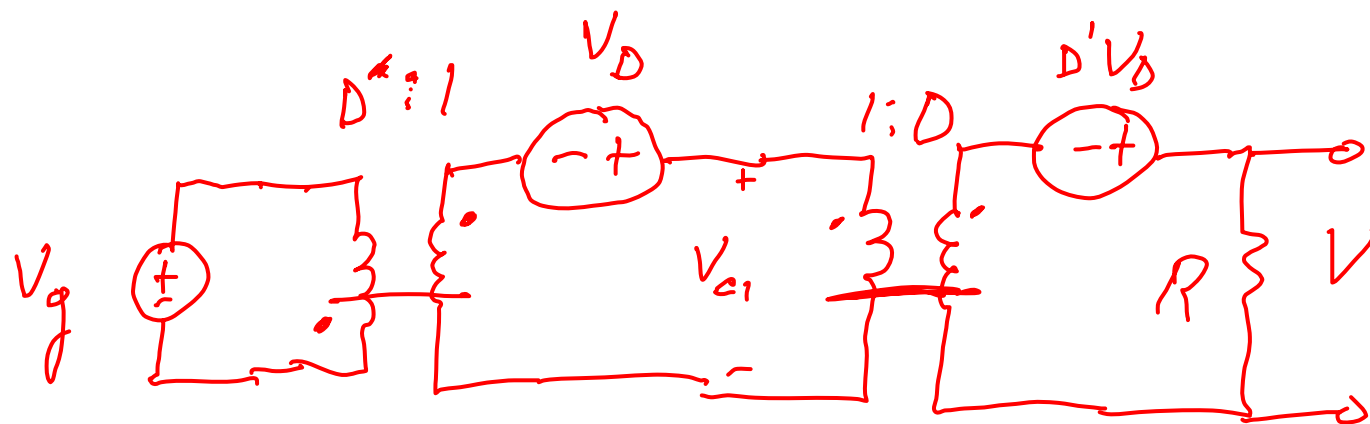ideal: $V_D \rightarrow 0 \Rightarrow \frac{V}{V_g} = M(0)_{ideal} = -\frac{D}{D'} = -\frac{D}{1-D}$




$$V_{c1} = -\frac{V_g}{D'} + V_D$$



$$\underline{V_{c1}} = -\frac{V_g}{D'} \left(1 - \frac{D' V_D}{V_g} \right)$$

IDEAL

I_{L2} vs I_{L1}

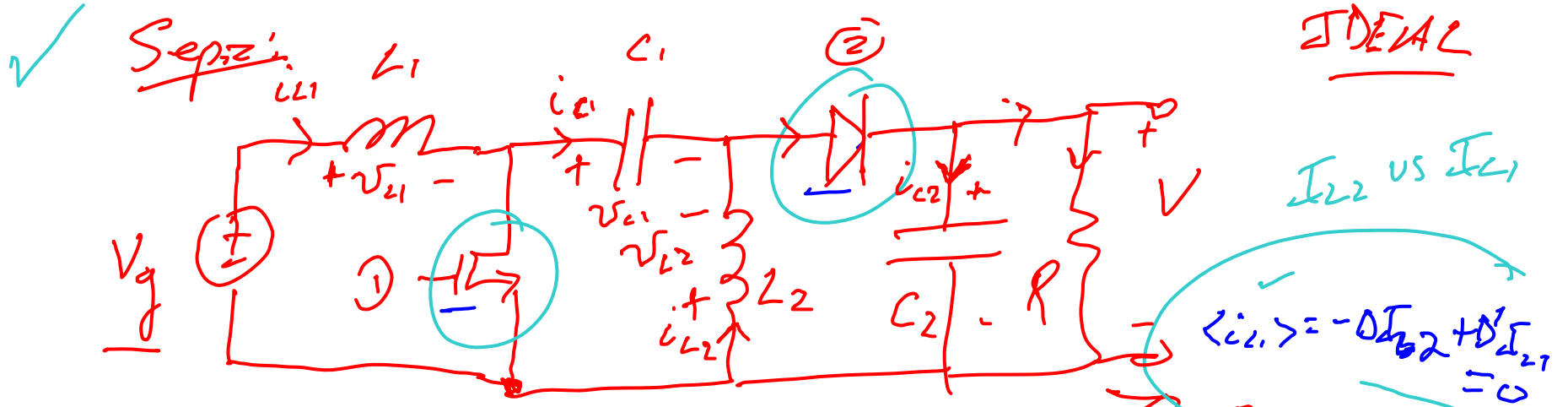

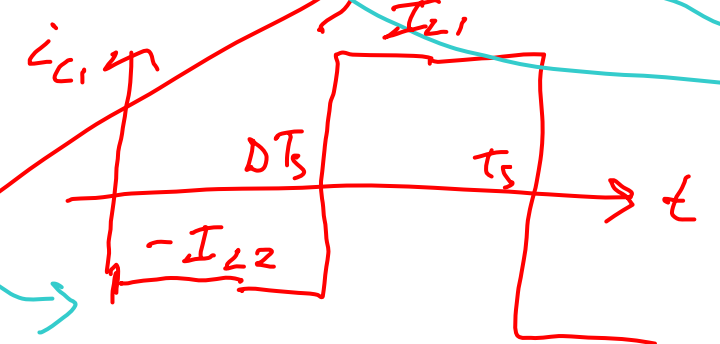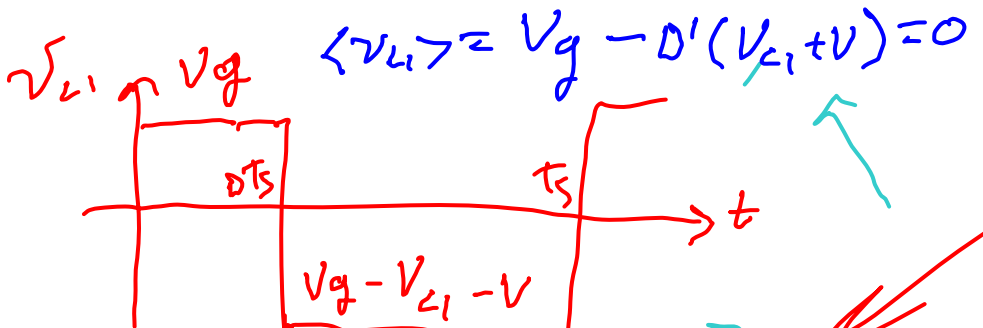$\langle i_{C1} \rangle = -D I_{L2} + D' I_{L1} = 0$



$\langle v_{L2} \rangle = D V_{C1} - D' V = 0$ ✓

$\langle i_{C2} \rangle = D'(I_{L1} + I_{L2}) - V/R = 0$

