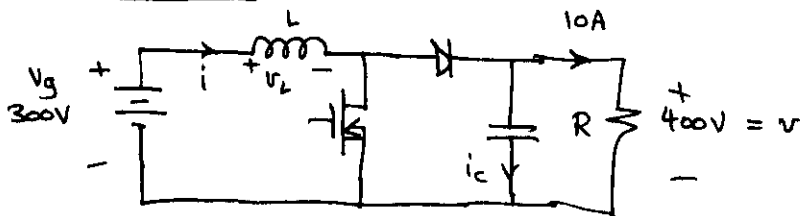


Tutorial  
Solution to Problem 3.9

Note paragraph  
 above Problem 3.8


Interface a 300V battery to a 400V, 10A load.  
 Investigate boost and buck-boost converters; which has better efficiency?  
 MOSFET has  $0.5\Omega$  on-resistance. All other losses can be ignored.

Boost converter



$$R = \frac{400V}{10A} = 40\Omega$$

transistor on diode off

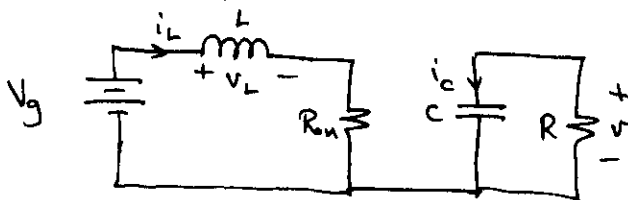


sm. ripple approximation

$$v_L(t) = V_g - i_L(t)R_{on} \approx V_g - I_L R_{on}$$

$$i_c(t) = -v(t)/R \approx -\frac{V}{R}$$

transistor off diode on

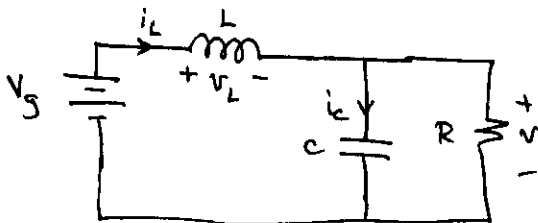

$$v_L(t) = V_g - v(t) \approx V_g - V$$

$$i_c(t) = i_L(t) - \frac{v(t)}{R} \approx I_L - \frac{V}{R}$$

Volt-second balance

$$\langle v_L(t) \rangle = 0 = D(V_g - I_L R_{on}) + D'(V_g - V) = V_g - D R_{on} I_L - D' V$$


charge balance

$$\langle i_c(t) \rangle = 0 = D\left(-\frac{V}{R}\right) + D'\left(I_L - \frac{V}{R}\right) = D' I_L - \frac{V}{R}$$


Construct equivalent circuit

inductor - loop equation

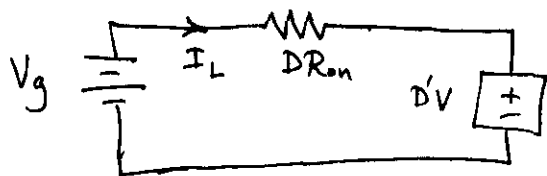
$$\langle v_L \rangle = 0 = V_g - D R_{on} I_L - D'V$$



capacitor - node equation

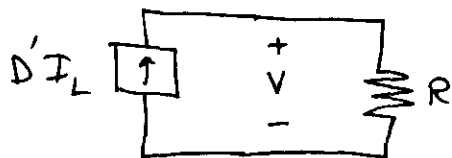

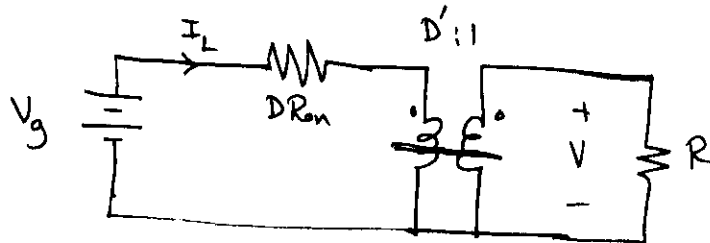Combine circuits, replace dependent sources with  $D':1$  transformer



Solution:

$$V = \frac{1}{D'} V_g \frac{1}{1 + \frac{D}{(D')^2} \frac{R_{on}}{R}}$$

$$I_L = \frac{V}{DR}$$

$$\eta = \frac{1}{1 + \frac{D}{(D')^2} \frac{R_{on}}{R}}$$

$$P_{loss} = I_L^2 D R_{on}$$

For the values  $V_g = 300$ ,  $V = 400$ ,  $R = 40$ ,  $R_{on} = 0.5$

find  $D$  and  $\eta$  (and also  $I_L$  and  $P_{loss}$ )

Solve quadratic equation for  $D$  (arises from  $\frac{V}{V_g} = \frac{1}{1-D} \frac{1}{1 + \frac{D}{(1-D)^2} \frac{R_{on}}{R}}$ )  
 $\Rightarrow D = 0.2543$  (note  $D \rightarrow 0.2500$  for  $R_{on} \rightarrow 0$ )


Then  $\eta = 0.9943$

99.43%


$I_L = 13.4 \text{ A}$

$P_{\text{loss}} = 22.9 \text{ W}$

Buck-boost converter

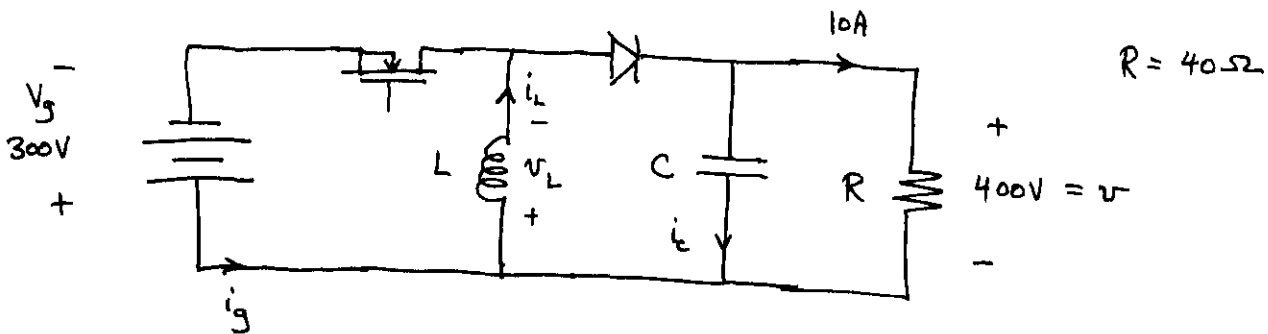

transistor on  $0 < t < DT_s$  diode off

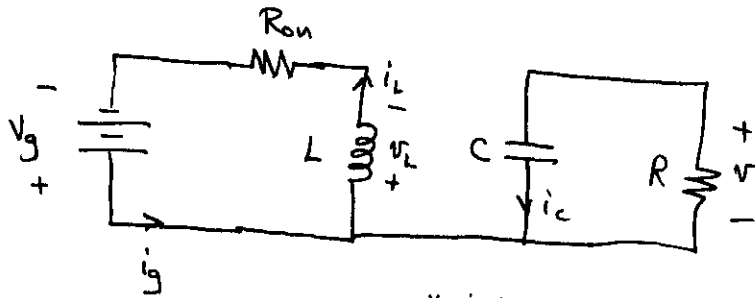

small ripple approximation

$v_L(t) = V_g - i_L R_{on} \approx V_g - I_L R_{on}$

$i_C(t) = -v(t)/R \approx -V/R$


$i_g(t) = i_L(t) \approx I_L$

Since the converter input current  $i_g(t)$  is pulsating, we must write equations for  $i_g(t)$  during each subinterval, then average to find the dc component

transistor off

$$DT_3 < t < T_3$$

diode on

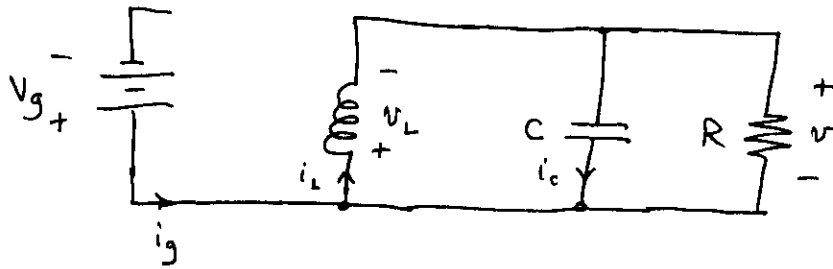

$$v_L(t) = -v(t) \approx -V$$

$$i_c(t) = i_L(t) - v(t)/R \approx I_L - V/R$$

$$i_g(t) = 0$$

Volt-second balance

$$\langle v_L(t) \rangle = 0 = D(V_g - I_L R_{on}) + D'(-V)$$

charge balance


$$\langle i_c(t) \rangle = 0 = D(-V/R) + D'(I_L - V/R)$$

average input current


$$\langle i_g \rangle = I_g = D(I_L) + D'(0)$$

Construct equivalent circuit

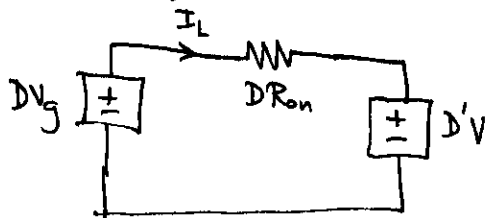
inductor loop equation:  $DV_g - I_L D R_{on} - D'V = \langle v_L \rangle = 0$



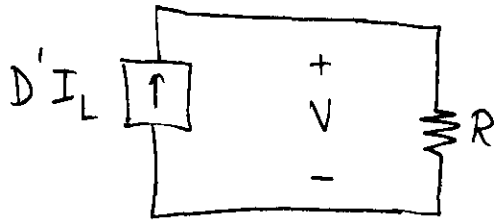
Capacitor node equation:  $D'I_L - \frac{V}{R} = \langle i_c \rangle = 0$



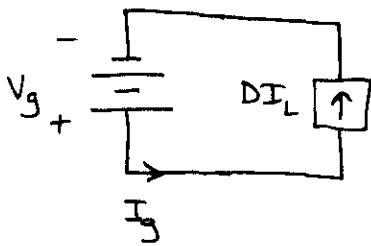
Input current (node) equation:  $I_g = DI_L$



Draw circuit models together:

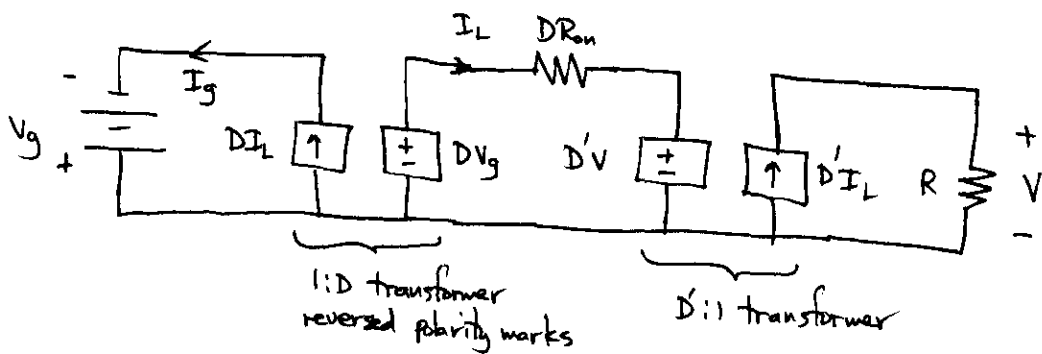

Model including ideal dc transformers:

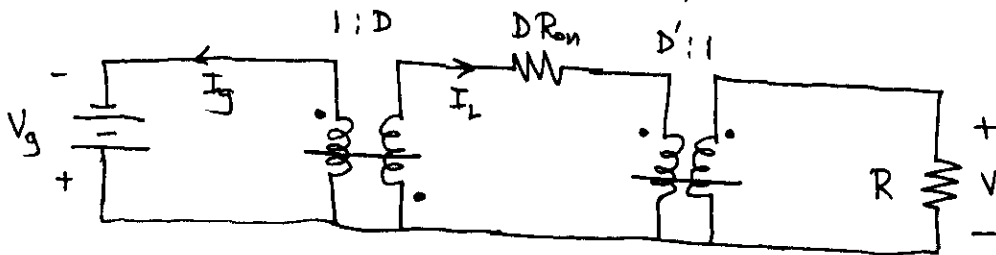

### Solution of model:

$$V = \frac{D}{D'} V_g \frac{R}{R + \frac{D}{(D')^2} R_{on}} \Rightarrow \frac{V}{V_g} = \frac{D}{D'} \frac{1}{1 + \frac{D}{(D')^2} \frac{R_{on}}{R}}$$

$$\eta = \frac{1}{1 + \frac{D}{(D')^2} \frac{R_{on}}{R}}$$

$$I_L = \frac{V}{D'R}$$

$$P_{loss} = I_L^2 D R_{on}$$

Note that, with the exception of the extra factor of  $D$  in the  $\frac{V}{V_g}$  equation, all of the above equations are identical to the respective boost converter equations on page 2.

Because of the extra factor of  $D$ , the buck-boost converter must operate at a larger duty cycle. This leads to increased inductor current, increased transistor conduction time, and increased power loss.

### Solution

$$D = 0.5813$$

$$\eta = 0.9602 \quad 96.02\%$$

$$I_L = 23.89 \text{ A}$$

$$P_{loss} = 165.8 \text{ W}$$

— more than 7 times larger than boost  
heatsink must be 7 times larger  
boost is much better than buck-boost  
in this application

End of problem