
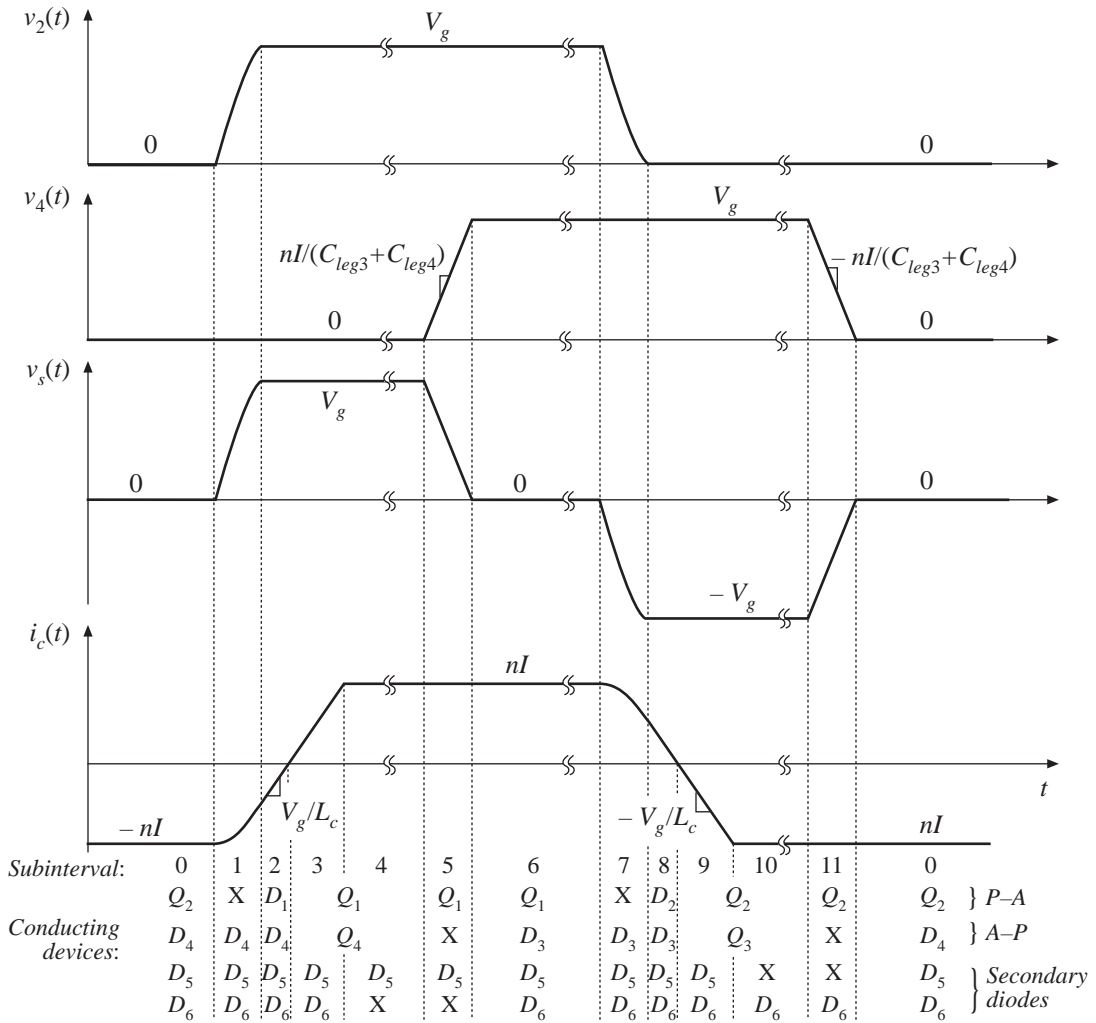


State Plane Analysis of Basic Zero-Voltage Transition (ZVT) Full-Bridge Converter

Schematic and waveforms:

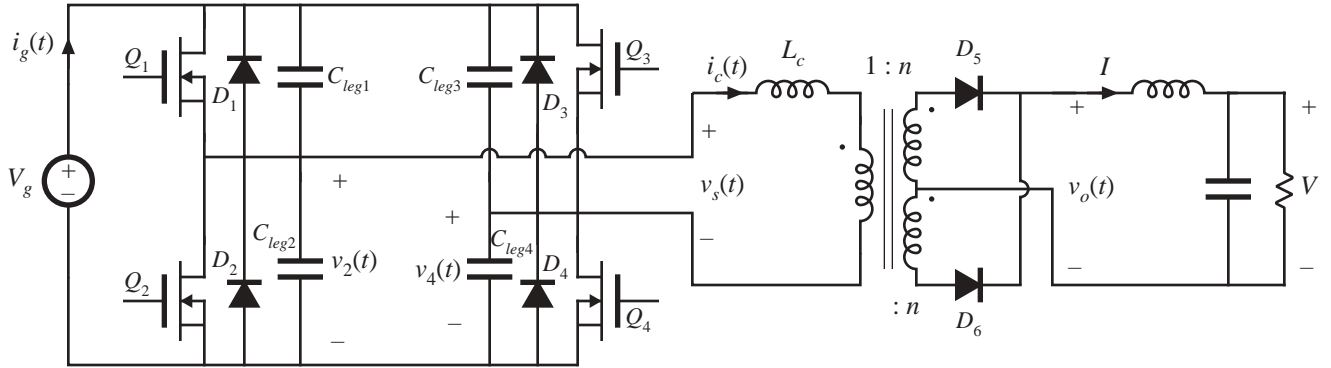

Subinterval 1


Begins when Q_2 turns off

D_4, D_5, D_6 conduct

Note that when D_5 and D_6 both conduct, then the transformer secondary is short-circuited.

$i_c \ll 0$. Initial $v_2 = 0, i_c = -nI$

Circuit becomes

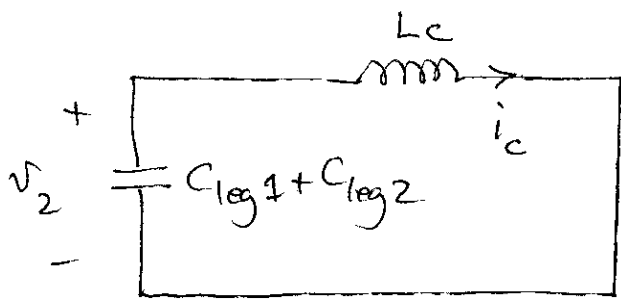


Normalized state plane: Define $V_{base} = V_g,$

$$I_{base} = \frac{V_g}{R_0}, \quad R_0 = \sqrt{\frac{L_c}{C_{leg1} + C_{leg2}}}$$

$$\omega_0 = \frac{1}{\sqrt{L_c (C_{leg1} + C_{leg2})}}$$

$$j_c = \frac{i_c}{I_{base}}, \quad J = \frac{nI}{I_{base}}, \quad m_2 = \frac{v_2}{V_{base}}$$

initial $j_c = -J, \quad m_2 = 0$

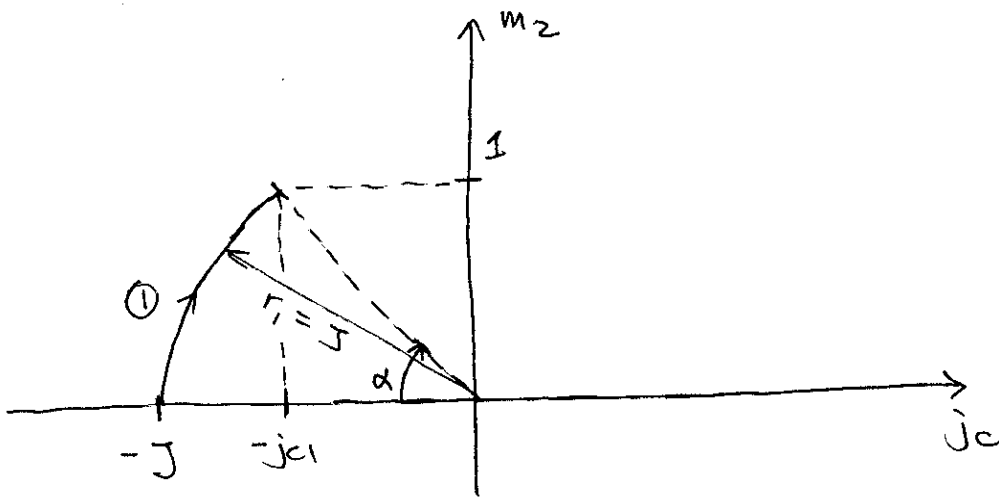

State plane trajectory follows circular arc centered at origin. Radius $r_1 = J$,

Interval ends when $v_2 = V_g$, forward-biasing D_1 .

At end of interval, $m_2 = 1$ and $j_c = -j_c1$

Solution of state plane geometry:

$$j_c1 = \sqrt{r_1^2 - 1} = \sqrt{J^2 - 1}$$

$$\text{and } \alpha = \omega_0 t_1 = \tan^{-1}\left(\frac{1}{+j_c1}\right) = \tan^{-1}\left(\frac{1}{\sqrt{J^2 - 1}}\right)$$

where interval 1 length = t_1 .

For zero-voltage switching, we require $J \geq 1$.

If $J < 1$, then v_2 never reaches V_g , and switching loss occurs when Q_1 turns on.


Subinterval 2 D_1 is forward-biased

Subinterval 3 conducting devices : D_1, D_4, D_5, D_6
or Q_1, Q_4, D_5, D_6

initial $i_c = -i_{c1}$

let $t_3+t_2 =$ length of intervals ② and ③

Circuit is

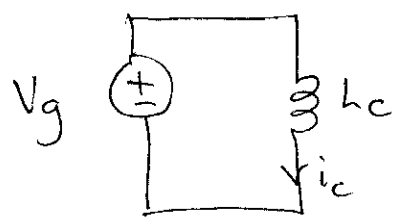


i_c increases with slope $\frac{V_g}{L_c}$

Interval end when $i_c = nI$; D_6 then becomes reverse-biased

so $\frac{V_g}{L_c}(t_2+t_3) = nI + i_{c1}$

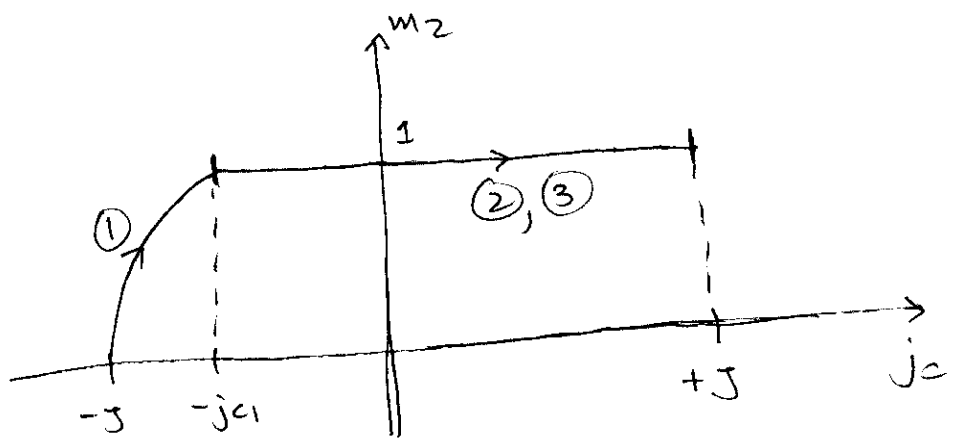$\Rightarrow t_3+t_2 = (nI + i_{c1}) \frac{L_c}{V_g}$




Subinterval ④

D_6 is reverse-biased.

Q_1, Q_4, D_5 conduct

Circuit is

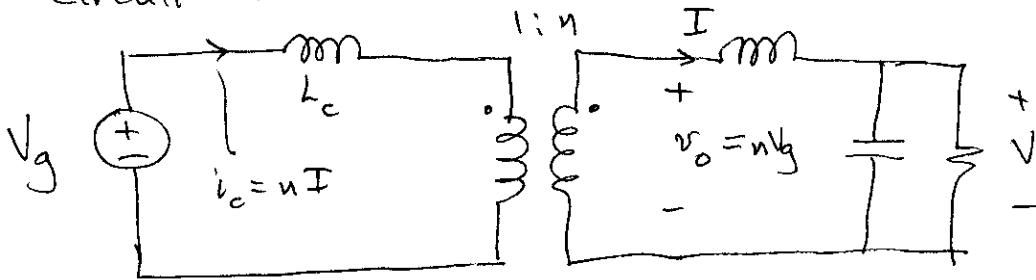

Power is transferred through switches and transformer to output.


$i_c = nI$ constant

$v_2 = V_g$ constant

Interval ends when controller turns off Q_4 .

Subinterval ⑤

Q_4 is off. Q_1, D_5 conduct

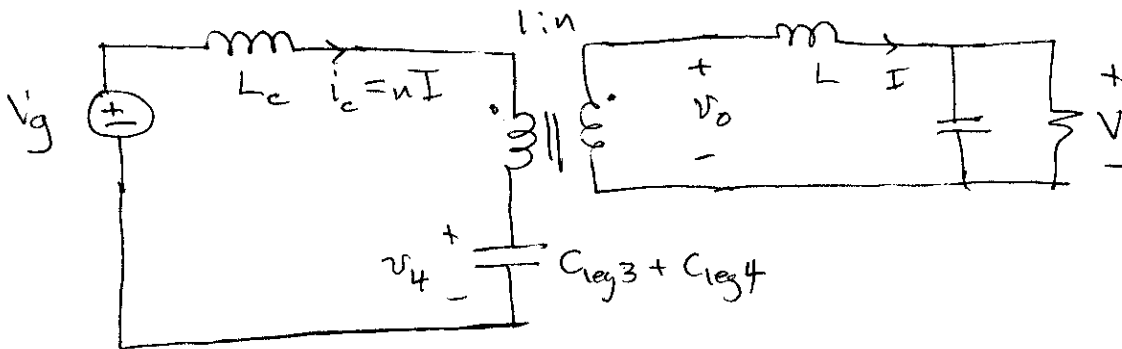

v_4 charges from 0 to V_g , with slope $\frac{nI}{C_{1g3} + C_{1g4}}$


Length of interval is $t_5 = \frac{V_g}{nI} (C_{1g3} + C_{1g4})$

During this interval, voltage across L_c is $L_c \frac{d(nI)}{dt} \times 0$
and $v_o = n(V_g - v_4)$

Subinterval ⑥

Q_1, D_3, D_5, D_6 conduct.
interval begins when D_3 and D_6 are forward-biased.

Circuit is

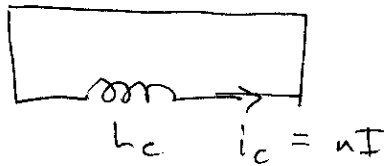

i_c remains constant and equal to nI

During this interval, the current $i_c = nI$ circulates around a loop containing the transformer primary winding, L_c , Q_1 , and D_3 . This current induces conduction loss in these elements.


This current is needed to induce zero-voltage switching during interval ⑦. However, if interval ⑥ is long in duration, then the conduction loss induced during interval ⑥ may be larger than the switching loss mitigated during interval ⑦.

To obtain a high-efficiency design, the transformer turns ratio should be chosen so that $M = V/nV_g$ is only slightly less than 1. Small values of M lead to long interval ⑥ lengths, with increased conduction loss.

During interval ⑥, $v_2 = 0, i_c = nI, v_o = 0.$

Subintervals ⑦ to ⑪ and ⑩ are symmetrical to subintervals ① to ⑥.


Complete state plane trajectory:

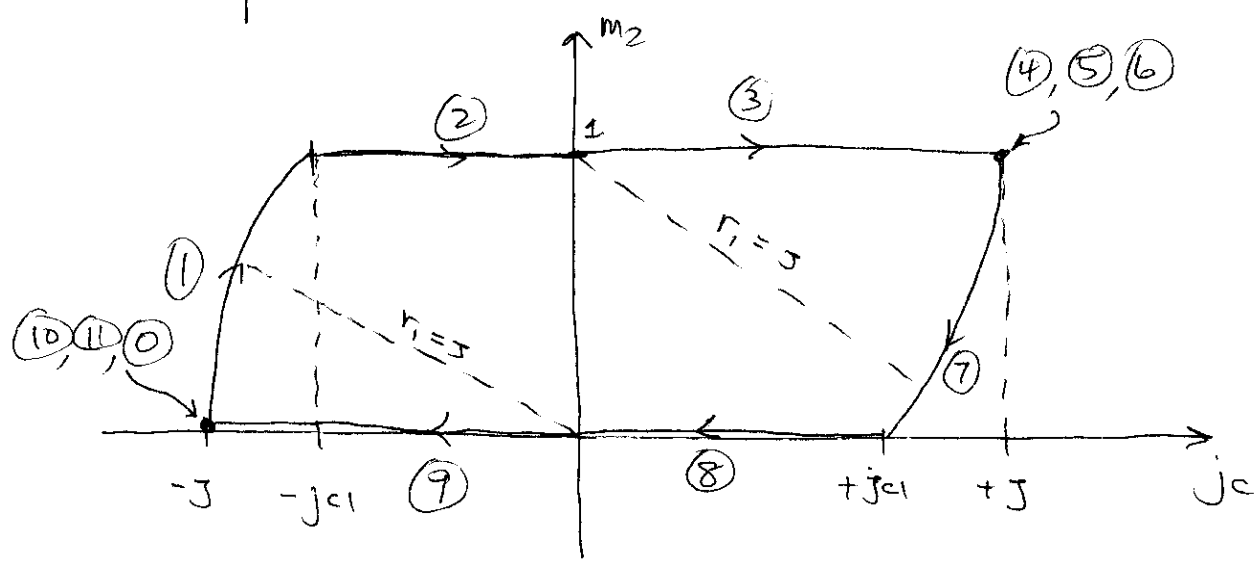

Averaging

$$\langle v_o \rangle = V = \frac{2}{T_s} \int_0^{\frac{T_s}{2}} v_o dt$$

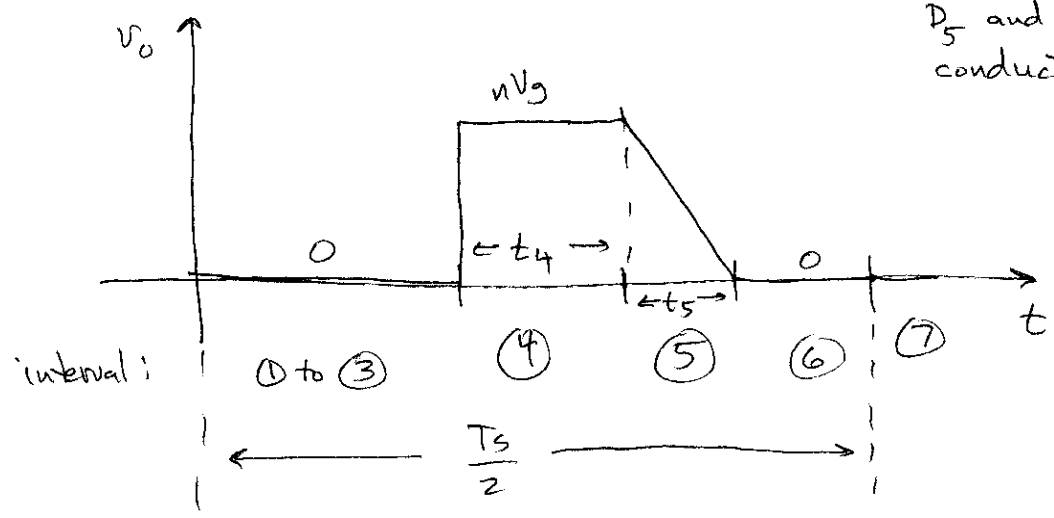note $v_o = 0$ whenever D_5 and D_6 both conduct.




$$\langle v_o \rangle = \frac{2}{T_s} \cdot \left[nV_g t_4 + \frac{1}{2} nV_g t_5 \right]$$

Length of interval (4) depends on control input.

Phase shift control:

Phase control variable ϕ performs the role of the duty cycle:

$$0 \leq \phi \leq 1$$

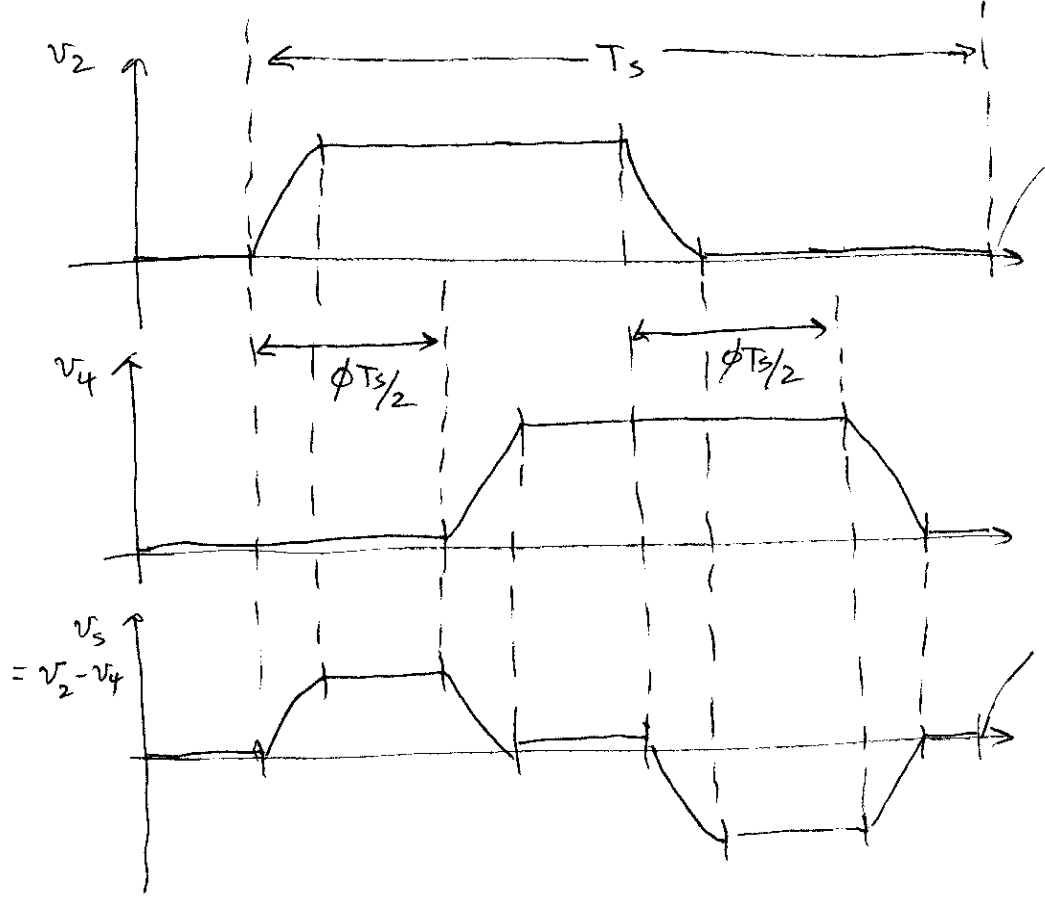

when $\phi=0$, v_2 and v_4 are in phase, and output voltage is minimized.

When $\phi=1$, v_2 and v_4 are of opposite phase, and output voltage is maximized.

$$\phi T_s / 2 = t_1 + t_2 + t_3 + t_4$$

(9)
RWE

$$\text{So } t_4 = \frac{\phi T_s}{2} - t_1 - t_2 - t_3$$

Hence

$$\langle v_o \rangle = \frac{2}{T_s} nV_g \left[\frac{\phi T_s}{2} - t_1 - t_2 - t_3 + \frac{1}{2} t_5 \right]$$

$$M = \frac{V}{nV_g} = \frac{\langle v_o \rangle}{nV_g} = \phi - \frac{2}{T_s} \left[t_1 + t_2 + t_3 - \frac{1}{2} t_5 \right]$$

$$\text{with } t_1 = \frac{1}{\omega_0} \tan^{-1} \left(\frac{1}{\sqrt{J^2 - 1}} \right)$$

$$t_2 + t_3 = (nI + ic_1) \frac{L_c}{V_g}$$

$$t_5 = \frac{V_g}{nI} (C_{leg3} + C_{leg4})$$

substitute and normalize to obtain

$$M = \phi + \frac{F}{2\pi} \left[\frac{1}{J} - 2 \tan^{-1} \left(\frac{1}{\sqrt{J^2 - 1}} \right) - 2J + 2\sqrt{J^2 - 1} \right]$$

which is of the form


with $J \geq 1$

$$M = \phi + F P_{2VT}(J)$$

with $F = \frac{f_s}{f_0}$ and

$$P_{2VT}(J) = \frac{1}{2\pi} \left[\frac{1}{J} - 2 \tan^{-1} \left(\frac{1}{\sqrt{J^2 - 1}} \right) - 2(J + \sqrt{J^2 - 1}) \right]$$
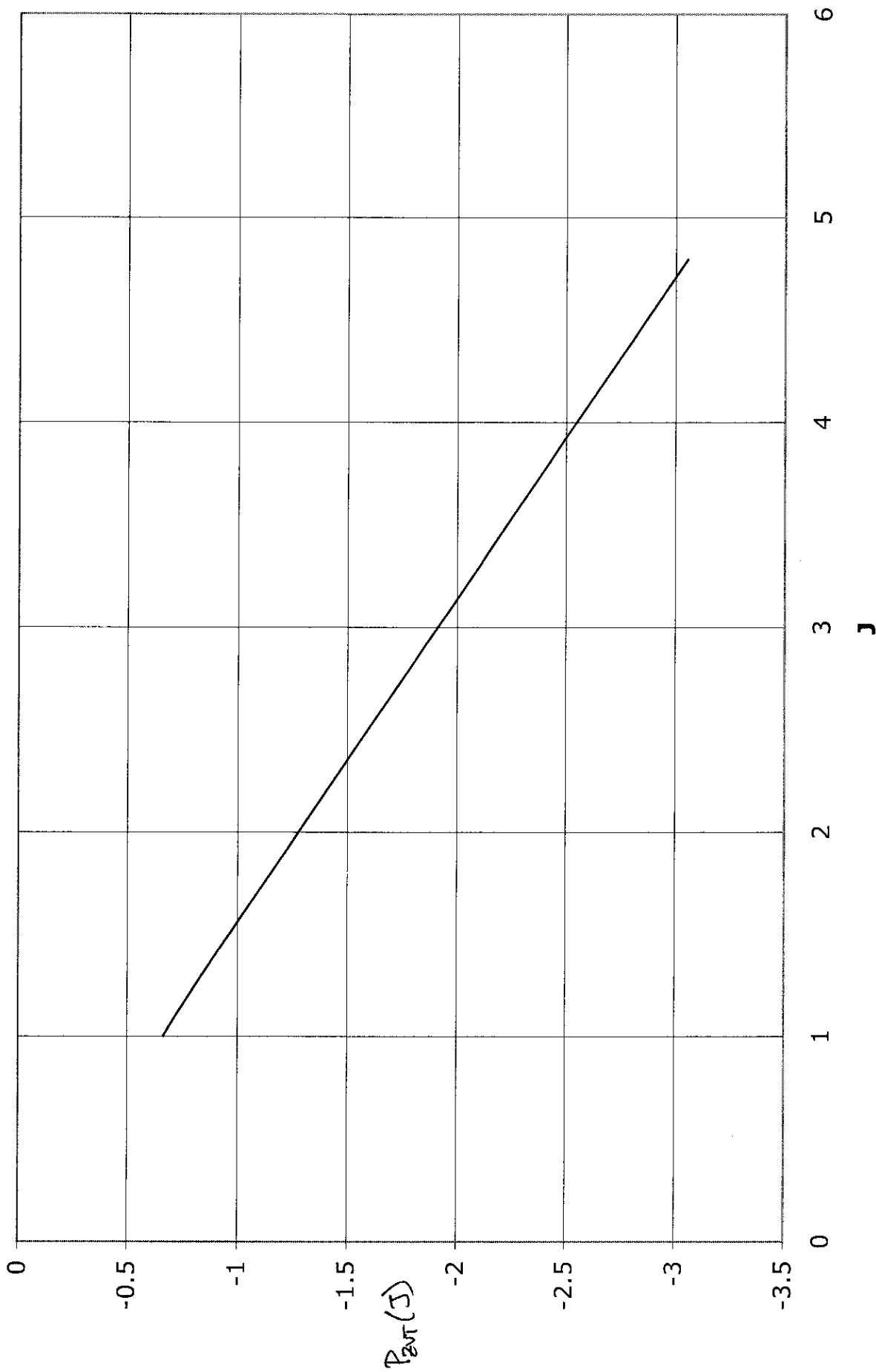
$$ZVT: M = \frac{V}{nV_0} = \phi + F P_{ZVT}(J), \quad F = \frac{f_s}{f_0}, \quad P_{ZVT}(J) = \frac{1}{2\pi} \left[\frac{1}{J} - 2 \tan^{-1} \frac{1}{\sqrt{J^2-1}} - 2(J + \sqrt{J^2-1}) \right]$$



$P_{2VT}(J)$ is negative and not very large in magnitude.

Also, if the resonant transitions are a small fraction of the switching period, then $F \ll 1$.

Hence $|FP_{2VT}(J)| \ll 1$, and $M \approx \emptyset$.

The exact M is slightly smaller than \emptyset .